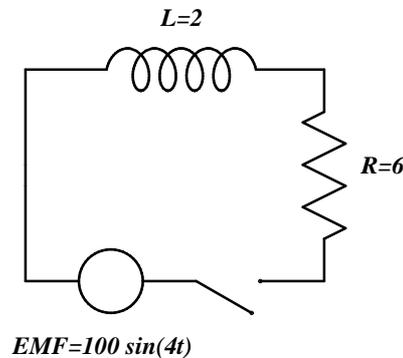


**III. Example 2: R-L AC Circuit**

Physical characteristics of the circuit: EMF  $E(t) = 100 \sin(4t)$  connected in series with a 2 henry inductor and a 6 ohm resistor; current flows when the open switch is closed.

**Questions:**

- [a] Describe in words how the current changes over time.
- [b] What is the current 1 second after the switch is closed?
- [c] At what time does the current equal 8 amps?
- [d] What is the largest current achieved and when is it achieved?

**Solution of IVP.**

By Kirchoff's laws we have:  $E_L + E_R = EMF$  which translates, with  $E_L = L \cdot I'(t)$  and  $E_R = R \cdot I(t)$ , into the following Initial Value Problem (for  $t \geq 0$ ):

$$2 I'(t) + 6 I(t) = 100 \sin(4t), \quad I(t) = 0 \quad \text{at} \quad t = 0$$

After looking closely at this ODE, we realize that we cannot use the method of separation of variables because the variables  $I$  and  $t$  cannot be isolated on separate sides of the equality sign.

A common technique to solve ODEs like this one is to introduce an *integrating factor*.

**Outline of solution by *integrating factor***

After dividing both sides of the ODE in

$$2 I'(t) + 6 I(t) = 100 \sin(4t), \quad I(t) = 0 \quad \text{at} \quad t = 0$$

by 2, we get the ODE in standard form

$$I' + 3I = 50 \sin(4t) \tag{*}$$

Since 3 is the coefficient of  $I$  in (\*), then the integrating factor

$$\mu = e^{\int 3 dt} = e^{3t}$$

Multiply both side of (\*) by  $\mu$  and integrate to get

$$e^{3t}I = e^{3t}[-8 \cos(4t) + 6 \sin(4t)] + C$$

Divide through by  $e^{3t}$  and use the initial condition  $I(0) = 0$  in order to get the circuit current


$$I(t) = -8 \cos(4t) + 6 \sin(4t) + 8e^{-3t}$$

More details for all these steps may be found below, after the Answers.
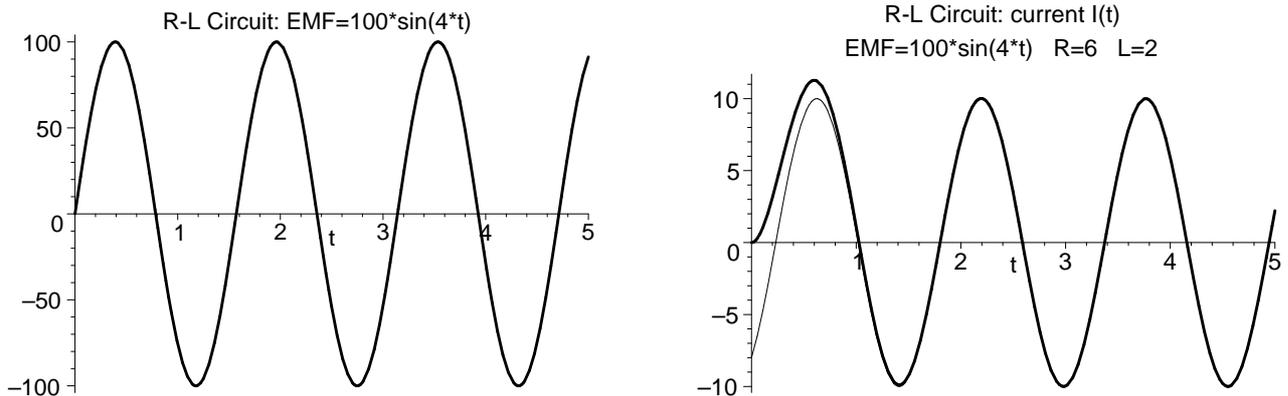
### Answers:

[a] Describe in words how the current changes over time.

The graph below left is that of the EMF  $E(t) = 100 \sin(4t)$  which oscillates with amplitude 100 and completes one cycle in period  $2\pi/4 = \pi/2 \approx 1.57$  seconds. The graph of  $I$  shown below right (dark curve) suggests that the current soon after  $t = 0$  also appears oscillatory with amplitude 10 and period  $\pi/2$ .



To establish this last observation, we first see that after a couple of seconds, the “transient term”  $8e^{-3t}$  of the current is very nearly 0, at which time

$$I \approx -8 \cos(4t) + 6 \sin(4t)$$

We can use trigonometry identities to write this as

$$I \approx 10 \sin(4t + \phi)$$

where

$$\phi = 2 \arctan \frac{-8}{6 + \sqrt{(-8)^2 + (6)^2}} = 2 \arctan(-0.5) \text{ radians} \approx -53^\circ$$


is called the *phase angle*. The initial portion of the graph of  $10 \sin(4t + \phi)$  is shown as a lighter colored curve in the last graph. So indeed, after the transient term dies off, the current behaves like the EMF: oscillating with amplitude 10, period  $\pi/2$ , and with a horizontal time shift.

[b] What is the current 1 second after the switch is closed?

$$I(1) = -8 \cos(4) + 6 \sin(4) + 8e^{-3} \approx 1.0866 \text{ amps}$$

[c] At what time does the current equal 8 amps?

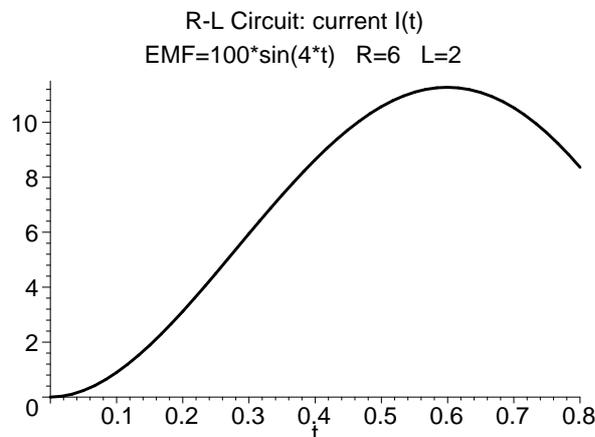From the oscillatory behavior of  $I(t)$  we see that it equals 8 amps infinitely many times. Using a graphing calculator we get an approximation (by tracing the curve or zooming) for the *first time*  $I(t) = 8$  at  $t \approx 0.374$  seconds. The following plot suggests this answer is correct. Also, we should numerically check that  $I(0.374) \approx 7.99$ .



[d] What is the largest current achieved and when is it achieved?

Using a graphing calculator, we get the maximum current to be about 11.27 amps at about 0.6 seconds after the switch is closed. See the preceding graph of  $I(t)$ .

**Details of solution** by *integrating factor*

After dividing both sides of the ODE in

$$2I'(t) + 6I(t) = 100 \sin(4t), \quad I(t) = 0 \quad \text{at} \quad t = 0$$

by 2, we get the ODE in standard form

$$I' + 3I = 50 \sin(4t) \quad (*)$$

and the left hand side of this ODE reminds us of the product rule for derivatives

$$[f(t)g(t)]' = f'(t)g(t) + f(t)g'(t)$$

In fact, if we let  $f(t) = I(t)$  and  $g(t) = e^{3t}$  then we have

$$[Ie^{3t}]' = [I]'e^{3t} + I[e^{3t}]' = I'e^{3t} + 3Ie^{3t}$$

So if we multiply both sides of equation (\*) by the *integrating factor*  $\mu = e^{\int 3 dt} = e^{3t}$ , we get:

$$\begin{aligned} I'e^{3t} + 3Ie^{3t} &= 50e^{3t} \sin(4t) \\ [Ie^{3t}]' &= 50e^{3t} \sin(4t) \\ Ie^{3t} &= 50 \int e^{3t} \sin(4t) dt \end{aligned}$$

when we integrate. The right hand side of the last equation is calculated (see, for example, chapter 5 of Stewart: **Calculus—Concepts and Contexts**, 2nd ed, and in particular Example 4 on p. 399) by the method of *integration by parts*, which gives us

$$Ie^{3t} = 50e^{3t} \left[ \frac{-4}{3^2 + 4^2} \cos(4t) + \frac{3}{3^2 + 4^2} \sin(4t) \right] + C$$

Multiplying both sides of this last equation by  $e^{-3t}$  and simplifying the fractions, we are left with

$$I(t) = -8 \cos(4t) + 6 \sin(4t) + Ce^{-3t}$$

Using the initial condition  $I(0) = 0$  we get

$$\begin{aligned} 0 = I(0) &= -8 \cos(0) + 6 \sin(0) + Ce^0 \\ \implies 0 &= -8 + 0 + C \cdot 1 \\ \implies 0 &= -8 + C \\ \implies C &= 8 \end{aligned}$$

So for any time  $t$  we have the current

$$I(t) = -8 \cos(4t) + 6 \sin(4t) + 8e^{-3t}$$