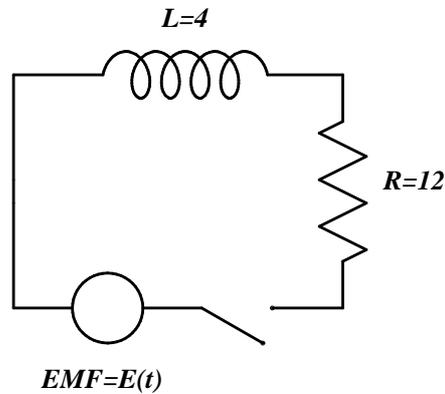


III. Example 2: R-L Circuit with general EMF

Physical characteristics of the circuit: a 4 henry inductor and a 12 ohm resistor connected in series with an unspecified EMF $E(t)$; current flows when the open switch is closed.



Task: Determine the circuit current formula in terms of the unknown EMF function $E(t)$.

Solution:

By Kirchhoff's laws we have: $E_L + E_R = EMF$ which, with $E_L = L \cdot I'(t)$ and $E_R = R \cdot I(t)$, translates into the following Initial Value Problem (for $t \geq 0$):

$$4I'(t) + 12I(t) = E(t), \quad I(t) = 0 \quad \text{at} \quad t = 0$$

We will use the method of *integrating factors*.

[a] Put the ODE in standard form.

After dividing through by the coefficient of $I'(t)$ the ODE

$$4I'(t) + 12I(t) = E(t)$$

becomes

$$I'(t) + 3I(t) = \frac{1}{4}E(t)$$

[b] Determine the integrating factor μ .

From the general standard form ODE $y' + p(x)y = q(x)$ we recognize that

$$I'(t) + 3I(t) = \frac{1}{4}E(t)$$

has $p(t) = 3$ and so

$$\mu = e^{\int p(t) dt} = e^{\int 3 dt} = e^{3t}$$

[c] Multiply the standard form ODE by the integrating factor.

Standard form:

$$I' + 3I = \frac{1}{4}E(t)$$

Integrating factor:

$$\mu = e^{3t}$$

Product:

$$e^{3t}I' + 3e^{3t}I = \frac{1}{4}e^{3t}E(t)$$

[d] Use the product rule for derivatives to simplify the preceding equation so that $[\mu I]'$ is on one side of it.

By the product rule

$$e^{3t}I' + 3e^{3t}I = [e^{3t}I]'$$

So the preceding ODE

$$e^{3t}I' + 3e^{3t}I = \frac{1}{4}e^{3t}E(t)$$

is equivalent to

$$[e^{3t}I]' = \frac{1}{4}e^{3t}E(t)$$

[e] Integrate both sides of the preceding equation with respect to t .

Integrating both sides of

$$[e^{3t}I]' = \frac{1}{4}e^{3t}E(t)$$

yields

$$e^{3t}I = \frac{1}{4} \int e^{3t}E(t) dt$$

For our purposes, it is better to write this in terms of a *definite* integral:

$$e^{3t}I = \frac{1}{4} \int_0^t e^{3u}E(u) du + C$$

(This is part of “The Fundamental Theorem of Calculus, Part 1”; see, for example, p 382 of Stewart: **Calculus—Concepts and Contexts**, 2nd ed.)

[f] Solve the preceding equation for the solution I .

From

$$e^{3t}I = \frac{1}{4} \int_0^t e^{3u}E(u) du + C$$

we get

$$I = \frac{1}{4}e^{-3t} \int_0^t e^{3u}E(u) du + Ce^{-3t}$$

Using the initial condition $I(0) = 0$ we solve for C :

$$\begin{aligned}
 0 = I(0) &= \frac{1}{4}e^0 \int_0^0 e^{3u} E(u) du + C e^0 \\
 \implies 0 &= \frac{1}{4} \cdot 1 \cdot 0 + C \cdot 1 \\
 \implies 0 &= 0 + C \\
 \implies C &= 0
 \end{aligned}$$


So the current can be evaluated at any time t by

$$I(t) = \frac{1}{4}e^{-3t} \int_0^t e^{3u} E(u) du \tag{*}$$

Application: Let's look at the case when the EMF in the circuit is a 60 volt battery that is turned on at the same time the circuit switch is closed at $t = 0$ and then turned off $1/2$ second later. We represent $E(t)$ as a *piecewise defined function*

$$E(t) = \begin{cases} 60, & \text{if } 0 \leq t < 1/2 \\ 0, & \text{if } 1/2 \leq t \end{cases}$$

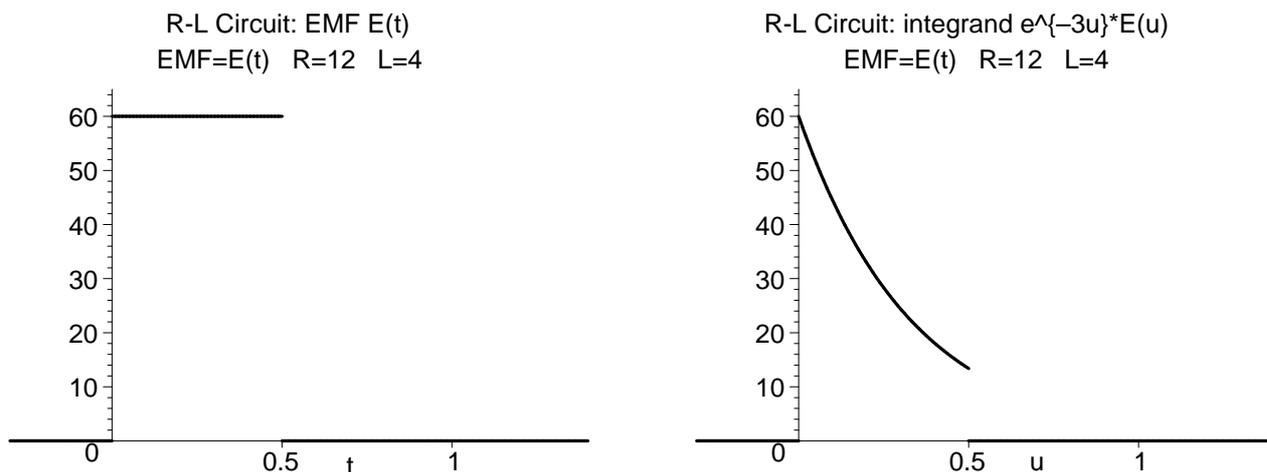The following two plots show both the EMF (lower left) and the integrand of the integral in equation (*) (lower right).



Our formula in equation (*) is based on computing the area under the upper right curve between $u = 0$ and $u = t$. Since that curve “changes” at $t = 1/2$, we have two cases to consider.

Case 1. We have from equation (*) for $0 \leq t < 1/2$:

$$\begin{aligned}
 I(t) &= \frac{1}{4} e^{-3t} \int_0^t e^{3u} E(u) du \\
 &= \frac{1}{4} e^{-3t} \int_0^t e^{3u} 60 du \\
 &= \frac{1}{4} \cdot 60 \cdot e^{-3t} \int_0^t e^{3u} du \\
 &= 15 e^{-3t} \cdot \left. \frac{1}{3} e^{3u} \right]_{u=0}^{u=t} \\
 &= 5 e^{-3t} (e^{3 \cdot t} - e^{3 \cdot 0}) \\
 &= 5 e^{-3t} (e^{3t} - e^0) \\
 &= 5 (e^{-3t} \cdot e^{3t} - e^{-3t} \cdot 1) \\
 &= 5 (1 - e^{-3t})
 \end{aligned}$$

And if the battery is not turned off, this would be the current for all $t \geq 0$.

Case 2. For $1/2 \leq t$:


$$\begin{aligned}
 I(t) &= \frac{1}{4} e^{-3t} \int_0^t e^{3u} E(u) du \\
 &= \frac{1}{4} e^{-3t} \left(\int_0^{1/2} e^{3u} 60 du + \int_{1/2}^t e^{3u} 0 du \right) \\
 &= 5 e^{-3t} (e^{3/2} - e^0) + 0 \\
 &= 5 (e^{3/2} - 1) e^{-3t}
 \end{aligned}$$

using steps similar to Case 1.

Putting the results of these two cases together:

$$I(t) = \begin{cases} 5 (1 - e^{-3t}), & \text{if } 0 \leq t < 1/2 \\ 5 (e^{3/2} - 1) e^{-3t}, & \text{if } 1/2 \leq t \end{cases}$$

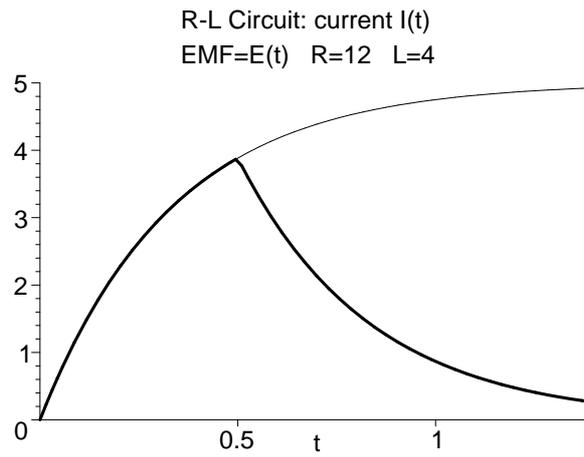This current shown in the next graph as the thicker curve with the thinner curve representing the current if the battery is not switched off at $t = 1/2$.



Can you see how the current changes when no longer driven by the 60 volt EMF?