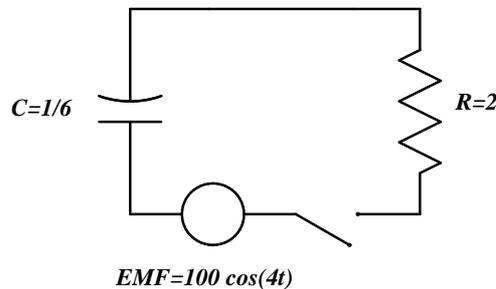


**III. Practice Problem 1: R-C AC Circuit**

**Task:** Work on solving for the charge and current for the given circuit; indicated links give (partial) solutions.



An R-C circuit consists of a  $100 \cos(4t)$  volt AC generator connected in series with a 2 henry inductor and a  $1/6$  farad capacitor; there is no initial charge on the capacitor and no current flows until the switch is closed. The associated Initial Value Problem is

$$2Q'(t) + \frac{Q(t)}{1/6} = 100 \cos(4t), \quad Q(0) = 0$$

**Method of Integrating Factor:**

- [a] Put the ODE in standard form.
- [b] Determine the integrating factor  $\mu$ .
- [c] Multiply the standard form ODE by the integrating factor.
- [d] Use the product rule for derivatives to simplify the preceding equation so that  $[\mu Q]'$  is on one side of it.
- [e] Integrate both sides of the preceding equation with respect to  $t$ .
- [f] Solve the preceding equation for the general solution  $Q$ .
- [g] Use the initial condition to determine the charge  $Q(t)$  for this circuit.
- [h] Determine the current  $I(t)$  for this circuit.

[a] Put the ODE in standard form.

$$2Q'(t) + \frac{Q(t)}{1/6} = 100 \cos(4t)$$

becomes

$$Q'(t) + 3Q(t) = 50 \cos(4t)$$

[b] Determine the integrating factor  $\mu$ .

From the general standard form ODE  $y' + p(x)y = q(x)$  we recognize that

$$Q'(t) + 3Q(t) = 50 \cos(4t)$$

has  $p(t) = 3$  and so

$$\mu = e^{\int p(t) dt} = e^{\int 3 dt} = e^{3t}$$

[c] Multiply the standard form ODE by the integrating factor.

Standard form:

$$Q'(t) + 3Q(t) = 50 \cos(4t)$$

Integrating factor:

$$\mu = e^{3t}$$

Product:

$$e^{3t}Q' + 3e^{3t}Q = 50e^{3t} \cos(4t)$$

[d] Use the product rule for derivatives to simplify the preceding equation so that  $[e^{3t} Q]'$  is on one side of it.

By the product rule

$$e^{3t} Q' + 3 e^{3t} Q = [e^{3t} Q]'$$

So the preceding ODE

$$e^{3t} Q' + 3 e^{3t} Q = 50 e^{3t} \cos(4t)$$

is equivalent to

$$[e^{3t} Q] = 50 e^{3t} \cos(4t)$$

[e] Integrate both sides of the preceding equation with respect to  $t$ .

Integrating both sides of

$$[e^{3t} Q]' = 50 e^{3t} \cos(4t)$$

yields

$$e^{3t} Q = \int 50 e^{3t} \cos(4t) dt$$

[f] Solve the preceding equation for the general solution  $Q$ .

Using integration by parts on the right hand side of

$$e^{3t}Q = \int 50 e^{3t} \cos(4t) dt$$

we get

$$e^{3t}Q = 50 e^{3t} \left[ \frac{3}{3^2 + 4^2} \cos(4t) + \frac{4}{3^2 + 4^2} \sin(4t) \right] + C$$

which, after simplifying the numbers and dividing both sides by  $e^{3t}$ , becomes

$$Q(t) = 6 \cos(4t) + 8 \sin(4t) + C e^{-3t}$$

[g] Use the initial condition to determine the charge  $Q(t)$  for this circuit.

From the general solution

$$Q(t) = 6 \cos(4t) + 8 \sin(4t) + C e^{-3t}$$

in the preceding part we have at  $t = 0$

$$Q(0) = 6 \cos(0) + 8 \sin(0) + C e^0 = 6 \cdot 1 + 8 \cdot 0 + C = 6 + C$$

whereas by the initial condition from the IVP we have

$$Q(0) = 0$$

So these two equations together imply that

$$6 + C = 0 \quad \text{or} \quad C = -6$$

Putting this  $C$  into the general solution yields the circuit charge

$$Q(t) = 6 \cos(4t) + 8 \sin(4t) - 6 e^{-3t}$$

[h] Determine the current  $I(t)$  for this circuit.

Since current is the time derivative of charge  $I(t) = Q'(t)$  we get from the preceding part

$$I(t) = [6 \cos(4t) + 8 \sin(4t) - 6 e^{-3t}]'$$

or

$$I(t) = -24 \sin(4t) + 32 \sin(4t) + 18e^{-3t}$$

for  $t > 0$ .