

Electric Circuit Exercises

Setting Up Electric Circuit ODE and Verifying Solution

In each of the following problems you are to: [a] use Kirchhoff's law to write down the Initial Value Problem — ODE and initial condition(s) — for the given circuit ; [b] show that the given function is the solution to the IVP . (The quantities R , L , C , and E below do not necessarily represent realistic physical electric circuits.)

1. [a] $L = 25$ henries, $R = 50$ ohms, no capacitor, constant EMF $E(t) = 100$ volts, initial current is 0 amps when the switch is closed; [b] $I(t) = 2 - 2e^{-2t}$
2. [a] No inductor, $R = 30$ ohms, $C = 0.01$ farads, constant EMF $E(t) = 50$ volts, initial charge is 0 coulombs when the switch is closed; [b] $Q(t) = \frac{1}{2} - \frac{1}{2}e^{-10t/3}$
3. [a] $L = 25$ henries, $R = 25$ ohms, no capacitor, decaying EMF $E(t) = 50e^{-2t}$ volts, initial current is 0 amps when the switch is closed; [b] $I(t) = 2e^{-t} - 2e^{-2t}$
4. [a] No inductor, $R = 25$ ohms, $C = 0.01$ farads, decaying EMF $E(t) = 50e^{-2t}$ volts, initial charge is 0 coulombs when the switch is closed; [b] $Q(t) = e^{-2t} - e^{-4t}$
5. [a] $L = 15$ henries, $R = 40$ ohms, no capacitor, oscillatory EMF $E(t) = 50 \cos(6t)$ volts, initial current is 0 amps; [b] $I(t) = \frac{1}{97} (20 \cos(6t) + 45 \sin(6t) - 20e^{-8t/3})$
6. [a] No inductor, $R = 25$ ohms, $C = 0.005$ farads, oscillatory EMF $E(t) = 50 \cos(6t)$ volts, initial charge is 0 coulombs; [b] $Q(t) = \frac{1}{25} (4 \cos(6t) + 3 \sin(6t) - 4e^{-8t})$
7. [a] A simple series circuit consists of 25 ohm resistor, a 25 henry inductor, and an EMF $E(t) = 20e^{-3t} + 10e^{-6t}$ volts; the initial current is 0 amps when the switch is closed; [b] $I(t) = \frac{1}{25} (12e^{-t} - 10e^{-3t} - 2e^{-6t})$
8. [a] A simple series circuit consists of a 20 ohm resistor, a 0.01 farad capacitor, and an EMF $E(t) = 20e^{-3t} + 10e^{-6t}$ volts; the initial charge on the capacitor is 0 coulombs when the switch is closed; [b] $Q(t) = \frac{1}{2} (e^{-3t} - e^{-6t})$
9. [a] A simple series circuit consists of 25 ohm resistor, a 25 henry inductor, and a decaying oscillatory EMF $E(t) = 50e^{-3t} \cos(4t)$ volts; the initial current is 0 amps when the switch is closed; [b] $I(t) = \frac{1}{5} (e^{-t} - e^{-3t} \cos(4t) + 2e^{-3t} \sin(4t))$
10. [a] A simple series circuit consists of a 25 ohm resistor, a 0.01 farad capacitor, and a decaying oscillatory EMF $E(t) = 50e^{-2t} \cos(6t)$ volts; the initial charge on the capacitor is 0 coulombs when the switch is closed; [b] $Q(t) = \frac{1}{10} e^{-2t} (\cos(6t) + 3 \sin(6t) - e^{-2t})$
11. [a] A simple series circuit consists of a 1 henry inductor, 12 ohm resistor, a 0.01 farad capacitor, and a constant EMF $E(t) = 100$ volts; the initial charge on the capacitor

is 0 coulombs and the current is 0 amps when the switch is closed; [b] $Q(t) = 1 - e^{-6t}(\cos(8t) + (3/4)\sin(8t))$

12. [a] A simple series circuit consists of a 2 henry inductor, 60 ohm resistor, a 0.004 farad capacitor, and a constant EMF $E(t) = 50$ volts; the initial charge on the capacitor is 0 coulombs and the current is 0 amps when the switch is closed; [b] $Q(t) = \frac{1}{5} - \frac{1}{4}e^{-5t} + \frac{1}{20}e^{-25t}$

Electric Circuit Exercises Solving Electric Circuit ODEs

(The quantities R , L , C , and E below do not necessarily represent realistic physical electric circuits.)

13. A simple series circuit consists of a 50 ohm resistor, a 25 henry inductor, and a constant EMF $E(t) = 100$. If the initial current is 0 amps when the switch is closed:
- [a] write down the (DE and initial condition) mathematics model from Kirchhoff's law;
 - [b] determine the current $I(t)$ for any time $t > 0$;
 - [c] compute the current at $t = 0.01$;
 - [d] compute the current at $t = 1.0$;
 - [e] find the "steady-state" current $\lim_{t \rightarrow \infty} I(t)$;
 - [f] approximate the time(s) when the current is at 90% of steady-state.
14. Repeat the preceding problem for a simple series circuit that consists of a 100 ohm resistor, a 25 henry inductor, a constant EMF $E(t) = 50$, and an initial current of 0 amps.
15. A simple series circuit consists of a 30 ohm resistor, a 0.01 farad capacitor, and a constant EMF $E(t) = 50$. If the initial charge on the capacitor is 0 coulombs when the switch is closed:
- [a] write down the (DE and initial condition) mathematics model from Kirchhoff's law;
 - [b] determine the charge $Q(t)$ for any time $t > 0$;
 - [c] compute the charge at $t = 0.01$;
 - [d] compute the charge at $t = 1.0$;
 - [e] find the "steady-state" charge $\lim_{t \rightarrow \infty} Q(t)$;
 - [f] approximate the time(s) when the charge is at 90% of steady-state.
16. Repeat the preceding problem for a simple series circuit that consists of a 50 ohm resistor, a 0.005 farad capacitor, a constant EMF $E(t) = 100$, and an initial charge of 0 coulombs.
17. A simple series circuit consists of a 25 ohm resistor, a 25 henry inductor, and a decaying EMF $E(t) = 50e^{-2t}$. If the initial current is 0 amps when the switch is closed:
- [a] write down the (DE and initial condition) mathematics model from Kirchhoff's law;
 - [b] determine the current $I(t)$ for any time $t > 0$;
 - [c] compute the current at $t = 0.01$;
 - [d] compute the current at $t = 1.0$;

- [e] approximate what the maximum current is and the time when it is achieved.
18. Repeat the preceding problem for a simple series circuit that consists of a 40 ohm resistor, a 10 henry inductor, a decaying EMF $E(t) = 50e^{-4t}$, and an initial current of 0 amps.
19. A simple series circuit consists of a 25 ohm resistor, a 0.01 farad capacitor, and a decaying EMF $E(t) = 50e^{-2t}$. If the initial charge on the capacitor is 0 coulombs when the switch is closed:
- [a] write down the (DE and initial condition) mathematics model from Kirchhoff's law;
 - [b] determine the charge $Q(t)$ for any time $t > 0$;
 - [c] compute the charge at $t = 0.01$;
 - [d] compute the charge at $t = 1.0$;
 - [e] approximate what the maximum charge is and the time when it is achieved.
20. Repeat the preceding problem for a simple series circuit that consists of a 25 ohm resistor, a 0.01 farad capacitor, a decaying EMF $E(t) = 50e^{-4t}$, and an initial charge of 0 coulombs.
21. A simple series circuit consists of a 40 ohm resistor, a 15 henry inductor, and an oscillatory EMF $E(t) = 50 \cos(6t)$. If the initial current is 0 amps when the switch is closed:
- [a] write down the (DE and initial condition) mathematics model from Kirchhoff's law;
 - [b] determine the current $I(t)$ for any time $t > 0$;
 - [c] compute the current at $t = 0.01$;
 - [d] compute the current at $t = 1.0$;
 - [e] identify the "steady-state" current as an oscillatory function.
22. Repeat the preceding problem for a simple series circuit that consists of a 25 ohm resistor, a 15 henry inductor, an oscillatory EMF $E(t) = 50 \cos(3t)$, and an initial current of 0 amps.
23. A simple series circuit consists of a 25 ohm resistor, a 0.005 farad capacitor, and an oscillatory EMF $E(t) = 50 \cos(6t)$. If the initial charge on the capacitor is 0 coulombs when the switch is closed:
- [a] write down the (DE and initial condition) mathematics model from Kirchhoff's law;
 - [b] determine the charge $Q(t)$ for any time $t > 0$;
 - [c] compute the charge at $t = 0.01$;
 - [d] compute the charge at $t = 1.0$;
 - [e] identify the "steady-state" charge as an oscillatory function.
24. Repeat the preceding problem for a simple series circuit that consists of a 25 ohm resistor, a 0.005 farad capacitor, an oscillatory EMF $E(t) = 50 \cos(3t)$, and initial charge 0 coulombs.
25. A simple series circuit consists of a 25 ohm resistor, a 25 henry inductor, and an EMF $E(t) = 20e^{-3t} + 10e^{-6t}$. If the initial current is 0 amps when the switch is closed:
- [a] write down the (DE and initial condition) mathematics model from Kirchhoff's law;
 - [b] determine the current $I(t)$ for any time $t > 0$;

-
- [c] compute the current at $t = 0.01$;
- [d] compute the current at $t = 1.0$;
- [e] approximate what the maximum current is and the time when it is achieved.
- 26.** Repeat the preceding problem for a simple series circuit that consists of a 20 ohm resistor, a 5 henry inductor, an EMF $E(t) = 20e^{-t} + 10e^{-4t}$, and an initial current of 0 amps.
- 27.** A simple series circuit consists of a 20 ohm resistor, a 0.01 farad capacitor, and an EMF $E(t) = 20e^{-3t} + 10e^{-6t}$. If the initial charge on the capacitor is 0 coulombs when the switch is closed:
- [a] write down the (DE and initial condition) mathematics model from Kirchhoff's law;
- [b] determine the charge $Q(t)$ for any time $t > 0$;
- [c] compute the charge at $t = 0.01$;
- [d] compute the charge at $t = 1.0$;
- [e] approximate what the maximum charge is and the time when it is achieved.
- 28.** Repeat the preceding problem for a simple series circuit that consists of a 20 ohm resistor, a 0.01 farad capacitor, an EMF $E(t) = 20e^{-t} + 10e^{-4t}$, and an initial charge of 0 coulombs when the switch is closed.
- 29.** A simple series circuit consists of a 25 ohm resistor, a 25 henry inductor, and a decaying oscillatory EMF $E(t) = 50e^{-3t} \cos(4t)$. If the initial current is 0 amps when the switch is closed:
- [a] write down the (DE and initial condition) mathematics model from Kirchhoff's law;
- [b] determine the current $I(t)$ for any time $t > 0$;
- [c] compute the current at $t = 0.01$;
- [d] compute the current at $t = 1.0$;
- [e] approximate what the maximum current is and the time when it is achieved.
- 30.** Repeat the preceding problem for a simple series circuit that consists of a 15 ohm resistor, a 30 henry inductor, a decaying EMF $E(t) = 50e^{-2t} \cos(6t)$ and an initial current of 0 amps.
- 31.** A simple series circuit consists of a 25 ohm resistor, a 0.01 farad capacitor, and a decaying oscillatory EMF $E(t) = 50e^{-2t} \cos(6t)$. If the initial charge on the capacitor is 0 coulombs when the switch is closed:
- [a] write down the ODE and initial condition mathematics model from Kirchhoff's law;
- [b] determine the charge $Q(t)$ for any time $t > 0$;
- [c] compute the charge at $t = 0.01$;
- [d] compute the charge at $t = 1.0$;
- [e] approximate what the maximum charge is and the time when it is achieved.
- 32.** Repeat the preceding problem for a simple series circuit that consists of a 25 ohm resistor, a 0.01 farad capacitor, a decaying oscillatory EMF $E(t) = 50e^{-4t} \cos(3t)$, and a charge of 0 coulombs when the switch is closed.

- 33.** A simple series circuit consists of a 50 ohm resistor, a 25 henry inductor, and an EMF $E(t)$ that is a constant 100 volt battery that drives the circuit for one second and then is disconnected. If the initial current is 0 amps when the switch is closed, then determine the current $I(t)$ for any time $t > 0$. [Suggestion: first solve the problem for an EMF that is constantly 100 volts, then determine the current $I(1)$ and use this value as the initial value for the same circuit with an EMF of 0 volts. Piece these two solutions together to get the current for the given circuit.]
- 34.** A simple series circuit consists of a 50 ohm resistor, a 0.01 farad capacitor, and an EMF $E(t)$ that is a constant 25 volt battery that drives the circuit for one second and then is disconnected. If the initial charge on the capacitor is 0 coulombs when the switch is closed, then determine the charge $Q(t)$ for any time $t > 0$. [Suggestion: first solve the problem for an EMF that is constantly 25 volts, then determine the charge $Q(1)$ and use this value as the initial value for the same circuit with an EMF of 0 volts. Piece these two solutions together to get the charge for the given circuit.]
- 35.** A simple series circuit consists of a 100 ohm resistor, a 25 henry inductor, and an EMF $E(t)$ that is a constant 50 volt battery that drives the circuit for two seconds and then is disconnected. If the initial current is 0 amps when the switch is closed, then determine the current $I(t)$ for any time $t > 0$.
- 36.** A simple series circuit consists of a 20 ohm resistor, a 0.01 farad capacitor, and an EMF $E(t)$ that is a constant 50 volt battery that drives the circuit for two seconds and then is disconnected. If the initial charge on the capacitor is 0 coulombs when the switch is closed, then determine the charge $Q(t)$ for any time $t > 0$.
- 37.** Use an appropriate integrating factor to solve the following ODE:
- [a] $\frac{dy}{dx} - y = 2e^{3x}$
- [b] $xy' + 2y = x \cos(x^3)$
- [c] $LI'(t) + RI(t) = V$ where L , R , and V are positive constants.
- 38.** A simple series circuit consists of a varying resistance of $50/(1 + 0.5t)$ ohms, a 25 henry inductor, and a constant EMF $E(t) = 100$. If the initial current is 0 amps when the switch is closed: [a] write down the (DE and initial condition) mathematics model from Kirchoff's law; [b] determine the current $I(t)$ for any time $t > 0$.
- 39.** A simple series circuit consists of a 50 ohm resistor, a varying capacitance of $0.005 + 0.01t$ farads, and a constant EMF $E(t) = 100$. If the initial charge on the capacitor is 0 coulombs when the switch is closed: [a] write down the (DE and initial condition) mathematics model from Kirchoff's law; [b] determine the charge $Q(t)$ for any time $t > 0$;