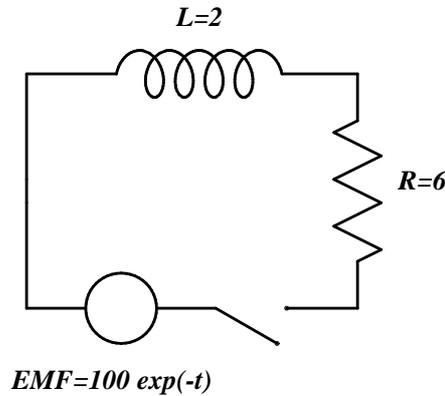


### III. Example 1: R-L Circuit with decaying EMF

Physical characteristics of the circuit: EMF  $E(t) = 100e^{-t}$  connected in series with a 2 henry inductor and a 6 ohm resistor; current flows when the open switch is closed.



#### Questions:

- [a] Describe in words how the current changes over time.
- [b] What is the current 1 second after the switch is closed?
- [c] At what time does the current equal 8 amps?
- [d] What is the largest current achieved and when is it achieved?

#### Solution:

By Kirchoff's laws we have  $E_L + E_R = EMF$  which, with  $E_L = L \cdot I'(t)$  and  $E_R = R \cdot I(t)$ , translates into the following Initial Value Problem (for  $t \geq 0$ ):

$$2I'(t) + 6I(t) = 100e^{-t}, \quad I(t) = 0 \quad \text{at} \quad t = 0$$

A common technique to solve DEs like this one is to introduce an *integrating factor*. After dividing through by 2 in order to get the DE into what is called "standard form"

$$I' + 3I = 50e^{-t} \tag{*}$$

the left side of the DE reminds us of the product rule for derivatives

$$[f(t)g(t)]' = f'(t)g(t) + f(t)g'(t)$$

In fact, if we let  $f(t) = I(t)$  and  $g(t) = e^{3t}$  then we have

$$[Ie^{3t}]' = [I]'e^{3t} + I[e^{3t}]' = I'e^{3t} + 3Ie^{3t}$$

So if we multiply both sides of equation (\*) by the *integrating factor*  $\mu = e^{\int 3 dt} = e^{3t}$ , we get

$$I'e^{3t} + 3Ie^{3t} = 50e^{-t}e^{3t}$$

or

$$[Ie^{3t}]' = 50e^{2t}$$

When we integrate both sides of the preceding equation we have

$$\begin{aligned} Ie^{3t} &= 50 \int e^{2t} dt \\ &= 25e^{2t} + C \end{aligned}$$

We can solve for current  $I$  by multiplying through this last equation by  $e^{-3t}$ :

$$I(t) = 25e^{-t} + C e^{-3t}$$

Again, the initial condition  $I(0) = 0$  allows us to determine  $C$  from the last equation

$$\begin{aligned} 0 &= I(0) = 25e^0 + C e^0 \\ \implies 0 &= 25 \cdot 1 + C \cdot 1 \\ \implies 0 &= 25 + C \\ \implies C &= -25 \end{aligned}$$



Hence for any time  $t$ :

$$I(t) = 25(e^{-t} - e^{-3t})$$

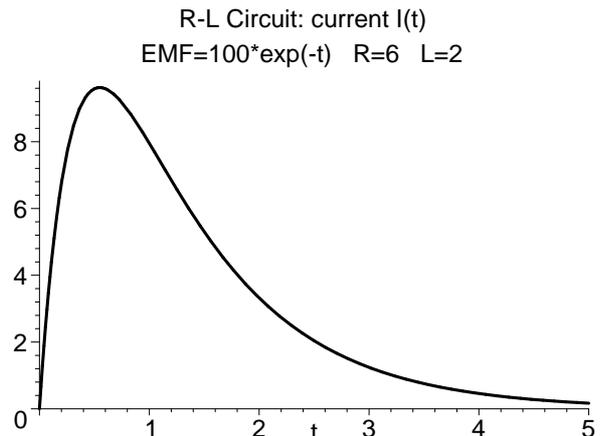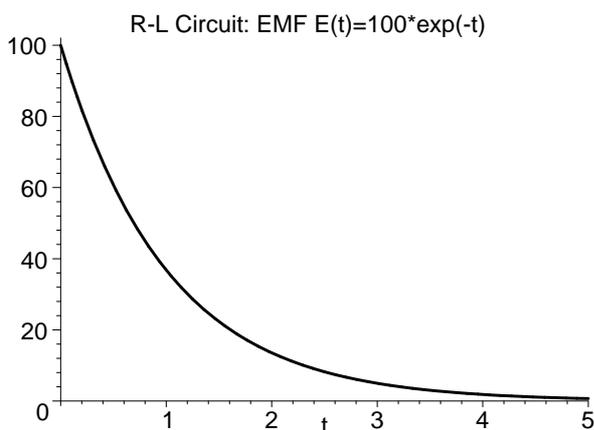**Answers:**

[a] Describe in words how the current changes over time.


The graph below left is that of the EMF  $E(t) = 100e^{-t}$  which starts out at 100 and quickly decays toward 0. The graph of  $I$  shown below right suggests that the current starts out growing like the case where the EMF is a constant 100 but then dies off since the EMF dies off.



[b] What is the current 1 second after the switch is closed?

$$I(1) = 25 (e^{-1} - e^{-3}) \approx 7.95$$

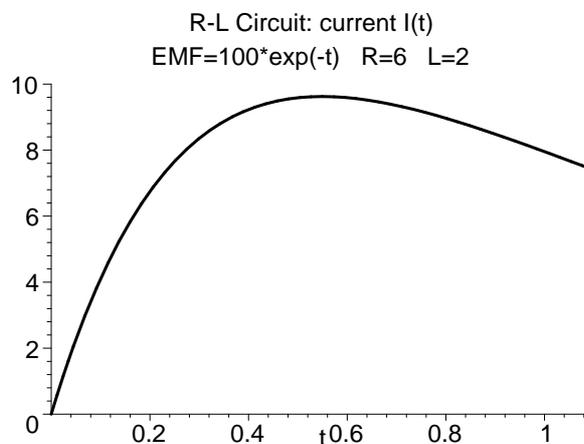which agrees with the following plot of  $I(t)$ .



[c] At what time does the current equal 8 amps?

We can use our graphing calculator to trace the solution curve and zoom to see that it equals 8 at two times:  $t \approx 0.27$  and  $t \approx 0.99$ . Check these with the preceding graph of  $I(t)$ .

[d] What is the largest current achieved and when is it achieved?

Again, using a graphing calculator we see that the maximum current  $I \approx 9.62$  at  $t \approx 0.55$  which agrees with the preceding graph of  $I(t)$ .