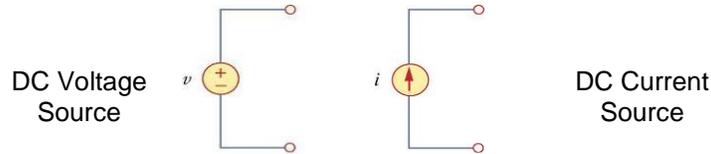


**CURRENT SOURCES / SOURCE CONVERSION**

**Learning Objectives**


- a. Analyze a circuit consisting of a current source, voltage source and resistors.
- b. Convert a current source and a resistor into an equivalent circuit consisting of a voltage source and a resistor.
- c. Evaluate a circuit that contains several current sources in parallel.

**Ideal sources** An ideal source is an active element that provides a specified voltage or current that is completely independent of other circuit elements.



**Constant Current Sources** The voltage across the current source ( $V_S$ ) is *dependent* on how other components are connected to it. Additionally, the current source voltage polarity does not have to follow the current source's arrow!

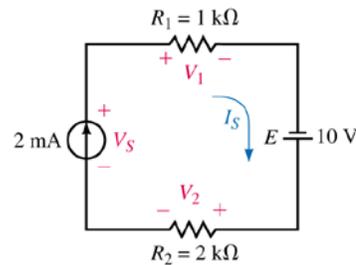Example. Determine  $V_S$  in the circuit shown below.




Solution:

Example. Determine  $V_S$  in the circuit shown above, but with  $R_2$  replaced by a  $6\text{ k}\Omega$  resistor.

Solution:

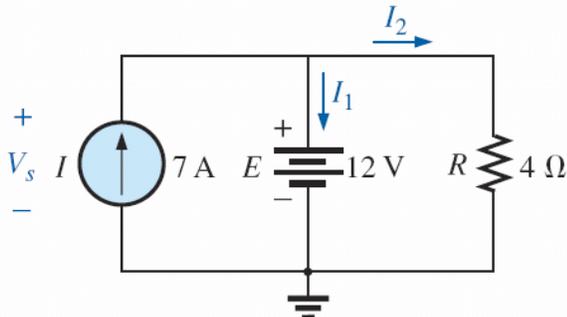Example. Determine  $I_1$  and  $I_2$  in the circuit shown below.




Solution:

Figure taken from Boylestad, *Introductory Circuit Analysis*, 12<sup>th</sup> ed., Prentice Hall, 2010

**EE301 – Lesson 9**  
Reading: Sections 8.1-8.5

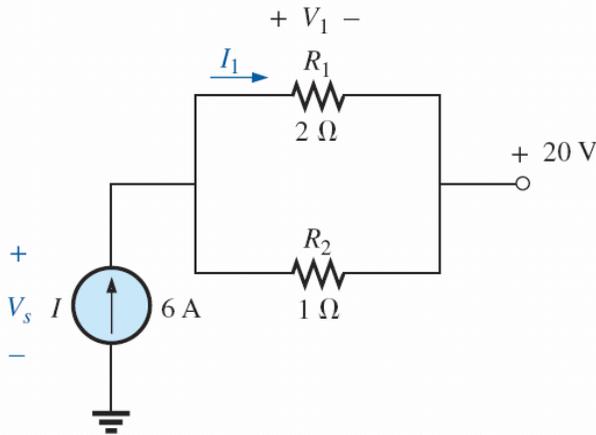
Example. Determine  $I_1$  and  $V_s$  in the circuit shown below.



Solution:


Figure taken from Boylestad, *Introductory Circuit Analysis*, 12<sup>th</sup> ed., Prentice Hall, 2010

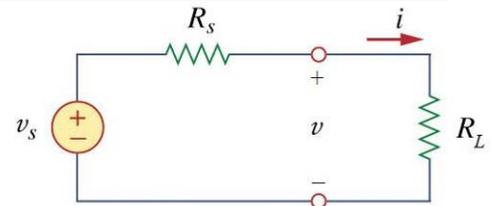**Practical voltage sources** A real or practical source supplies its rated voltage when its terminals are not connected to a load (open-circuited) but its voltage drops off as the current it supplies increases.




We can model a practical voltage source using an ideal source  $V_s$  in series with an internal resistance  $R_s$ .

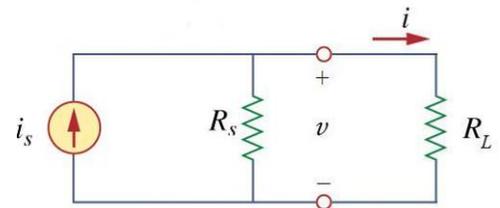**Practical current source** A practical current source supplies its rated current when its terminals are short-circuited but its current drops off as the load resistance increases.



We can model a practical current source using an ideal current source in parallel with an internal resistance  $R_s$ .

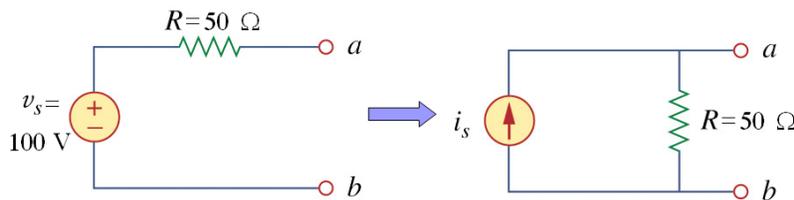**Source transformation: Voltage Source to Current Source** We can, for the purposes of circuit analysis, replace a voltage source  $v_s$  in series with a resistor  $R$  by a current source  $i_s$  in parallel with the same resistor  $R$ .




Question: How do you calculate the new current source value?

Answer:  $i_s = \frac{v_s}{R} = \frac{100}{50} = 2 \text{ A}.$

**EE301 – Lesson 9**  
Reading: Sections 8.1-8.5

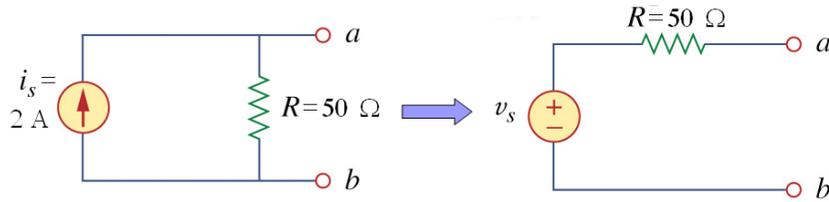**Source transformation: Current Source to Voltage Source** We can replace a current source  $i_s$  in parallel with a resistor  $R$  by a voltage source  $v_s$  in series with the **SAME** resistor  $R$ .



Question: How do you calculate the new voltage source value?

Answer:  $v_s = i_s R = (2A)(50\Omega) = 100\text{ V}$ .

Example. Determine the current  $I_2$  in the circuit shown below.


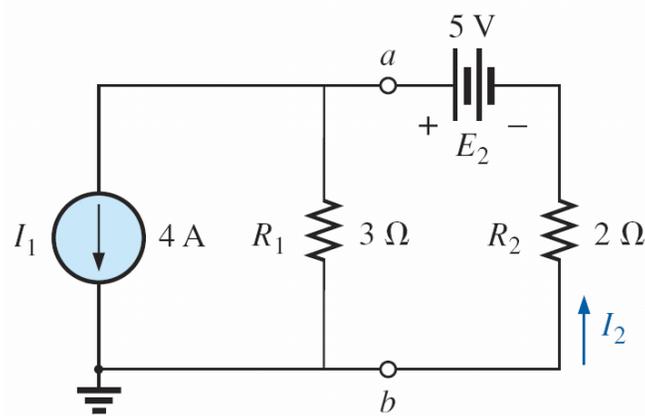


Figure taken from Boylestad, *Introductory Circuit Analysis*, 12<sup>th</sup> ed., Prentice Hall, 2010

Solution:


**EE301 – Lesson 9**  
Reading: Sections 8.1-8.5

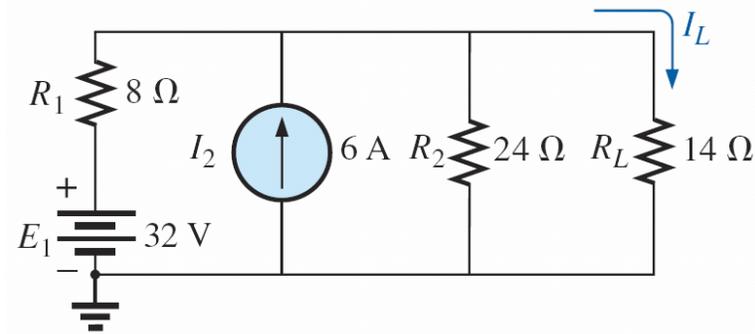Example: Determine  $I_L$  in the circuit shown below:




Solution:

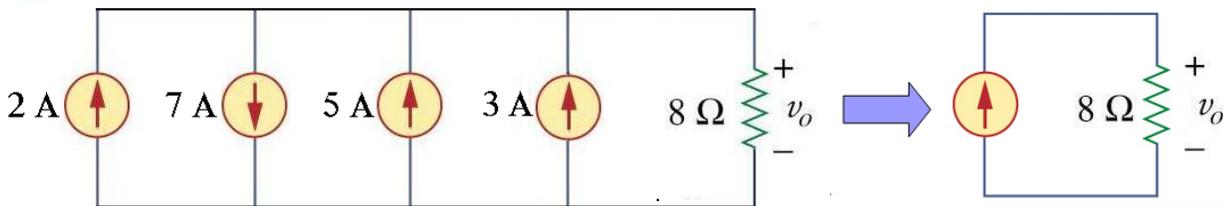**Parallel Current Sources** Parallel current sources simply add together, and can be simplified by a single current source. The value of the single current source on the right is 3 A.




**Current Sources in Series** Don't ever do this! Civilization will collapse and the world will end. And besides, it's against MIDREGS.

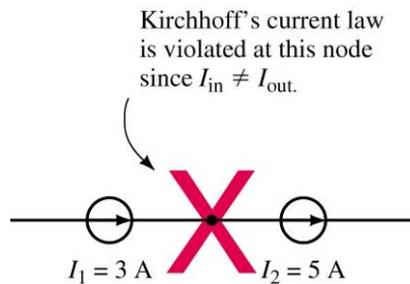

**EE301 – Lesson 9**  
Reading: Sections 8.1-8.5

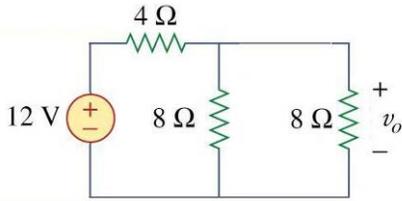
Example. In the circuit below, use a source transformation to determine  $v_o$ .



Solution:

---

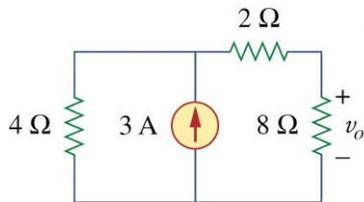
Example. In the circuit below, use a source transformation to determine  $v_o$ .



Solution:

---

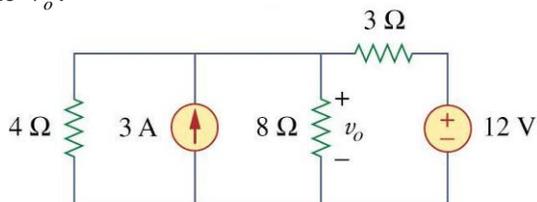
Example. In the circuit below, use a source transformation and the parallel current source rule to determine  $v_o$ .



Solution:


**EE301 – Lesson 9**  
Reading: Sections 8.1-8.5

Example. Determine  $v_o$ .

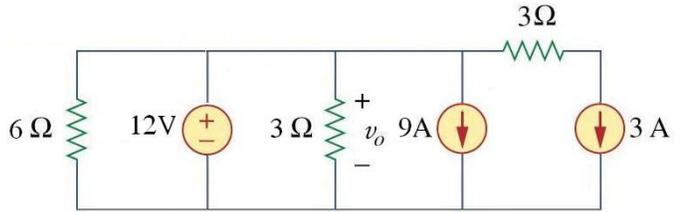

Solution:

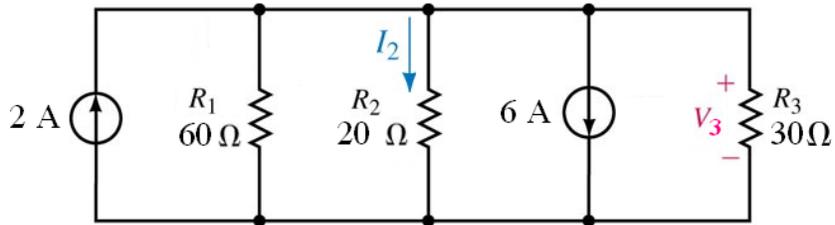Example. Determine  $I_2$  and  $V_3$  in the circuit below.



Solution: