

Name: _____

Section: _____


NOTICE:

1. Detach these last two (2) pages and take them with you. Write your name and section above.
2. Set aside 1 hour in privacy to complete this section using Multisim.
3. You may not discuss the problems with anyone until after you turn in this sheet with the answers to your professor on Monday, 12 September.
4. Complete this sheet by filling in the answers and signing the certification at the bottom of the last page.

III. PART 3

Multisim Problems

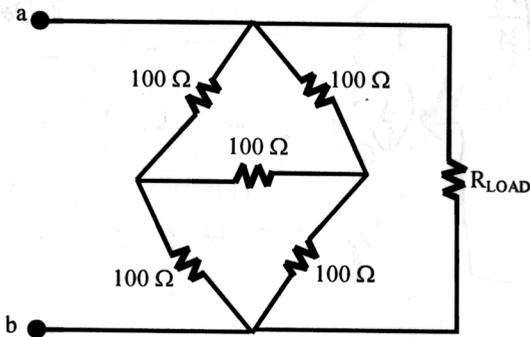22. (2 pts) The input resistance for the circuit below is measured by placing an ohmmeter across the terminals a to b. The bridge network of $100\ \Omega$ resistors is being used so that the input resistance is exactly $50\ \Omega$. Use Multisim to find the value of the resistor R_{LOAD} so that the input resistance is $50\ \Omega$.




*the bridge resistance is $100\ \Omega$
 Put this in parallel
 with $R_{LOAD} = 100\ \Omega$ to
 get a $50\ \Omega$ input resistance*

$R_{LOAD} = \underline{100\ \Omega}$

23. (8 pts) Construct the circuit below in Multisim.

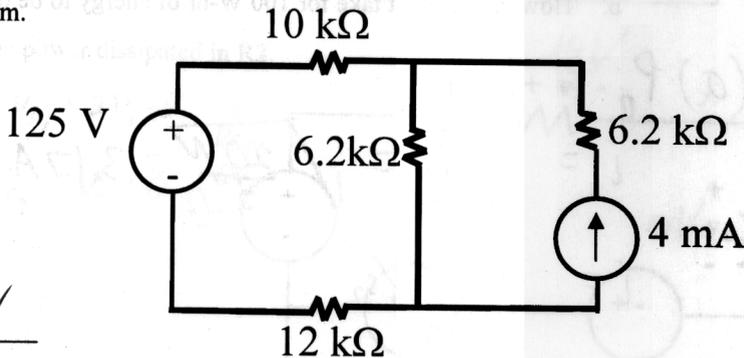- a. Measure the voltage across the $10\ \text{k}\Omega$ resistor.



$V_{10K} = \underline{35.532\ V}$