

Lesson 14: Permanent magnet DC machine speed control

Linear motor summary

$$F = I_A LB$$



force exerted on bar due to current I_A

$$E_A = BLu$$

induced voltage due to velocity of bar u

$$I_A = \frac{V_A - E_A}{R_A}$$

current in the bar

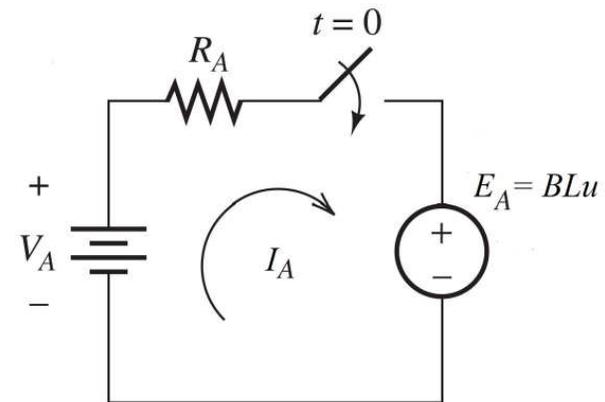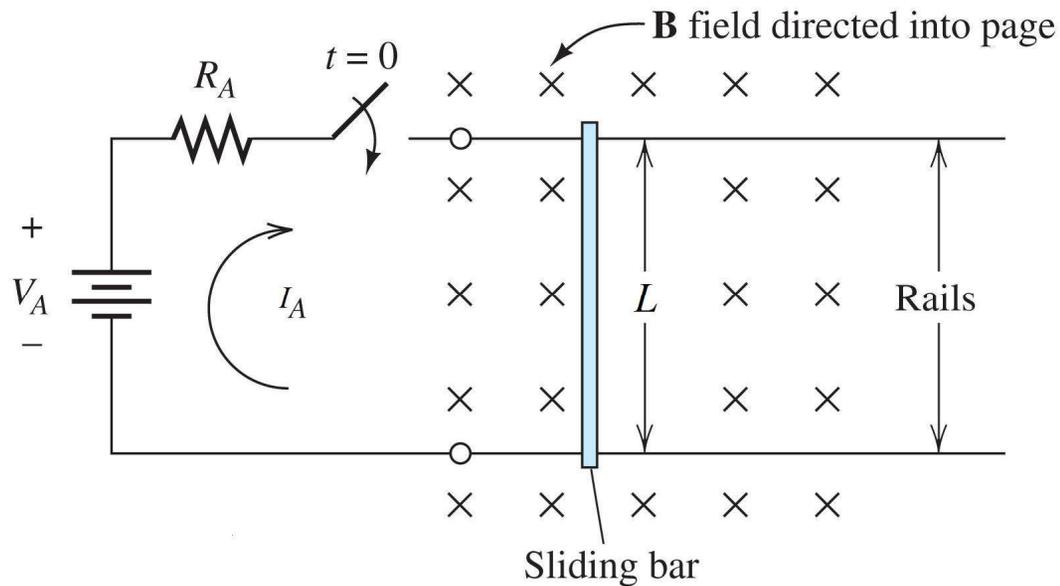



Rotating dc motor summary

$T_e = K_v I_A$ torque developed due to current I_A

$E_A = K_v \omega_m$ back emf due to rotational velocity ω_m



$I_A = \frac{V_T - E_A}{R_A}$ armature current

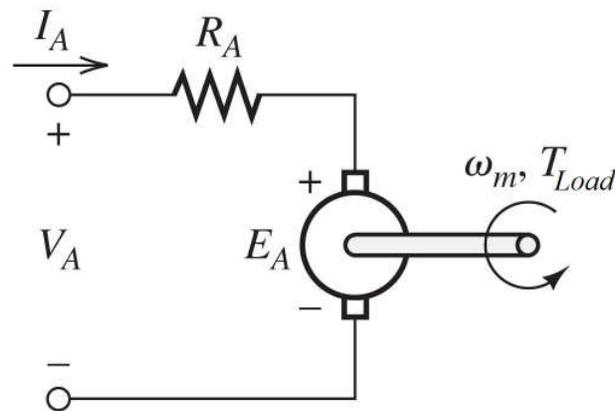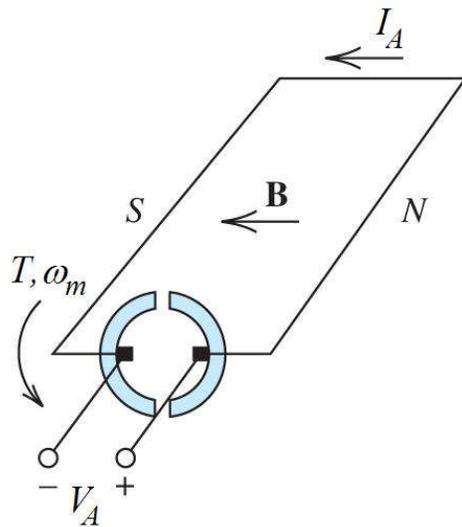$T_{Load} = T_e - T_{Loss}$ output torque




Speed control

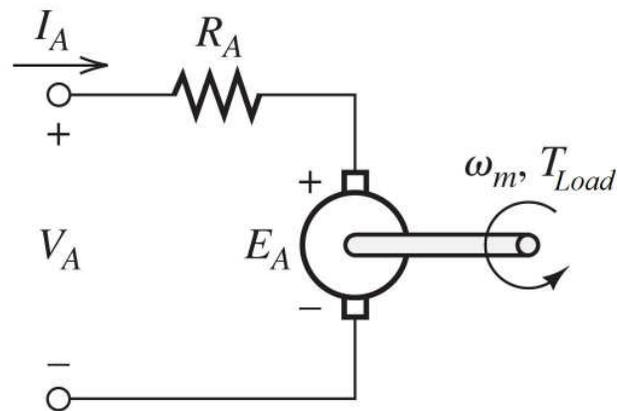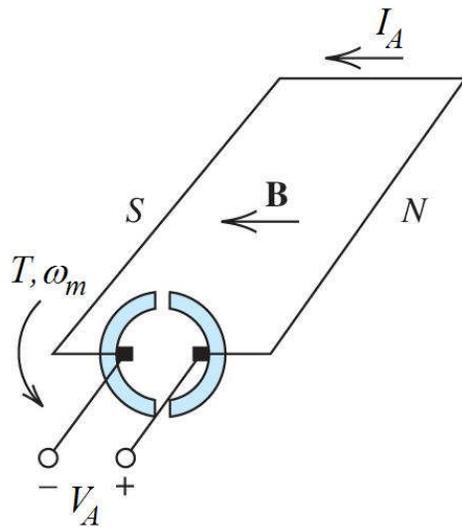- What determines the motor speed ω_m ?
- How can we *control* the motor speed ω_m ?



Torque-speed characteristic

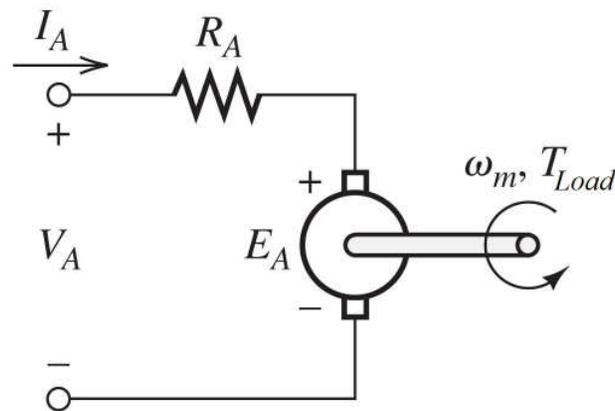
- Steady-state motor speed ω_m is determined by the balance between T_{Load} and T_e . (assuming $T_{Loss} = 0$).
- Write an expression for T_e in terms of V_A .



Torque-speed characteristic


- Write an expression for T_e in terms of V_A .
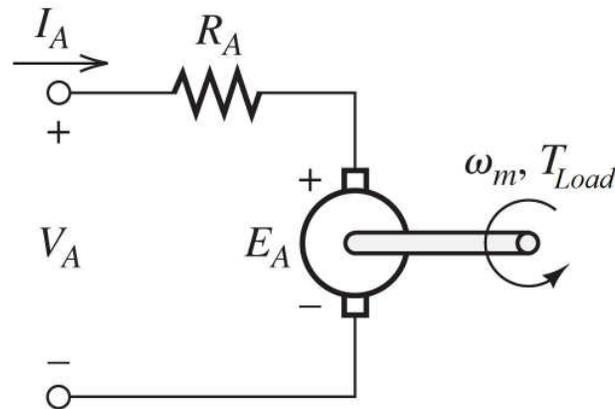
$$\begin{aligned} T_e &= K_v I_A \\ &= K_v \left(\frac{V_T - E_A}{R_A} \right) \\ &= \frac{K_v V_A}{R_A} - \frac{K_v^2}{R_A} \omega_m \end{aligned}$$



Motor torque-speed characteristic
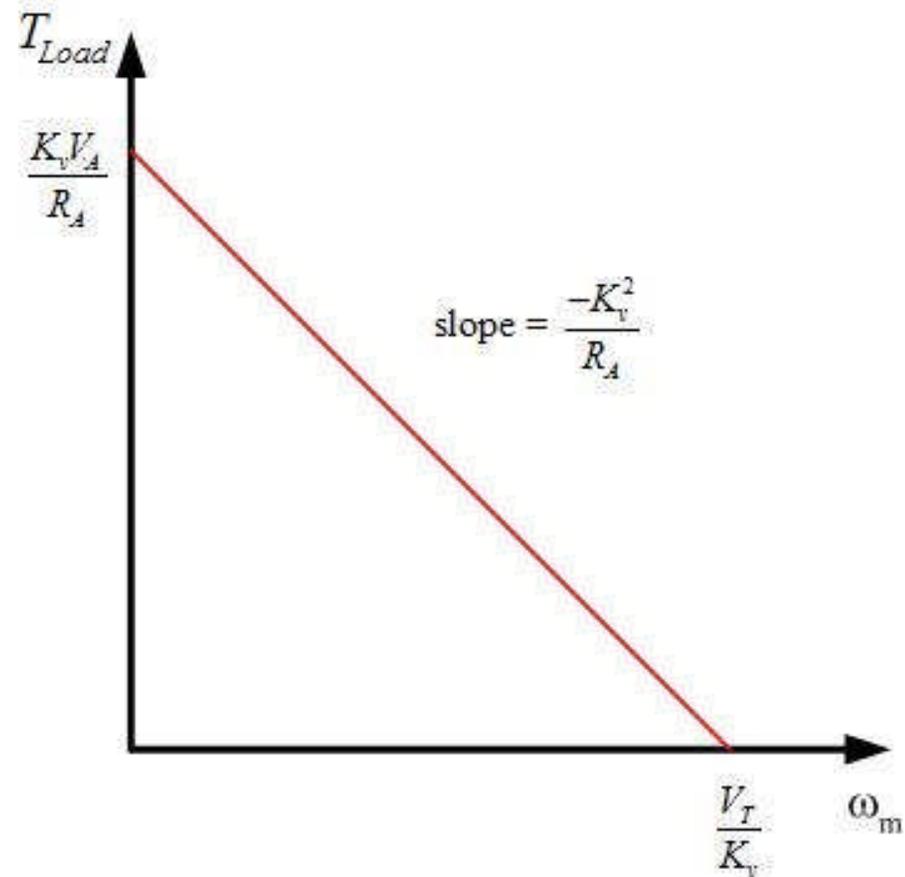
$$T_e = \frac{K_v V_A}{R_A} - \frac{K_v^2}{R_A} \omega_m$$




BMW M3 V-8




The New M3




BMW M3 V8 torque-speed characteristic

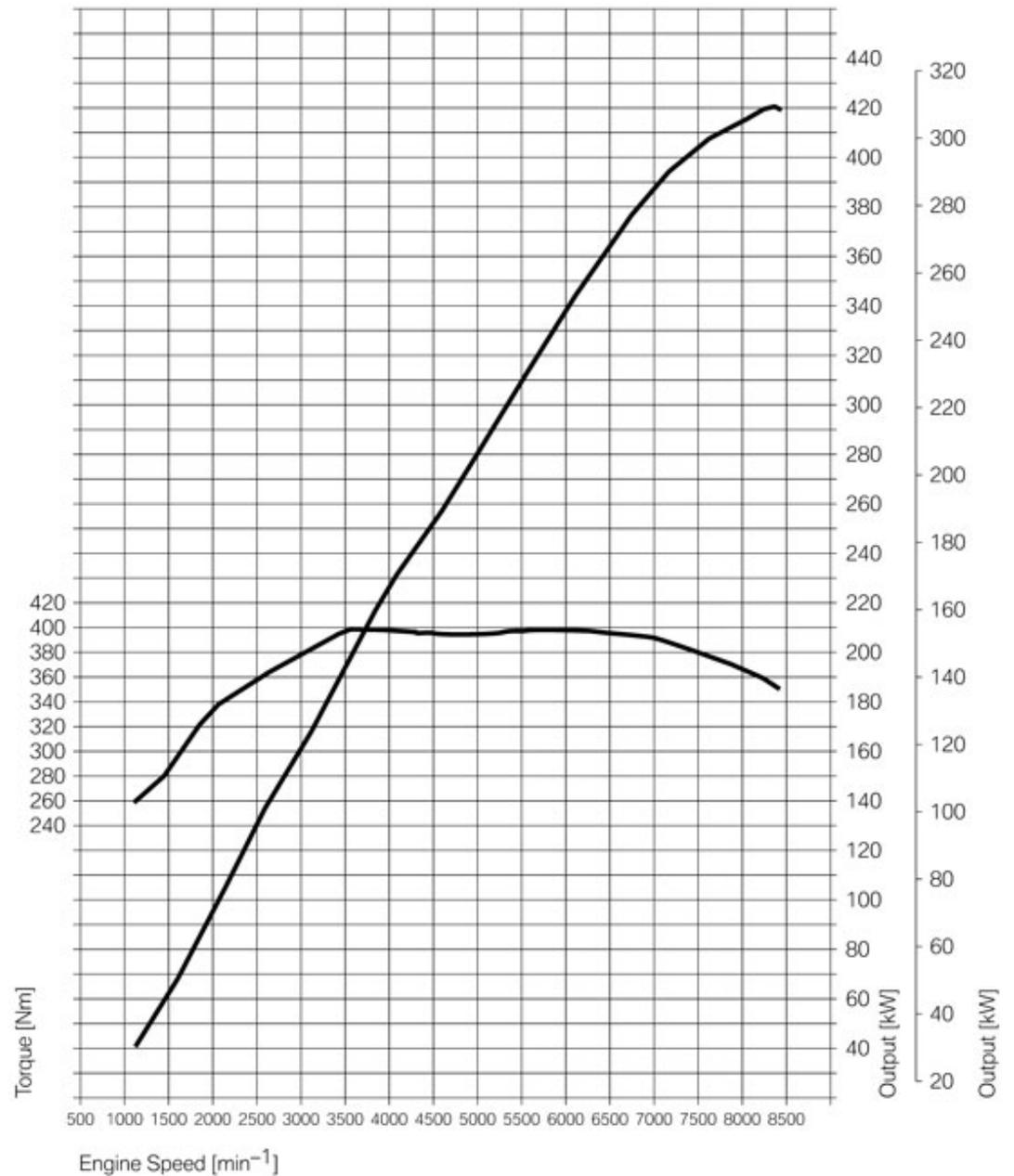

Load torque-speed characteristic

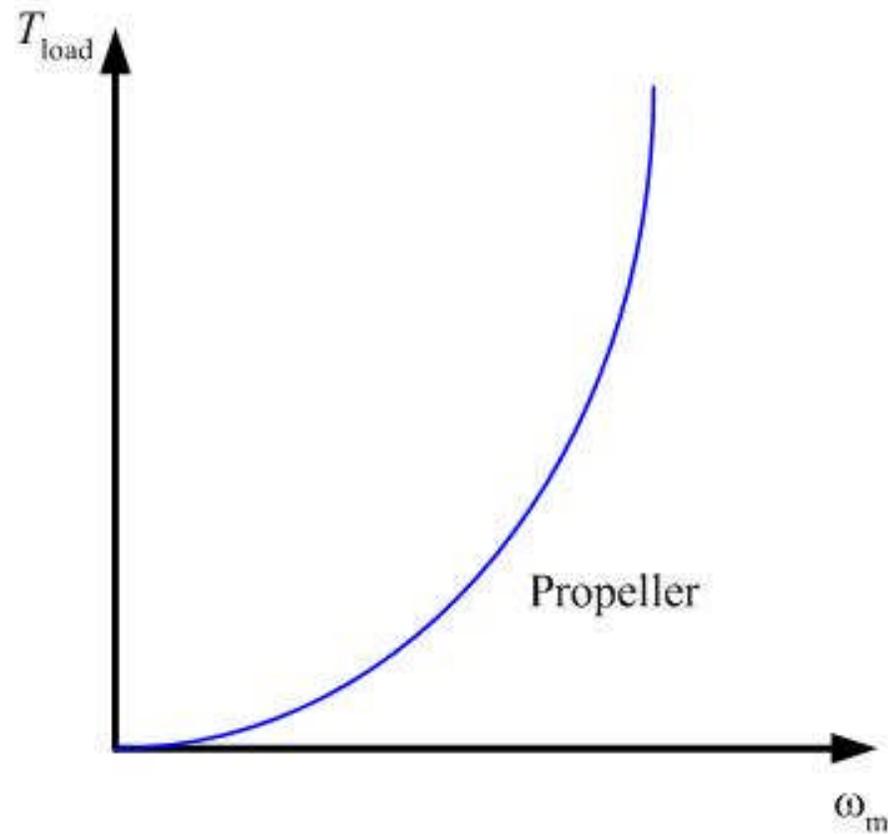

Overlay torque-speed characteristics

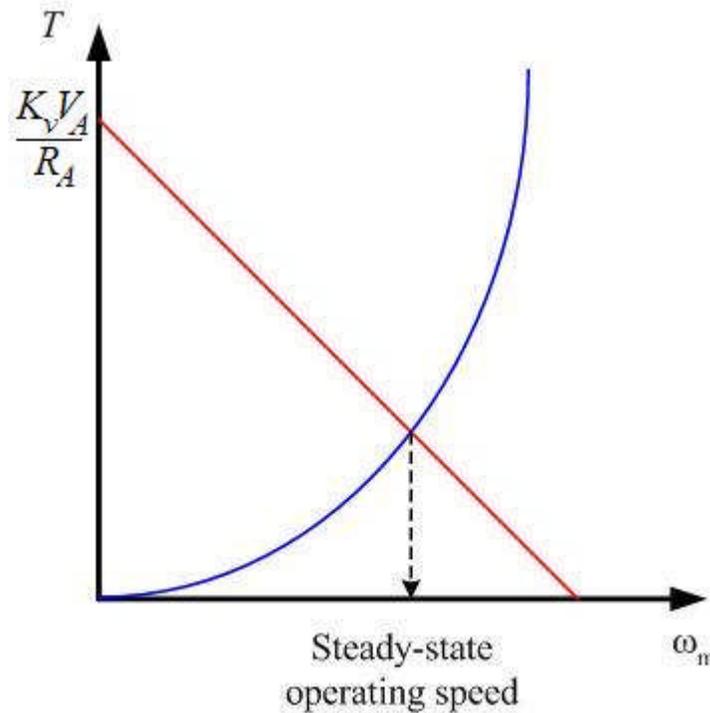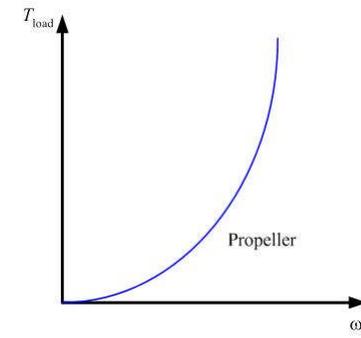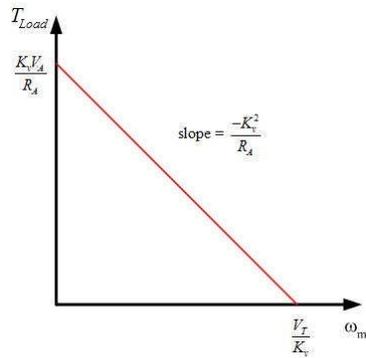




Controlling steady-state speed



- If the load characteristic is fixed, we can adjust the steady-state speed by varying the source voltage V_A .
- Adjusting V_A shifts the motor's torque-speed characteristic vertically yields a new operating point and thus a new steady-state speed.

Controlling steady-state speed

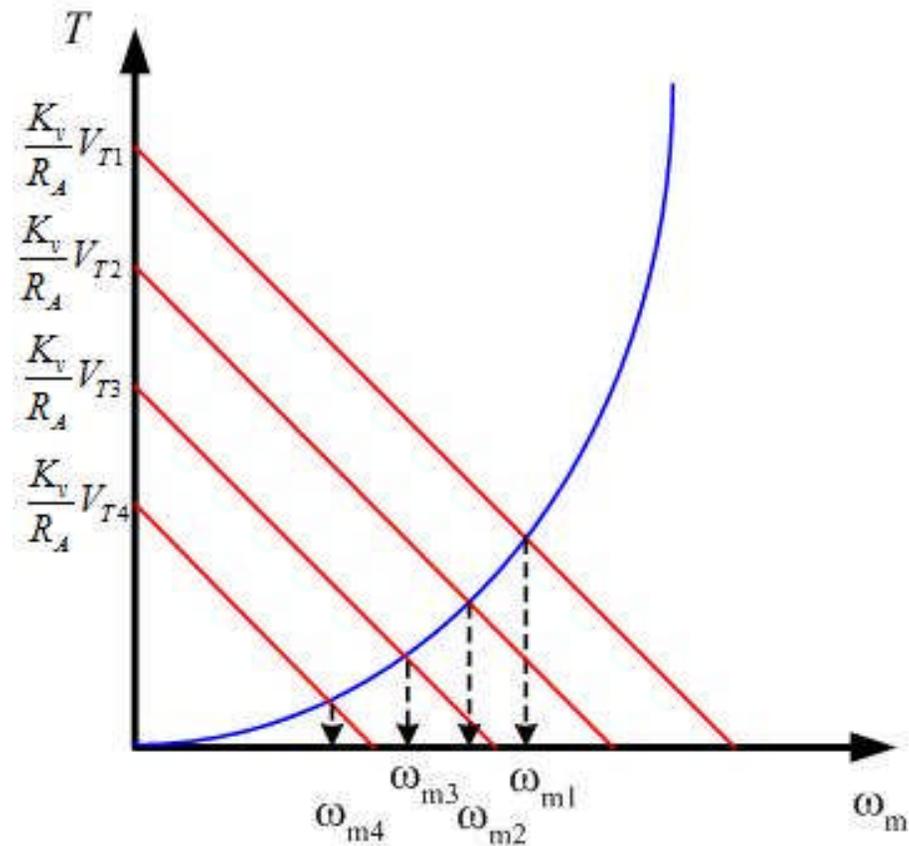


Method of adjusting source voltage

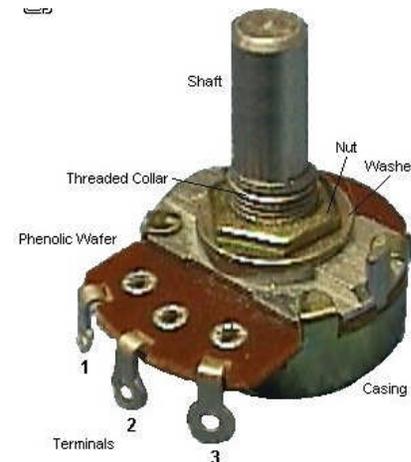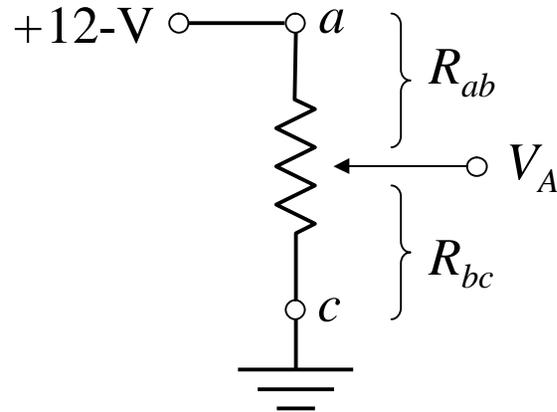- A simple method of adjusting voltage would be to use a variable resistor.
- This is inefficient and impractical for other than small motors.



Method of adjusting source voltage

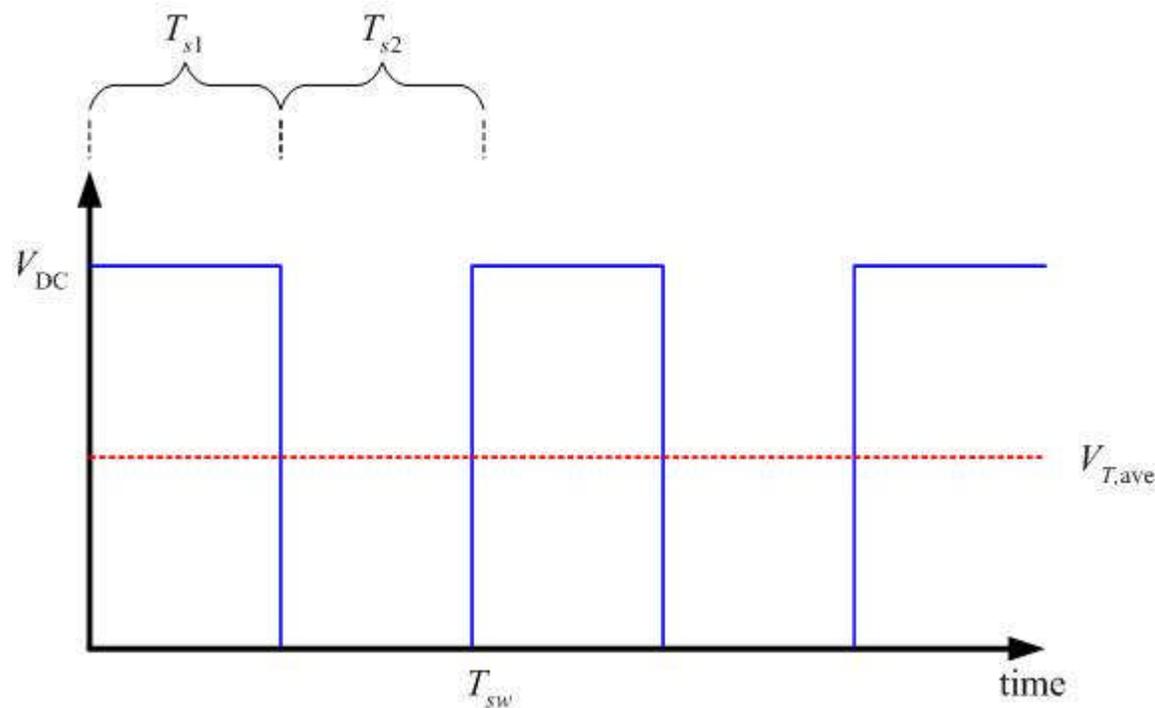
- A more efficient method uses a square wave with an adjustable duty cycle (D).




$$D = \frac{T_{s1}}{T_{sw}}$$

$$V_{A,ave} = \frac{T_{s1} V_{DC}}{T_{sw}} = D V_{DC}$$

Adjusting duty cycle

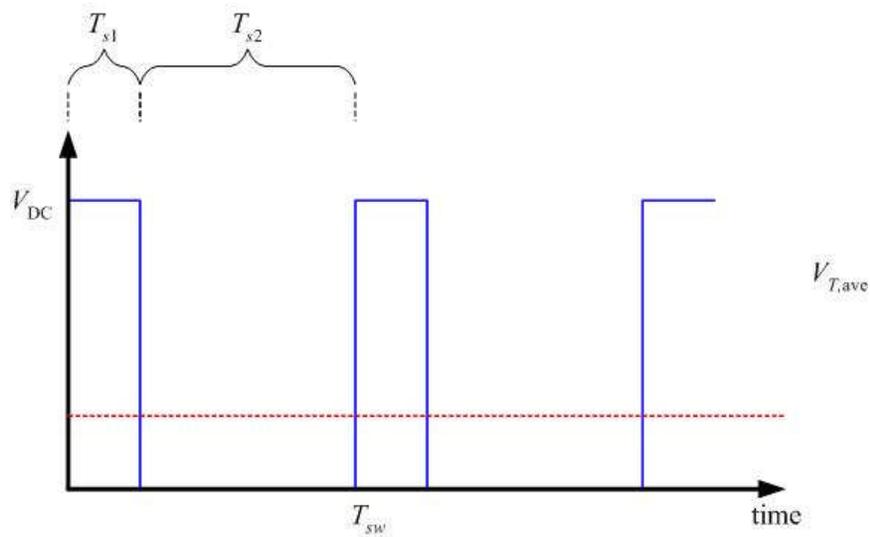

$D = 25\%$

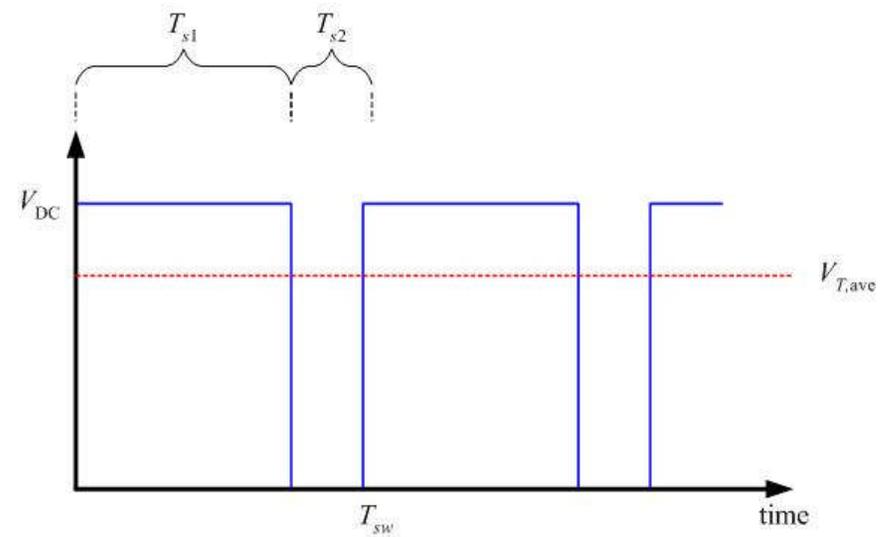


$D = 75\%$



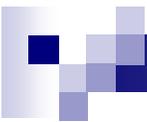Example Problem 1

A permanent magnet DC motor is rated for 24V, 2A and 1500 rpm. If the machine is 85% efficient at rated condition, find R_A and K_v . If $T_{Load} = 0.18$ N·m, what is the new mechanical speed?



Example Problem 2

Suppose we wish to change the speed of the machine in the previous example to operate at 100 rad/s with $T_{\text{load}} = 0.18$ N·m applied, what is the required average armature voltage $V_{A,\text{ave}}$? If the DC voltage is 24 V, what is the required duty cycle?