

## Lesson 17: Transient analysis


### Introduction

- Previously we had only considered resistive circuits.
  - The voltages and currents resulting were constant in time (dc).
- Today we consider simple circuits comprised of either a resistor and capacitor (RC) or resistor and inductor (RL).
  - These will result in \_\_\_\_\_ differential equations.
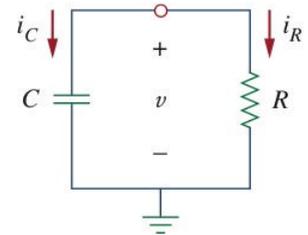
### Source-free RC circuit


Source-free refers a circuit in which the only energy source the energy already stored in the capacitor.

- Consider a dc source previously connected then removed at  $t = 0$ . For the circuit below, assume  $v(0) = V_0$ .
- What is  $v(t)$  for  $t > 0$ ?



Using KCL and evaluating the first-order differential equation with the initial condition  $v(0) = V_0$ , yields

$v(t) =$

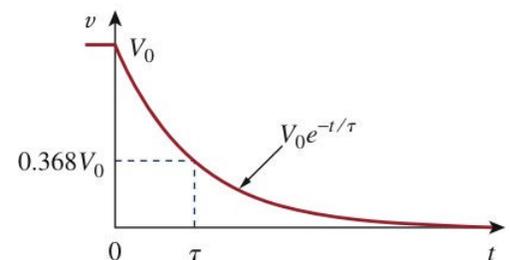

### Natural response

This is known as the \_\_\_\_\_ response of the circuit because it does not depend on any \_\_\_\_\_ of excitation.


### Time constant

The rate of voltage decay is dependent on the time constant  $\tau$  which is given  $\tau =$

The time constant of a circuit is the time required for the response to decay by a factor of  $1/e$  or 36.8 percent of its initial value.

Using the time constant, voltage is given  $v(t) =$

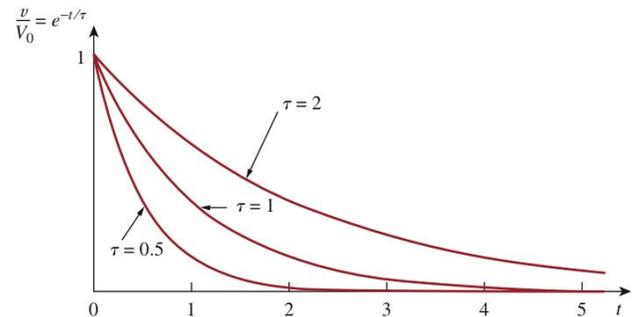For engineering purposes, it is assumed that the capacitor is fully discharged after  $5\tau$  (five time constants).



### Power dissipation

The power dissipated by the resistor is

$$p(t) =$$

The energy absorbed up to time  $t$  is

$$w_R(t) =$$


### Evaluating source-free RC circuits

1. Determine the initial voltage  $v(0) = V_0$  across the capacitor.
2. Find the time constant  $\tau$ . (note: R is often the Thévenin equivalent resistance as seen from the capacitor).

### Source-free RL circuit


Consider source free RL circuit below. Assume that at  $t = 0$ , the inductor has an initial current  $I_0$ .

- What is  $i(t)$  for  $t > 0$ ?

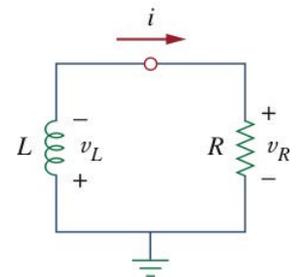

Using KVL and evaluating the first-order differential equation with the initial condition  $i(0) = I_0$  yields

$$i(t) =$$

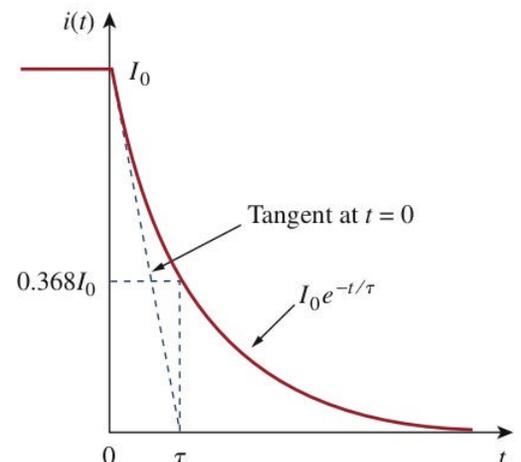

### Power dissipation

The power dissipated by the resistor is  $p(t) =$

The energy absorbed up to time  $t$  is  $w_R(t) =$

### Evaluating source-free RL circuits


1. Determine the initial current  $i(0) = I_0$  through the inductor.
2. Find the time constant  $\tau$ . (note that  $R$  is often the Thévenin equivalent resistance as seen from the inductor).

### Step function

The unit step function is a convenient way to mathematically represent the operation of a \_\_\_\_\_.


The unit step function  $u(t)$  is 0 for  $t < 0$  and 1 for  $t > 0$ .  $u(t) =$

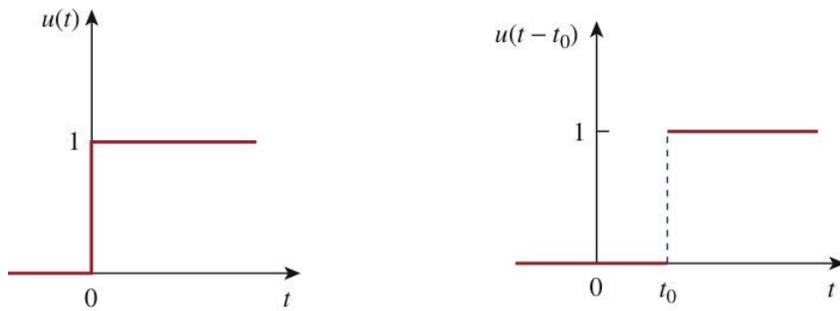The unit step function can be translated horizontally by adjusting its argument.  $u(t - t_0) =$


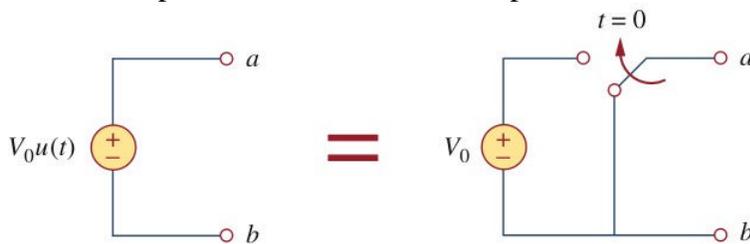
### Using the step function


The unit step function can be used to replace a switch as shown below.




### Step response of an RC circuit

Consider the circuit below in which a switch is thrown at  $t = 0$ . Assume initial voltage across the capacitor for  $t < 0$  is  $V_0$ .

- What is  $v(t)$  ?

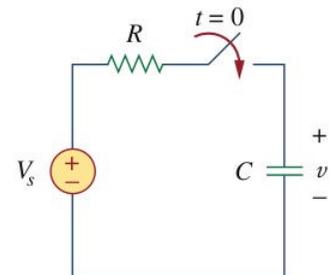

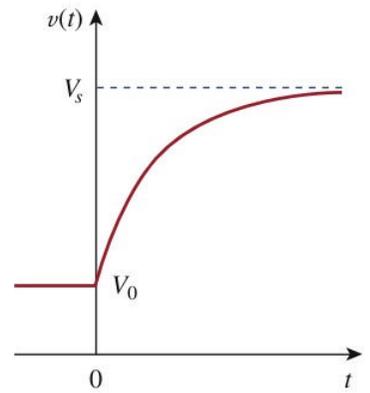

$$v(t) =$$

### Complete response

This is known as the complete response (or total response) of the circuit because it included the natural response and the response caused by the independent source.

$$\text{complete response} = \frac{\text{stored energy}}{\text{response}} + \frac{\text{independent source}}{\text{response}}$$

### Shortcut

Decompose the problem.

$$v =$$

### Evaluating RC circuits



1. Determine initial capacitor voltage  $v(0)$ .
2. Determine final capacitor voltage  $v(\infty) = V_0$ .
3. Find the time constant  $\tau$ .

$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{-t/\tau}$$

### Step response of an RL circuit

Consider the circuit below in which a switch is thrown at  $t = 0$ . Assume initial current through the inductor for  $t < 0$  is  $I_0$ .

- What is  $i(t)$  ?

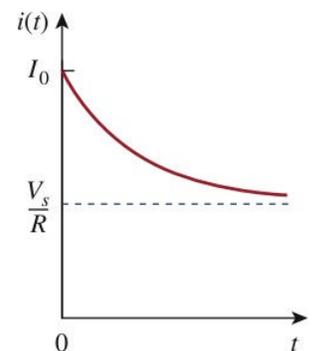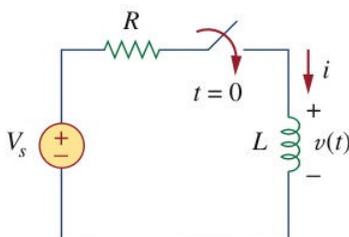


### Evaluating RL circuits

1. Determine initial inductor current  $i(0)$  at  $t=0$ .
2. Determine final inductor current  $i(\infty)$ .
3. Find the time constant  $\tau$ .

$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$$

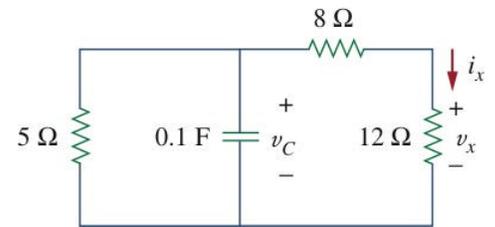
### Example Problem 1

For the circuit below, let  $v_c(0) = 15$  V. Find  $v_C$ ,  $v_x$ , and  $i_x$  for  $t > 0$ .



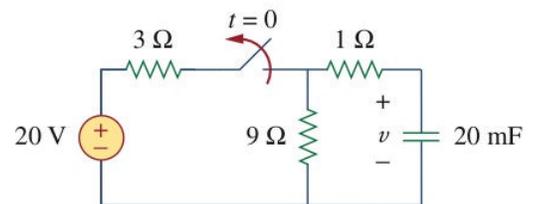
### Example Problem 2

The switch in the circuit below has been closed for a long time and is open at  $t = 0$ . Find  $v(t)$  for  $t \geq 0$ . Calculate the initial energy stored in the capacitor.



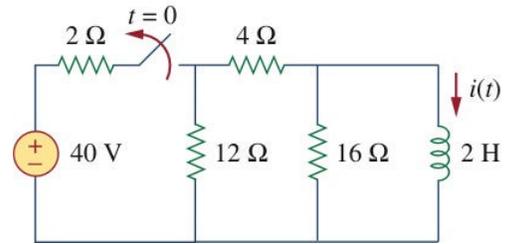
### Example Problem 3

The switch in the circuit below has been closed for a long time and is open at  $t = 0$ . Calculate  $i(t)$  for  $t \geq 0$ .


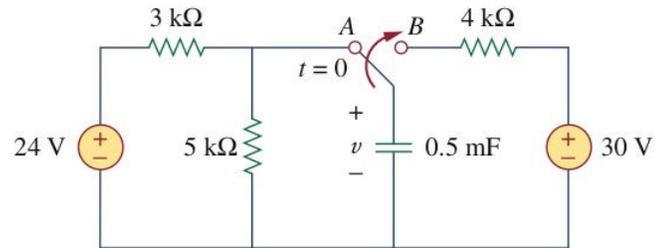
### Example Problem 4

The switch in the circuit below has been in position A for a long time. At  $t = 0$ , the switch moves to B. Determine  $v(t)$  for  $t \geq 0$  and calculate its value at  $t = 2$  and 4 sec.



### Example Problem 5

Find  $i(t)$  for  $t > 0$ . Assume the switch has been closed for a long time.

