

Lesson 19: Phasors and impedance

Complex numbers

A complex number z is a number of the form $z =$

where x, y are real numbers and $j =$

- x is the _____ part of z , $\text{Re}(z) =$
- y is the _____ part of z . $\text{Im}(z) =$

The complex number z can be represented geometrically by plotting it in the complex plane.

- The x axis is the real axis.
- The y axis is the imaginary axis.

The complex number z can be represented three ways:


rectangular form

polar form

exponential form

$$r = \quad \phi =$$

$$x = \quad y =$$

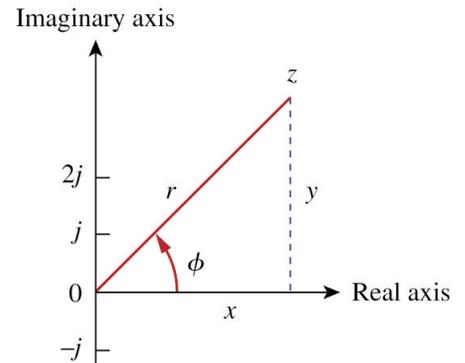

Complex numbers operations

Given two complex numbers z_1, z_2 defined $z_1 = x_1 + jy_1 = r_1 \angle \phi_1$ and $z_2 = x_2 + jy_2 = r_2 \angle \phi_2$

Addition: $z_1 + z_2 =$

Subtraction: $z_1 - z_2 =$

Multiplication: $z_1 \cdot z_2 =$

Division: $z_1 / z_2 =$

Reciprocal: $\frac{z_1}{z_2} =$

Square root: $\sqrt{z} =$

Complex conjugate: $z^* =$

Powers of j

Euler's identity

Euler's identity $e^{\pm j\phi} =$

shows that we may regard $\cos \phi$ and $\sin \phi$ as the real and imaginary parts of $e^{j\phi}$

Representation of sinusoids


Using Euler's identity, we can represent the sinusoid $v(t) =$

Thus, $v(t) = \text{Re}(\mathbf{V}e^{j\omega t})$ where $\mathbf{V} =$

\mathbf{V} is the phasor representation of the sinusoid $v(t)$.

- A phasor is a complex representation of the _____ and _____ of a sinusoid.

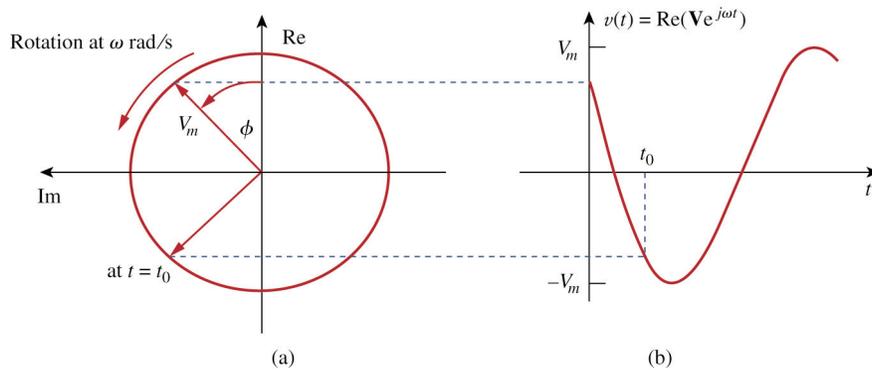Representation of $\mathbf{V}e^{j\omega t}$




Phasors

Phasors are complex quantities and may be expressed in rectangular, polar or exponential form.

Phasors have _____ and _____ and behave as vectors (printed in boldface).

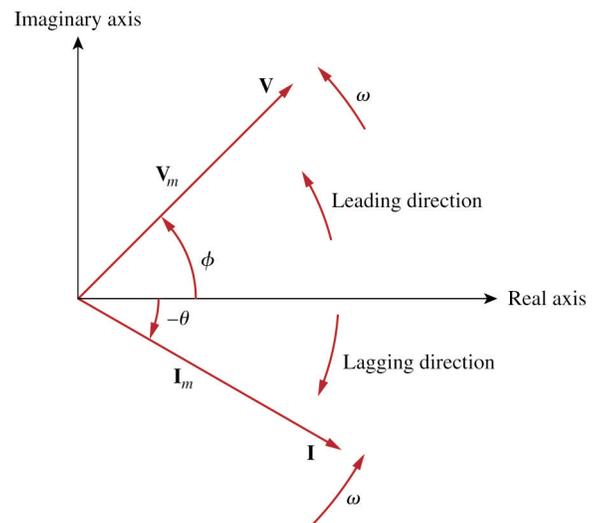Consider $\mathbf{V} = V_m \angle \phi$ and $\mathbf{I} = I_m \angle -\theta$.



Time-phasor points to remember

1. $v(t)$ is the instantaneous or time domain representation, while \mathbf{V} is the frequency or phasor domain representation.
2. $v(t)$ is the time dependent, \mathbf{V} is not.
3. $v(t)$ is always real with no complex term, while \mathbf{V} is generally complex.
4. Phasor analysis only applies when frequency is constant.


Phasor relationship for resistors

We want to develop voltage-current relationships for circuit elements in the phasor domain.

The voltage-current relation in phasor domain is unchanged from the time domain.


$\mathbf{V} =$

Voltage and current are _____.

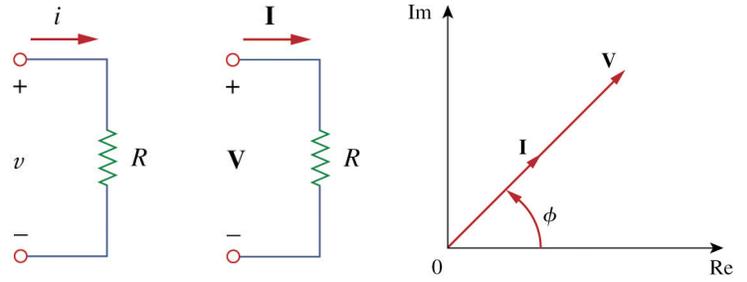

Phasor relationship for inductors

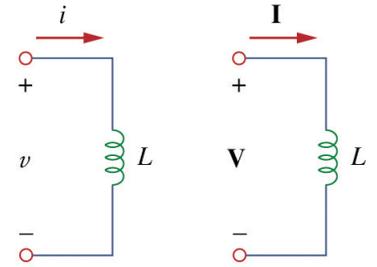Consider an inductor in which $i = I_m \cos(\omega t + \phi)$




The voltage-current relation in phasor domain is $\mathbf{V} =$

Current _____ voltage by 90° .

Phasor relationship for capacitors

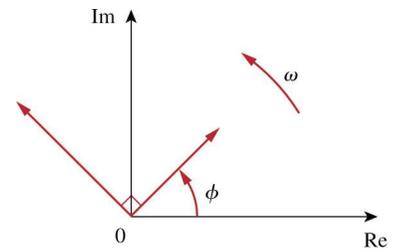
Consider a capacitor in which $v = V_m \cos(\omega t + \phi)$



The voltage-current relation in phasor domain is

$\mathbf{I} = \quad \Rightarrow \quad \mathbf{V} =$

Current _____ voltage by 90° .

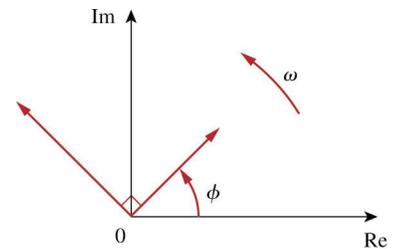

Summary of phasor relations

TABLE 9.2 Summary of voltage-current relationships.

Element	Time domain	Frequency domain
R	$v = Ri$	$\mathbf{V} = R\mathbf{I}$
L	$v = L \frac{di}{dt}$	$\mathbf{V} = j\omega L\mathbf{I}$
C	$i = C \frac{dv}{dt}$	$\mathbf{V} = \frac{\mathbf{I}}{j\omega C}$

Impedance

Previously we obtained the voltage-current relations $V = RI$, $V = j\omega LI$, $V = \frac{1}{j\omega C} I$

These could be written in terms of the ratio of phasor voltage to phasor current as

$$\frac{V}{I} = \quad , \quad \frac{V}{I} = \quad , \quad \frac{V}{I} =$$

From these equations we obtain Ohm's law in phasor form for any element as

$$Z = \quad \text{or} \quad V =$$

where Z is a frequency-dependent quantity known as impedance, measure in _____.

Frequency dependency

The impedance of capacitors and inductors is dependent on frequency.

Consider $\omega = 0$ (dc sources) $Z_L = j\omega L = \quad \Omega$ and $Z_C = \frac{1}{j\omega C} \rightarrow \quad \Omega$

Consider $\omega \rightarrow \infty$ (high frequency) $Z_L = j\omega L \rightarrow \quad \Omega$ and $Z_C = \frac{1}{j\omega C} = \quad \Omega$

Inductors

Capacitors



Impedance (Z)

Impedance is a complex quantity and may be expressed in rectangular form $Z =$ where R is the resistance and X is called _____.

Thus,

- $Z = R + jX$ is said to be _____.
- $Z = R - jX$ is said to be _____.

Impedance may also be expressed in polar form $Z =$

Since $Z = R + jX = |Z| \angle \theta$

Admittance (Y)

Admittance is the reciprocal of impedance $Y =$ which can also be expressed $Y =$

where G is the conductance and B is called the susceptance.

Example Problem 1

Evaluate these complex numbers.

$$(40\angle 50^\circ + 20\angle -30^\circ)^{1/2}$$

$$\frac{(10\angle -30^\circ + (3 - j4))}{(2 + j4)(3 - j5)^*}$$

Example Problem 2

Transform these sinusoids to phasors.

$$i = 6\cos(50t - 40^\circ) \text{ A}$$

$$v = -4\sin(30t + 50^\circ) \text{ V}$$

Example Problem 3

Find the sinusoids represented by these phasors.

$$\mathbf{I} = -3 + j4 \text{ A}$$

$$\mathbf{V} = j8e^{-j20^\circ} \text{ V}$$

Example Problem 4

The voltage $v = 12 \cos(60t + 45^\circ)$ is applied to a 0.1-H inductor. Find the steady-state current through the inductor.

Example Problem 5

Find $v(t)$ and $i(t)$ in the circuit below.

