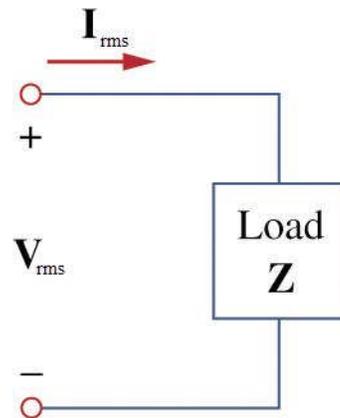


Lesson 23: AC Power

AC power

- Previously we addressed the question of power delivered to a load impedance \mathbf{Z} .




- Given the phasors \mathbf{V}_{rms} and \mathbf{I}_{rms} we found the complex power \mathbf{S} is given

$$\mathbf{S} = \mathbf{V}_{\text{rms}} \mathbf{I}_{\text{rms}}^* = S \angle \theta$$

Complex power (rectangular form)

- As its name implies, \mathbf{S} is complex quantity and its units are volt-amperes (VA).
- Complex power in rectangular form reveals its real (P) and imaginary (Q) components.
 - The real part is the average power (P) in watts.
 - The imaginary part is the reactive power (Q) in VAR.

$$\mathbf{S} = P + jQ$$



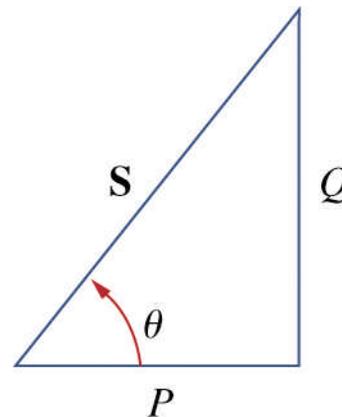


Complex power (polar form)

- Complex power in polar form is comprised of

$$\mathbf{S} = S \angle \theta$$

- Apparent power (S) in volt-amperes. $S = |\mathbf{S}|$
- Power factor angle (θ) which is the same angle as the load impedance \mathbf{Z} .

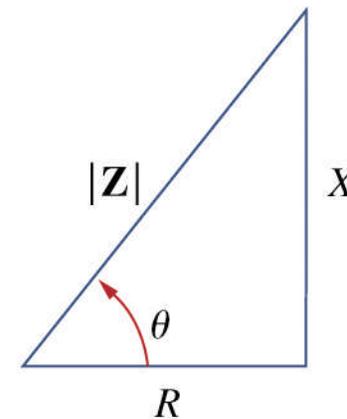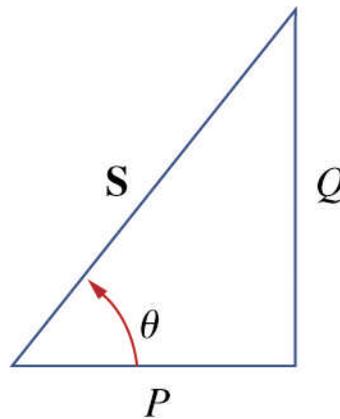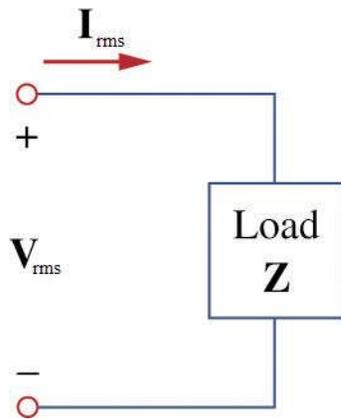

Power factor angle

- If $\theta_v - \theta_i > 0^\circ$ power factor is said to be **lagging** because current lags voltage.
 - Lagging power factor implies an inductive load.
- If $\theta_v - \theta_i < 0^\circ$ power factor is said to be **leading** because current leads voltage.
 - Leading power factor implies a capacitive load.


ICE

Current (**I**) leads voltage(**E**)
in a capacitor (**C**)


ELI

Voltage (**E**) leads current (**I**)
in an inductor (**L**)


Complex power

- Complex power can also be expressed in terms of the load impedance \mathbf{Z} .

$$\mathbf{Z} = \frac{\mathbf{V}_{\text{rms}}}{\mathbf{I}_{\text{rms}}} = \frac{V_{\text{rms}} \angle \theta_v}{I_{\text{rms}} \angle \theta_i}$$

Since $\mathbf{V}_{\text{rms}} = \mathbf{Z}\mathbf{I}_{\text{rms}}$, \mathbf{S} can be expressed
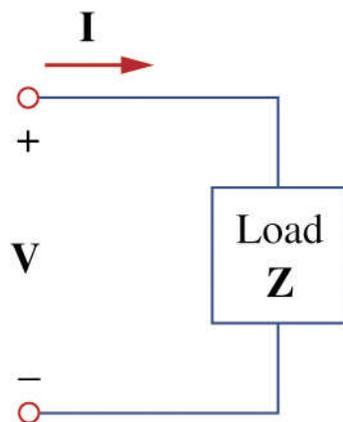
$$\mathbf{S} = \mathbf{V}_{\text{rms}} \mathbf{I}_{\text{rms}}^* = (\mathbf{Z}\mathbf{I}_{\text{rms}}) \mathbf{I}_{\text{rms}}^* = I_{\text{rms}}^2 \mathbf{Z}$$



$$\mathbf{S} = \mathbf{V}_{\text{rms}} \left(\frac{\mathbf{V}_{\text{rms}}}{\mathbf{Z}} \right)^* = \frac{V_{\text{rms}}^2}{\mathbf{Z}^*}$$



Real and reactive power

- Dividing the load impedance \mathbf{Z} into its real and imaginary components


$$\begin{aligned}\mathbf{S} &= I_{\text{rms}}^2 \mathbf{Z} \\ &= I_{\text{rms}}^2 (R + jX) \\ &= I_{\text{rms}}^2 R + jI_{\text{rms}}^2 X \\ &= P + jQ\end{aligned}$$

we observe that P and Q can be expressed

$$P = \text{Re}(\mathbf{S}) = I_{\text{rms}}^2 R, \quad Q = \text{Im}(\mathbf{S}) = I_{\text{rms}}^2 X$$

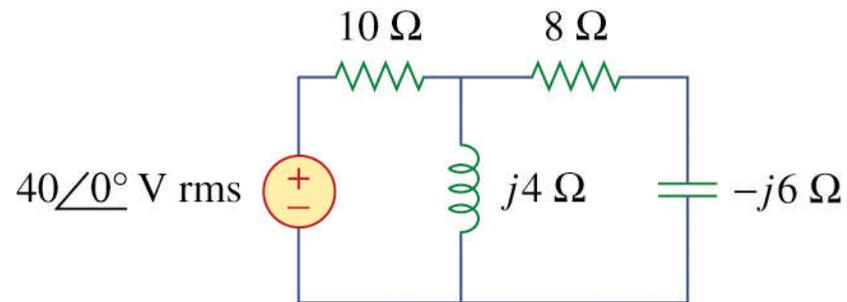
Example Problem 1

Determine the complex power delivered by the source. What is the average power, reactive power and power factor of the load?




Conservation of AC power

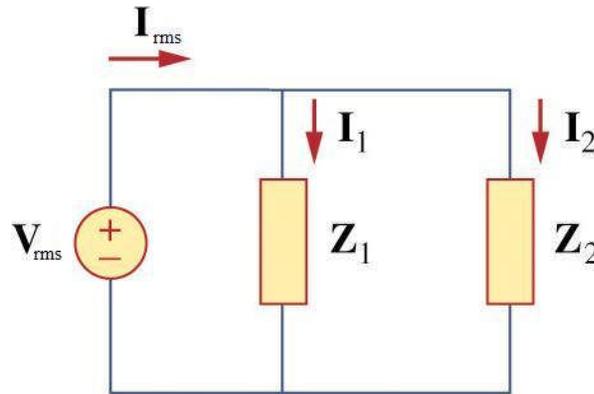- Consider the circuit below (all phasors are in RMS)



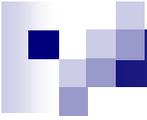- Determine the complex power S supplied by the source and delivered to each load.




Conservation of AC power

- The total complex power \mathbf{S} supplied by the source equals the total complex power delivered to the load.

$$\mathbf{S} = \mathbf{V}_{\text{rms}} \mathbf{I}_{\text{rms}}^* = \mathbf{V}_{\text{rms}} (\mathbf{I}_1^* + \mathbf{I}_2^*) = \mathbf{V}_{\text{rms}} \mathbf{I}_1^* + \mathbf{V}_{\text{rms}} \mathbf{I}_2^* = \mathbf{S}_1 + \mathbf{S}_2$$

- This can be extended to N loads.
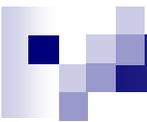
$$\mathbf{S} = \mathbf{S}_1 + \mathbf{S}_2 + \cdots + \mathbf{S}_N$$



Conservation of AC power

- We also notice that this is true of average power (P) and reactive power (Q).

$$\mathbf{S}_{\text{total}} = \mathbf{S}_1 + \mathbf{S}_2 + \cdots + \mathbf{S}_N$$

$$\begin{aligned} P_{\text{total}} + jQ_{\text{total}} &= (P_1 + jQ_1) + (P_2 + jQ_2) + \cdots + (P_N + jQ_N) \\ &= (P_1 + P_2 + \cdots + P_N) + j(Q_1 + Q_2 + \cdots + Q_N) \end{aligned}$$

Thus

$$P_{\text{total}} = P_1 + P_2 + \cdots + P_N$$

$$Q_{\text{total}} = Q_1 + Q_2 + \cdots + Q_N$$

- However, this is **not** true for apparent power (S)

$$S_{\text{total}} \neq S_1 + S_2 + \cdots + S_N$$

Example Problem 2

The figure below depicts a load being fed by a voltage source through a transmission line with impedance $4 + j2 \Omega$. Find the real power and reactive power absorbed by: (a) the source, (b) the line, and (c) the load.

