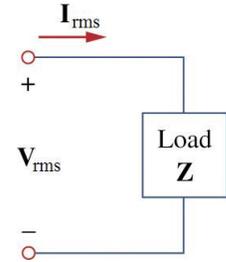


Lesson 27: 3-phase circuit analysis 1

Complex power (review)

Determine the power (P , Q , and S) by load Z .



Single-phase system (2-wire)

A single-phase ac power system consists of a generator connected through a pair of wires (transmission line) to a load.


- V_p is the magnitude of the source voltage given in RMS (the subscript P is for phase, not peak).
- ϕ is the phase.
- This is a _____-wire system.



Single-phase system (3-wire)


A three-wire single-phase system consists of two identical sources (equal _____ and _____) connected to two loads by two outer wires and a neutral.

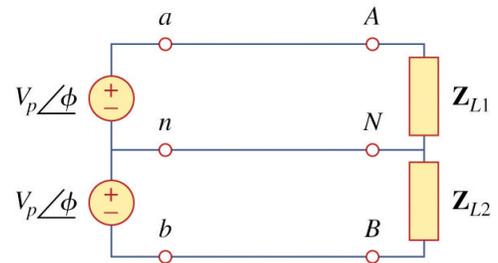This is typical of power supplied to houses.




Three-phase system (4-wire)

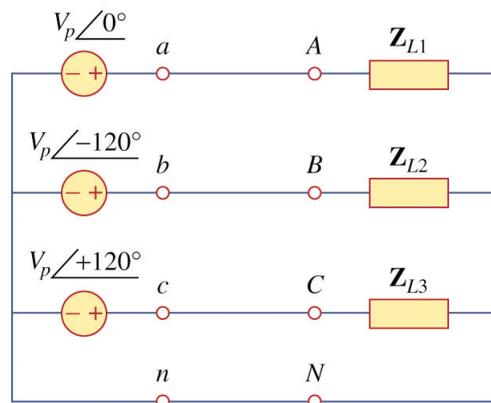A three-phase system is produced by three sources with the same amplitude and frequency but separated in phase by _____.



Why three-phase?

- Nearly all power generated and distributed is 3-phase, ___ Hz (or 50 Hz outside the U.S.).
 - When single phase is needed, it can simply be taken from one of the three phases.
- The instantaneous power in 3-phase system can be _____ (not pulsating).
 - Results in less _____ in 3-phase machines.
- Three phase systems are more economical than single.
 - Amount of _____ needed is less than single phase.


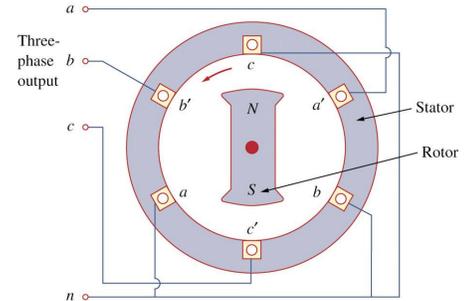


Balanced three-phase voltages

Three-phase voltages are produced by a three-phase ac generator (or alternator).

The stator contains 3 windings ($a-a'$, $b-b'$, $c-c'$) physically separated by _____°.

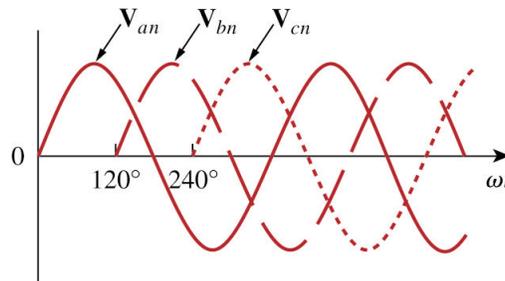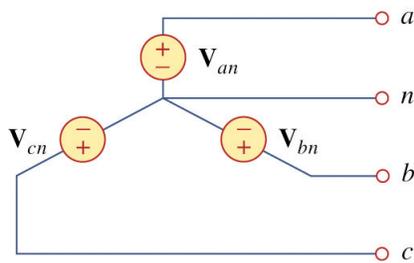The voltages induced in the windings are equal in magnitude but out of phase by 120°. The voltages V_{an} , V_{bn} , and V_{cn} are between lines a , b and c and the neutral line n . These are called _____ voltages.



Balanced three-phase voltages

If the voltages are equal in magnitude but out of phase by 120° they are said to be balanced. This implies


$$\mathbf{V}_{an} + \mathbf{V}_{bn} + \mathbf{V}_{cn} = 0$$

$$|\mathbf{V}_{an}| = |\mathbf{V}_{bn}| = |\mathbf{V}_{cn}|$$

Positive phase sequence (abc)

The _____ sequence or _____ sequence.

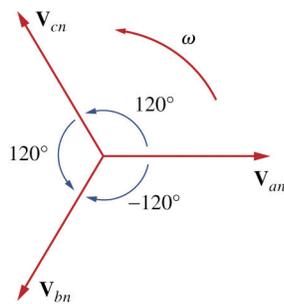
Note: V_P is the rms value of the phase voltage.



$$\mathbf{V}_{an} =$$


$$\mathbf{V}_{bn} =$$

$$\mathbf{V}_{cn} =$$

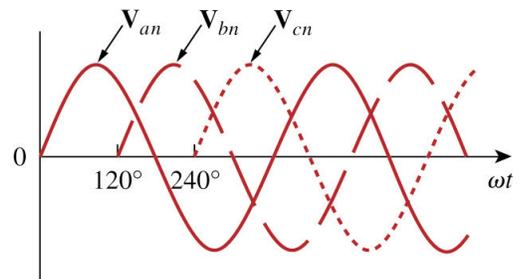


Negative phase sequence (acb)

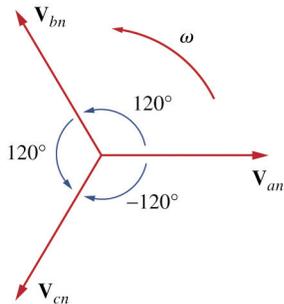The *acb* or negative sequence is produced when the generator rotates counterclockwise.


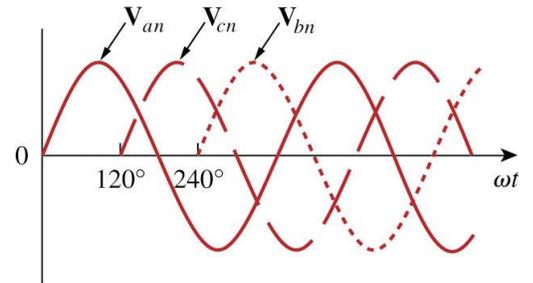
$$\begin{aligned} \mathbf{V}_{an} &= \\ \mathbf{V}_{cn} &= \\ \mathbf{V}_{bn} &= \end{aligned}$$



Phase sequence



The phase sequence is the time order in which the voltages pass through their respective maximum values.

Phase sequence is important because it determines the _____ of a connected motor.

Three-phase loads

Three-phase loads can be either _____-connected or _____-connected.

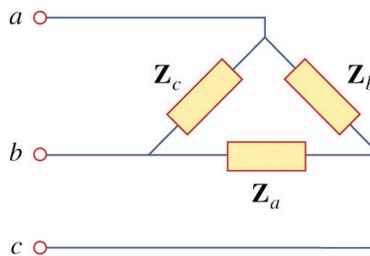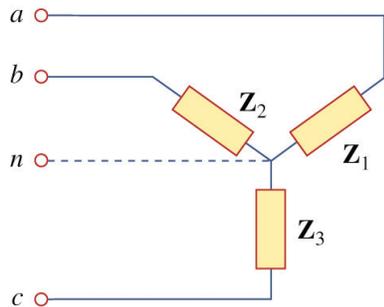Loads are said to be balanced if phase impedances ($\mathbf{Z}_1, \mathbf{Z}_2, \mathbf{Z}_3$ or $\mathbf{Z}_a, \mathbf{Z}_b, \mathbf{Z}_c$) are equal in magnitude and phase.



Wye-connected load

Whether a _____ line exists depends on if it is a three or four-wire system.

For a balanced wye-connected load

$$\mathbf{Z}_1 = \mathbf{Z}_2 = \mathbf{Z}_3 =$$



where \mathbf{Z}_Y is the load per phase.

Delta-connected load

A neutral line cannot exist in a Δ -connected load.

For a balanced Δ -connected load (where \mathbf{Z}_Δ is the load per phase.)
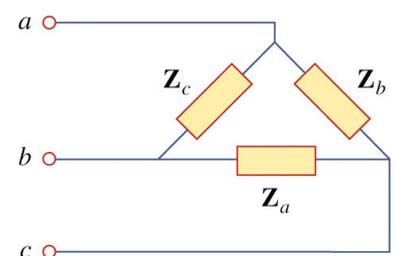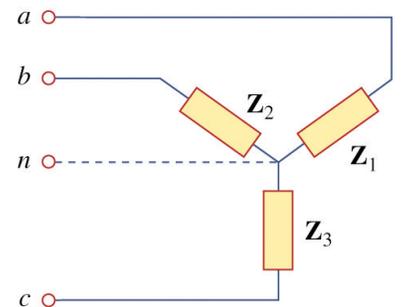
$$\mathbf{Z}_a = \mathbf{Z}_b = \mathbf{Z}_c =$$



Delta-wye transformation


How can we equate the wye- and delta-connected (balanced) loads?

For balanced loads, $Z_{\Delta} =$ _____ or $Z_Y =$ _____

Delta-connected sources

Sources may also be delta-connected.

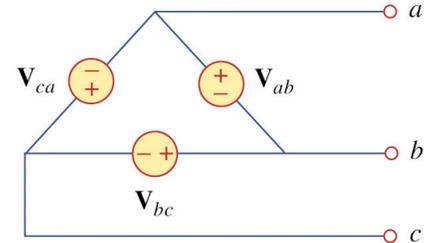In practice, this is rarely done because slight imbalances in the voltages result in a circulating current in the delta-mesh



Three-phase systems

Given that both loads and sources can be Y-connected and Δ -connected, we have 4 possible combinations to consider

- Y-Y connection
- Y- Δ connection
- Δ - Δ connection
- Δ -Y connection


In reality, the most common configuration is _____ .

Balanced Y-Y connection

We will consider a four-wire Y-Y system.

$Z_Y =$ _____

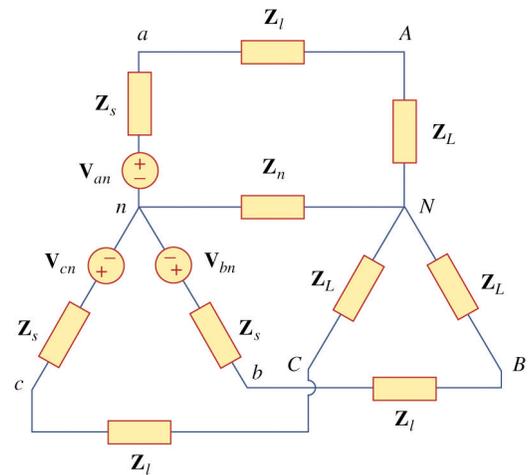The impedance Z_Y can be thought of as the sum of the _____, _____ and _____ impedances.




Balanced Y-Y connection

Because Z_S and Z_l are often quite small compared to Z_L , we will assume $Z_Y = Z_L$, simplifying our Y-Y system.

Source-load labeling convention


_____ are labeled using lowercase letters.

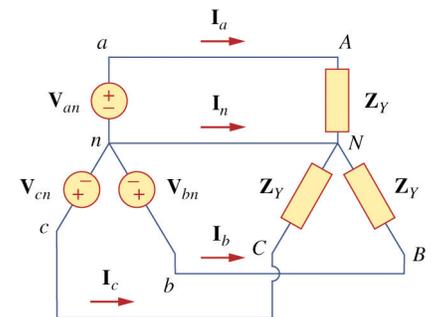_____ are labeled using uppercase letters.



Line voltages

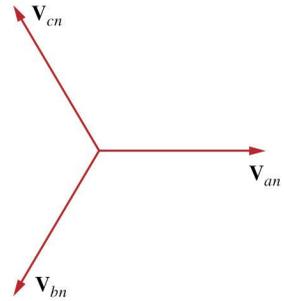How are the line voltages (\mathbf{V}_{ab} , \mathbf{V}_{bc} , \mathbf{V}_{ca}) related to the phase voltages (\mathbf{V}_{an} , \mathbf{V}_{bn} , \mathbf{V}_{cn}) ?



$$\mathbf{V}_{ab} = \mathbf{V}_{an} - \mathbf{V}_{bn} =$$

$$\mathbf{V}_{bc} = \sqrt{3}V_p \angle$$


$$\mathbf{V}_{ca} = \sqrt{3}V_p \angle$$

Line voltage are _____ times larger and lead their respective phase voltages by _____.

Line currents

What are the line currents (\mathbf{I}_a , \mathbf{I}_b , \mathbf{I}_c)?

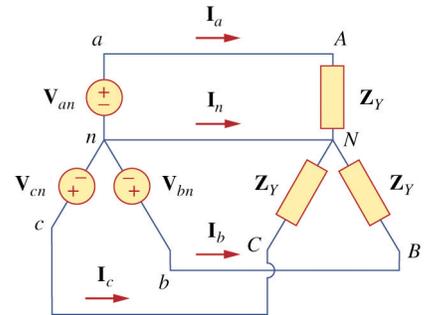What is the neutral line current (\mathbf{I}_n)?



Line currents are given

$$\mathbf{I}_a =$$


$$\mathbf{I}_b = \frac{\mathbf{V}_{bn}}{\mathbf{Z}_Y} = \frac{\mathbf{V}_{an} \angle -120^\circ}{\mathbf{Z}_Y} =$$

$$\mathbf{I}_c = \frac{\mathbf{V}_{cn}}{\mathbf{Z}_Y} = \frac{\mathbf{V}_{an} \angle -240^\circ}{\mathbf{Z}_Y} =$$

Since $\mathbf{I}_a + \mathbf{I}_b + \mathbf{I}_c = 0$, it follows that $\mathbf{I}_n =$ _____ .

Single-phase equivalent

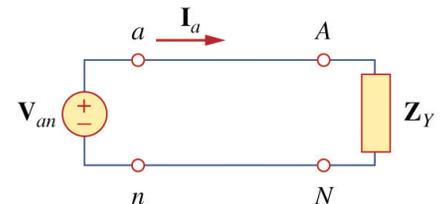In analyzing a balanced Y-Y system, it is sufficient to examine just one of the phases and apply the results to the other two phases (with appropriate phase delays).



Example Problem 1

Determine the phase sequence of the set of voltages.

$$v_{an} = 200 \cos(\omega t + 10^\circ)$$

$$v_{bn} = 200 \cos(\omega t - 230^\circ)$$

$$v_{cn} = 200 \cos(\omega t - 110^\circ)$$

Example Problem 2

Calculate the line currents in the three-wire Y-Y system.

