
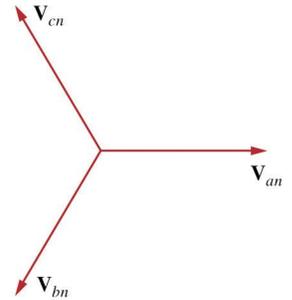


Lesson 28: 3-Phase Circuit Analysis 2

Line voltages (Y-Y)
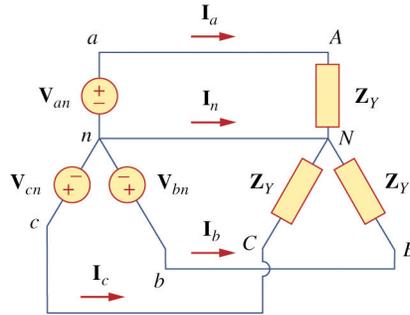
$$\begin{aligned} \mathbf{V}_{ab} &= \mathbf{V}_{an} - \mathbf{V}_{bn} = \\ \mathbf{V}_{bc} &= \sqrt{3}V_p \angle -90^\circ \\ \mathbf{V}_{ca} &= \sqrt{3}V_p \angle -210^\circ \end{aligned}$$



Line voltage are _____ times larger and lead their respective phase voltages by _____.


Line currents (Y-Y)

$$\mathbf{I}_a = \quad \mathbf{I}_b = \mathbf{I}_a \angle -120^\circ \quad \mathbf{I}_c = \mathbf{I}_a \angle -240^\circ$$

Since $\mathbf{I}_a + \mathbf{I}_b + \mathbf{I}_c = 0$, it follows that $\mathbf{I}_n = \underline{\hspace{2cm}}$.

Single-phase equivalent (Y-Y)

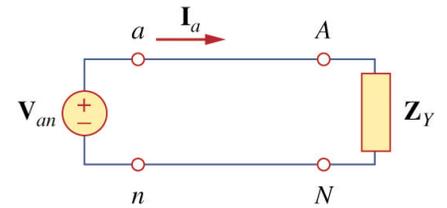In analyzing a balanced Y-Y system, it is sufficient to examine just one of the phases and apply the results to the other two phases (with appropriate phase delays).



Balanced Y-Δ connection


A balanced Y-Δ system consists of a Y-connected source feeding a Δ-connected load.

- There is no _____ connection.

Line voltages (Y-Δ)

For the Y-Δ system, the line voltages are still given
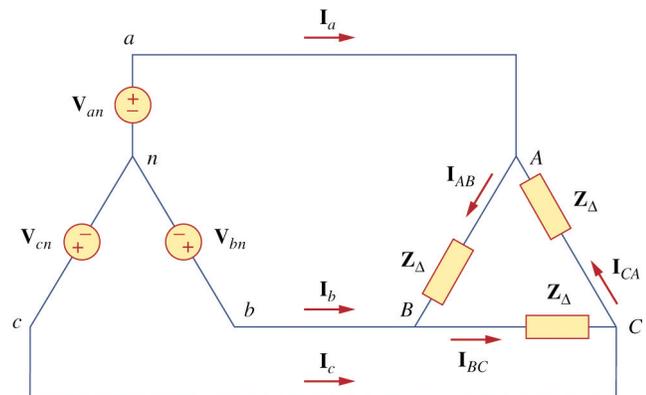
$$\begin{aligned} \mathbf{V}_{ab} &= \quad \quad \quad = \sqrt{3}V_p \angle 30^\circ = \mathbf{V}_{AB} \\ \mathbf{V}_{bc} &= \sqrt{3}V_p \angle -90^\circ = \mathbf{V}_{BC} \\ \mathbf{V}_{ca} &= \sqrt{3}V_p \angle -210^\circ = \mathbf{V}_{CA} \end{aligned}$$



Line currents (Y-Δ)

The currents through each phase of the Δ-load (\mathbf{I}_{AB} , \mathbf{I}_{BC} , \mathbf{I}_{CA}) are _____ the same as the line currents (\mathbf{I}_a , \mathbf{I}_b , \mathbf{I}_c).

$$\mathbf{I}_{AB} = \underline{\hspace{2cm}} \quad \mathbf{I}_{BC} = \frac{\mathbf{V}_{BC}}{\mathbf{Z}_\Delta} \quad \mathbf{I}_{CA} = \frac{\mathbf{V}_{CA}}{\mathbf{Z}_\Delta}$$

How do we obtain the line currents (\mathbf{I}_a , \mathbf{I}_b , \mathbf{I}_c). in terms of the phase currents (\mathbf{I}_{AB} , \mathbf{I}_{BC} , \mathbf{I}_{CA}) ?

We write a _____ expressions at A, B and C.


$$\mathbf{I}_a =$$

Line currents are _____ times larger and _____ their respective phase currents by 30° .

$$\mathbf{I}_a = \sqrt{3}\mathbf{I}_{AB} \angle -30^\circ$$

$$\mathbf{I}_b = \sqrt{3}\mathbf{I}_{AB} \angle -150^\circ$$
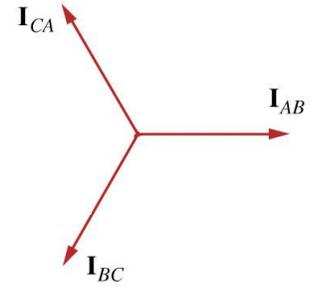
$$\mathbf{I}_c = \sqrt{3}\mathbf{I}_{AB} \angle -270^\circ$$




Single-phase equivalent

In analyzing a balanced Y- Δ , we can transform the load to form an equivalent Y-Y system.

$$\mathbf{Z}_Y =$$

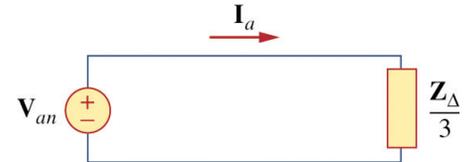Then a single phase can be examined to determine the phase current.



Balanced Δ - Δ connection

In a balanced Δ - Δ system, both source and load are Δ -connected.


Line voltages (Δ - Δ)

For the Δ - Δ system, the line voltages and phase voltages are the same.

$$\mathbf{V}_{ab} = V_p \angle 0^\circ = \mathbf{V}_{AB}$$

$$\mathbf{V}_{bc} = V_p \angle -120^\circ = \mathbf{V}_{BC}$$
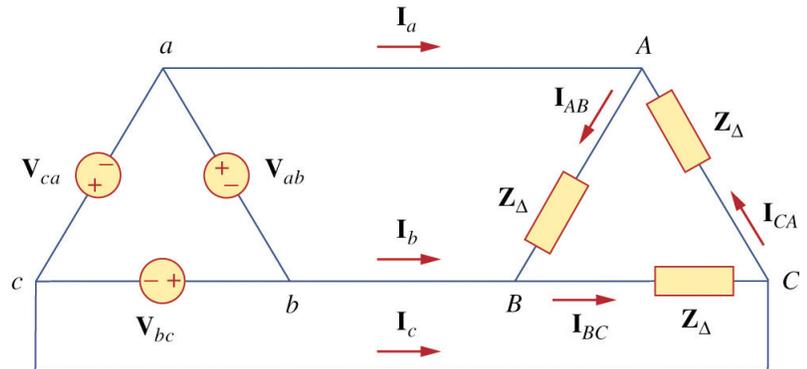
$$\mathbf{V}_{ca} = V_p \angle +120^\circ = \mathbf{V}_{CA}$$



Line currents (Δ - Δ)

The line currents for the Δ -connected load are identical to the previous Y- Δ system.

$$\mathbf{I}_a = \mathbf{I}_{AB} - \mathbf{I}_{CA} = \frac{\mathbf{V}_{ab}}{\mathbf{Z}_\Delta} - \frac{\mathbf{V}_{ca}}{\mathbf{Z}_\Delta} = \frac{\mathbf{V}_{ab}}{\mathbf{Z}_\Delta} - \frac{\mathbf{V}_{ab} \angle -240^\circ}{\mathbf{Z}_\Delta} = \frac{\mathbf{V}_{ab}}{\mathbf{Z}_\Delta} (1 - 1 \angle -240^\circ) =$$

Balanced Δ -Y connection

A balanced Δ -Y system consists of a Δ -connected source feeding a Y-connected load.

Line voltages (Δ -Y)

The line voltages and source phase voltages are the same.


$$\mathbf{V}_{ab} = V_p \angle 0^\circ$$

$$\mathbf{V}_{bc} = V_p \angle -120^\circ$$

$$\mathbf{V}_{ca} = V_p \angle -240^\circ$$

At the load, the per phase voltage relations are
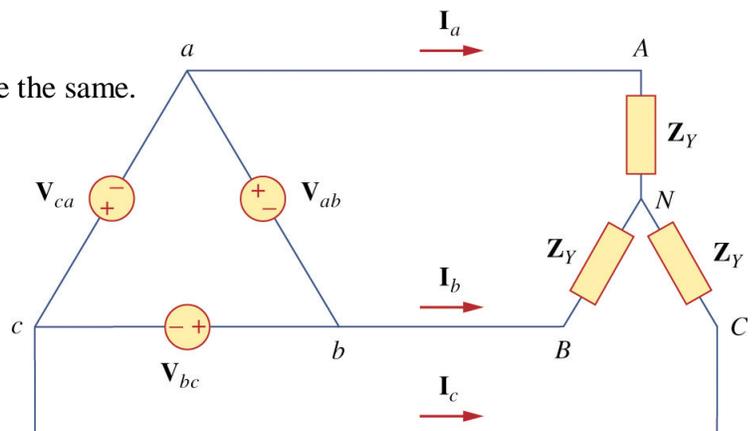
$$\mathbf{V}_{ab} = \sqrt{3}\mathbf{V}_{AN} \angle 30^\circ \Rightarrow \mathbf{V}_{AN} =$$



Line currents (Δ -Y)

The phase currents for the Y-connected load are identical to the line currents.

$$I_{AN} = I_a \quad I_{BN} = I_b \quad I_{CN} = I_c$$

We can express these in terms of the source voltages.

$$I_a = I_{AN} = \frac{V_{AN}}{Z_Y} = \frac{V_p \angle 0^\circ}{Z_Y}$$

Summary of balanced 3-phase systems

TABLE 12.1 Summary of phase and line voltages/currents for balanced three-phase systems.¹

Summary of phase and line voltages/currents for balanced three-phase systems.¹


Connection	Phase voltages/currents	Line voltages/currents
Y-Y	$V_{an} = V_p \angle 0^\circ$ $V_{bn} = V_p \angle -120^\circ$ $V_{cn} = V_p \angle +120^\circ$ Same as line currents	$V_{ab} = \sqrt{3}V_p \angle 30^\circ$ $V_{bc} = V_{ab} \angle -120^\circ$ $V_{ca} = V_{ab} \angle +120^\circ$ $I_a = V_{an}/Z_Y$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$
Y- Δ	$V_{an} = V_p \angle 0^\circ$ $V_{bn} = V_p \angle -120^\circ$ $V_{cn} = V_p \angle +120^\circ$ $I_{AB} = V_{AB}/Z_\Delta$ $I_{BC} = V_{BC}/Z_\Delta$ $I_{CA} = V_{CA}/Z_\Delta$	$V_{ab} = V_{AB} = \sqrt{3}V_p \angle 30^\circ$ $V_{bc} = V_{BC} = V_{ab} \angle -120^\circ$ $V_{ca} = V_{CA} = V_{ab} \angle +120^\circ$ $I_a = I_{AB} \sqrt{3} \angle -30^\circ$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$
Δ - Δ	$V_{ab} = V_p \angle 0^\circ$ $V_{bc} = V_p \angle -120^\circ$ $V_{ca} = V_p \angle +120^\circ$ $I_{AB} = V_{ab}/Z_\Delta$ $I_{BC} = V_{bc}/Z_\Delta$ $I_{CA} = V_{ca}/Z_\Delta$	Same as phase voltages $I_a = I_{AB} \sqrt{3} \angle -30^\circ$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$
Δ -Y	$V_{ab} = V_p \angle 0^\circ$ $V_{bc} = V_p \angle -120^\circ$ $V_{ca} = V_p \angle +120^\circ$ Same as line currents	Same as phase voltages $I_a = \frac{V_p \angle -30^\circ}{\sqrt{3}Z_Y}$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$

Beware!

Consider the following

When _____ impedances ($1 + j2 \Omega$) are present, we must be more judicious in the application of our formulas.
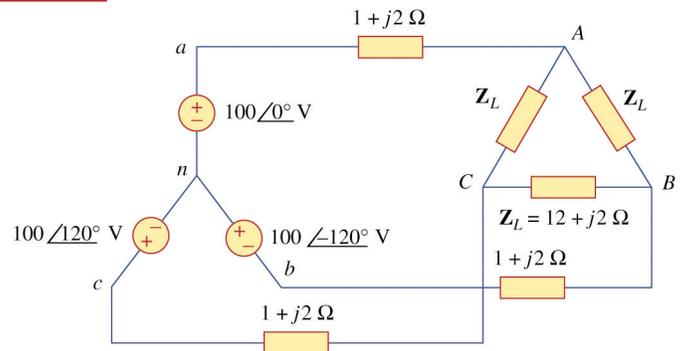
$$I_{AB} \neq \frac{V_{ab}}{Z_L} \quad V_{AB} \neq \sqrt{3}V_{an} \angle 30^\circ$$



Example Problem 1

A balanced abc -sequence Y-connected source with $\mathbf{V}_{an} = 1000\angle 10^\circ \text{ V}$ is connected to a Δ -connected balanced load $(8 + j4) \Omega$ per phase. Calculate the phase and line currents.

Example Problem 2

A balanced Δ -connected load having an impedance $20 + j15 \Omega$ is connected to a Δ -connected, positive-sequence generator having $V_{ab} = 330\angle 0^\circ \text{ V}$. Calculate the phase currents of the load and the line currents.

Example Problem 3

A balanced Y-connected load with a phase impedance of $40+j25 \Omega$ is supplied by a balanced, positive-sequence Δ -connected source with a line voltage of 210 V. Calculate the phase currents. Use V_{ab} as a reference.