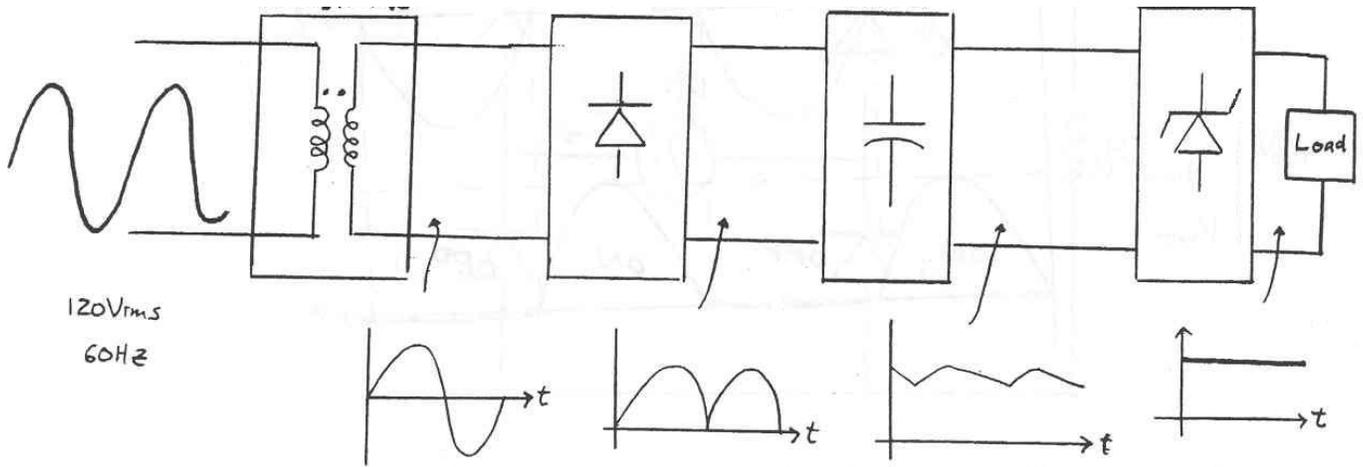


Lesson 33: Rectifiers and Filtering



Overview

Our ultimate goal is to construct a dc power supply depicted by the block diagram below.



Half-wave rectifier review

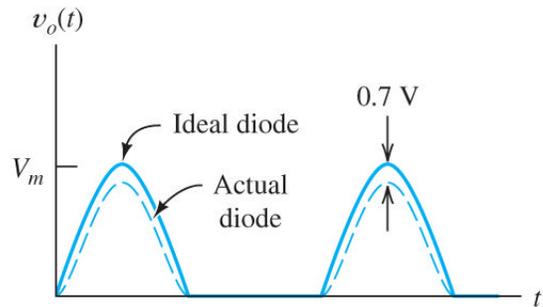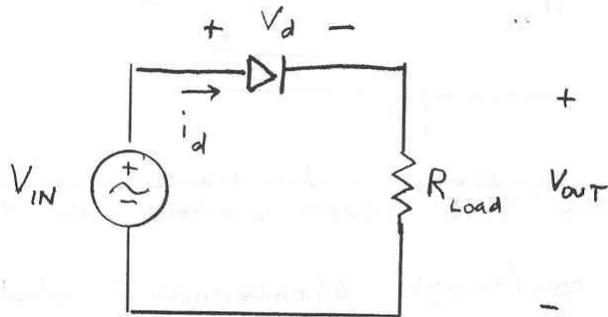Previously we examined the half-wave rectifier.



average output voltage $V_{out,ave} =$

rms output voltage $V_{out,rms} =$


Non-ideal effects

We also coupled it with a transformer to create a more realistic model which included diode voltage drop and transformer resistance.

$$V_{sec,pk} = (V_{sec,pk,NL} - 0.7) \frac{R_{Load}}{R_{Load} + R_{Tran}}$$

$$V_{out,ave} = \frac{V_{sec,pk}}{\pi}$$


$$V_{out,rms} = \frac{V_{sec,pk}}{2}$$

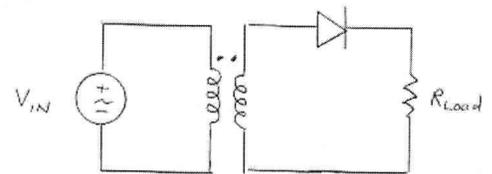


Full-wave rectifier

Let us consider the following rectifier circuit.

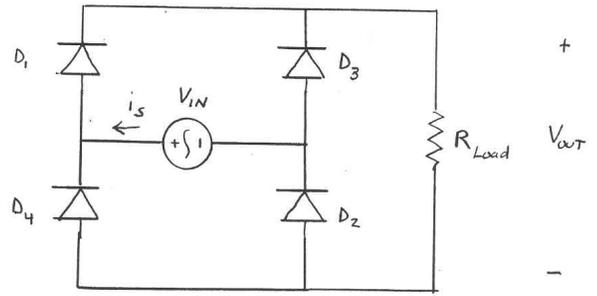
- Use the assumed diode states method of analysis.



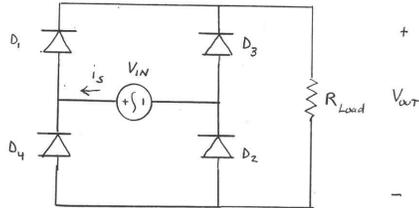There are two possible paths for the source current i_s .




when i_s is positive

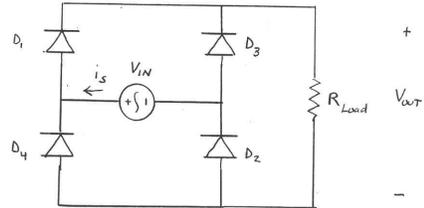

when i_s is negative

Step 1

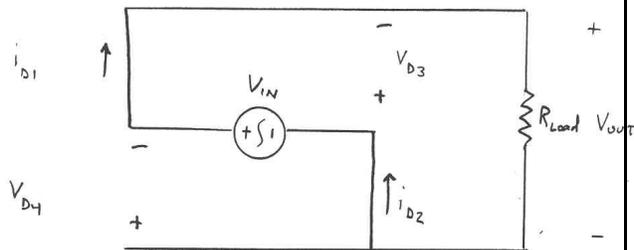Assume D_1 and D_2 are “on,” D_3 and D_4 are “off.”




- Consider i_{D1} , i_{D2} and v_{D4} , v_{D3} when $v_{in} = v_{pk} \sin \omega t$.
- When are our assumptions true?

Our assumptions are true when v_{in} _____.



Step 2

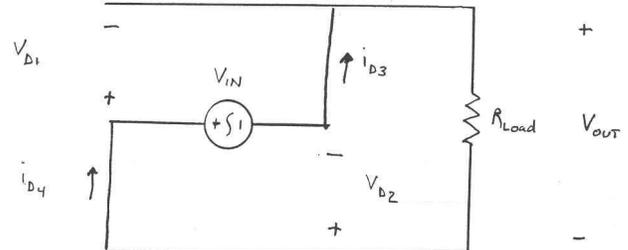Assume D_3 and D_4 are “on,” D_1 and D_2 are “off.”




- Consider i_{D3} , i_{D4} and v_{D1} , v_{D2} when $v_{in} = v_{pk} \sin \omega t$.
- When are our assumptions true?

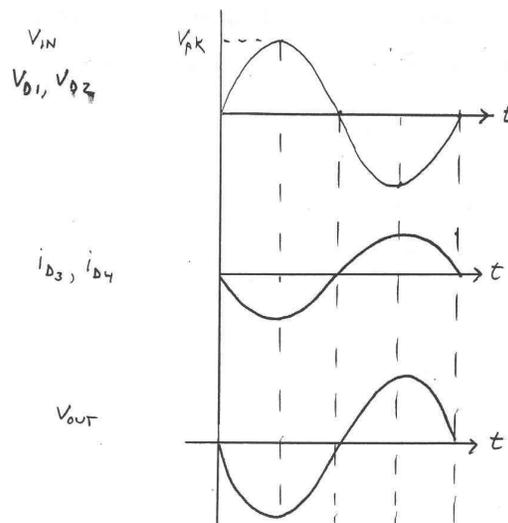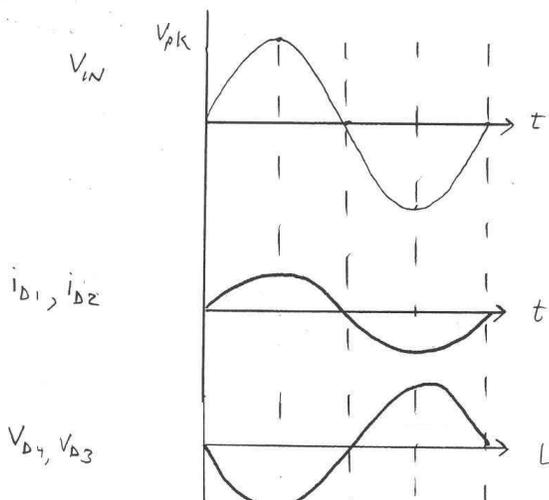Our assumptions are true when v_{in} _____.



Step 3

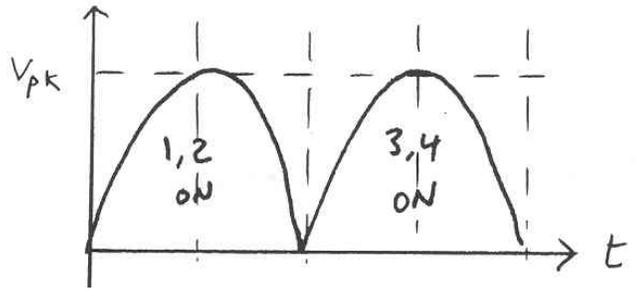Combining these results, we determine that v_{out} is given



What are $v_{out,ave}$ and $v_{out,rms}$?

Full-wave rectified sinusoid

The average and rms values for a full-wave rectified sinusoid are given

$$v_{out,ave} = \frac{1}{\pi} \int_0^{\pi} v_{pk} \sin \theta d\theta = \frac{v_{pk}}{\pi} (-\cos \theta) \Big|_0^{\pi} =$$

$$v_{out,rms} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} (v_{pk} \sin \theta)^2 d\theta} =$$


The average power delivered to the load is given $p_{load,ave} = \frac{v_{out,rms}^2}{R_{load}} =$

Non-ideal effects

As we did previously, our model should include

- Voltage drops of the conducting both diodes (now totaling ~1.4 V)
- Output resistance of transformer coil.

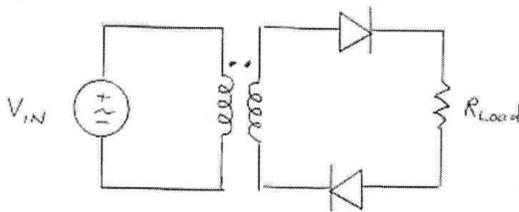These two factors reduce the peak secondary voltage ($v_{sec,pk}$) from that of the ideal case.




$$v_{pk} = (v_{sec,pk,NL} - 1.4) \frac{R_{load}}{R_{load} + R_{tran}}$$

Filtering


The goal of our power supply is to convert an ac signal into _____ dc.

An unfiltered, rectified signal would not be tolerated by most devices expecting a dc voltage.

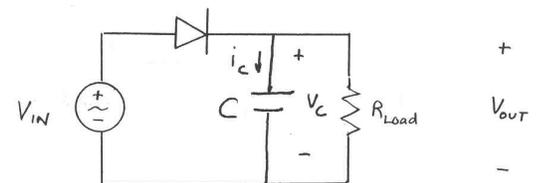
Let us consider a half-wave rectifier combined with a capacitor across the load.



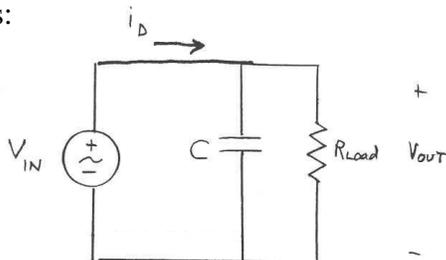
Assuming an "ideal" diode, the circuit has two possible states:



diode "on," capacitor _____

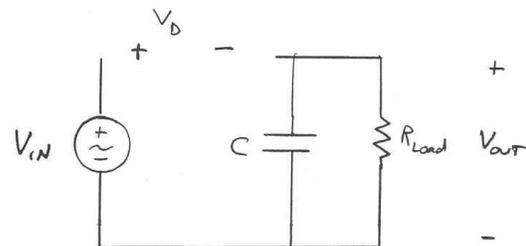

diode "off," capacitor _____

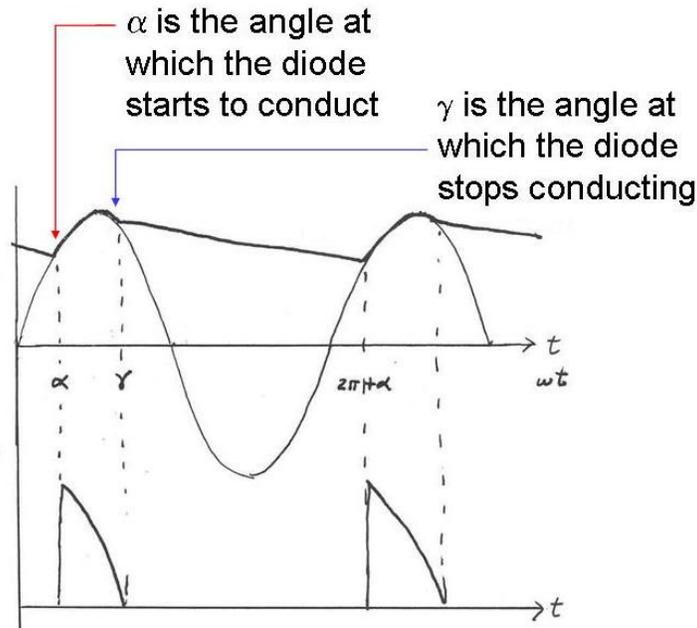


Step 1: diode "on"

Analyze the circuit when the diode is assumed "on" and determine when $i_d > 0$.

With diode "on" all three components are in parallel, so

$$v_{in} = v_{pk} \sin \omega t = v_{pk} \sin \theta$$


Determine an expression for i_d

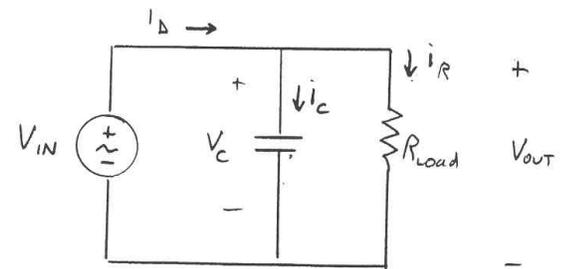

Analyze the circuit when the diode is assumed "on" and determine when $i_d > 0$.

time domain		phasor domain
$i_R = \frac{v_{in}}{R_{load}} = \frac{v_{pk}}{R_{load}} \sin \omega t$	\Rightarrow	$\tilde{I}_R = \frac{v_{pk}}{R_{load}} \angle 0^\circ$

$i_c = C \frac{dv_c}{dt} = v_{pk} C \omega \cos \omega t$	\Rightarrow	$\tilde{I}_c = v_{pk} C \omega \angle -90^\circ$
---	---------------	--

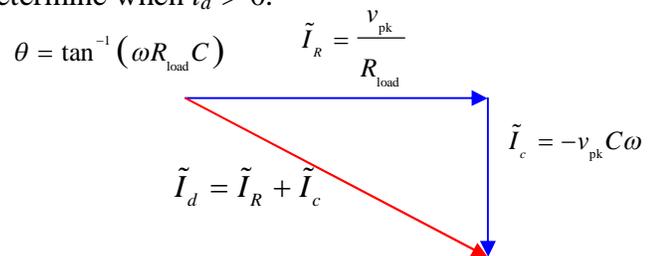

The time domain expression for i_d is given

$$i_d = v_{pk} \sqrt{\left(\frac{1}{R_{load}}\right)^2 + (C\omega)^2} \sin\left[\omega t + \tan^{-1}(\omega R_{load} C)\right]$$


$$|\tilde{I}_d| = \sqrt{\left(\frac{v_{pk}}{R_{load}}\right)^2 + (v_{pk} C \omega)^2}$$

The diode conducts until this current goes to zero $i_d = 0 \rightarrow \omega t + \tan^{-1}(\omega R_{load} C) = 0, \pi, 2\pi \dots$

We defined this angle $\omega t = \gamma$, thus $\gamma =$

Step 2: diode "off"

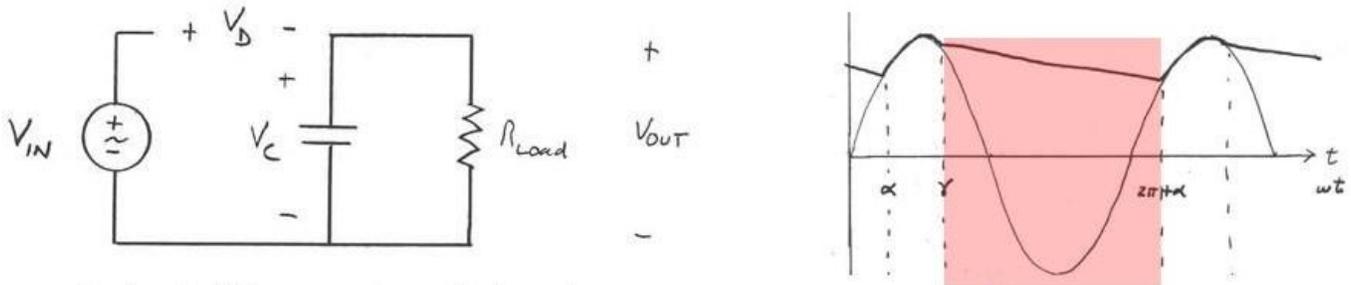Analyze the circuit when the diode is assumed "off" and determine when $v_d < 0$.



Determine an expression for v_c

- We need the initial voltage at $\omega t = \gamma$ when the diode turns off.

The initial voltage v_i is $v_i =$ and the capacitor voltage v_c is given $v_c = v_i e^{-\left(\frac{t-t_i}{RC}\right)} = v_i e^{-\left(\frac{\theta-\gamma}{RC}\right)}$

The diode voltage v_d is $v_d =$


The diode does not conduct until $v_d = 0$ when $\theta = 2\pi + \gamma$

$$v_d = v_{pk} \sin(2\pi + \alpha) - v_{pk} \sin(\gamma) e^{-\left(\frac{2\pi + \alpha - \gamma}{\omega R_{load} C}\right)} = 0$$

This equation can be solved numerically (calculator) for α

Step 3

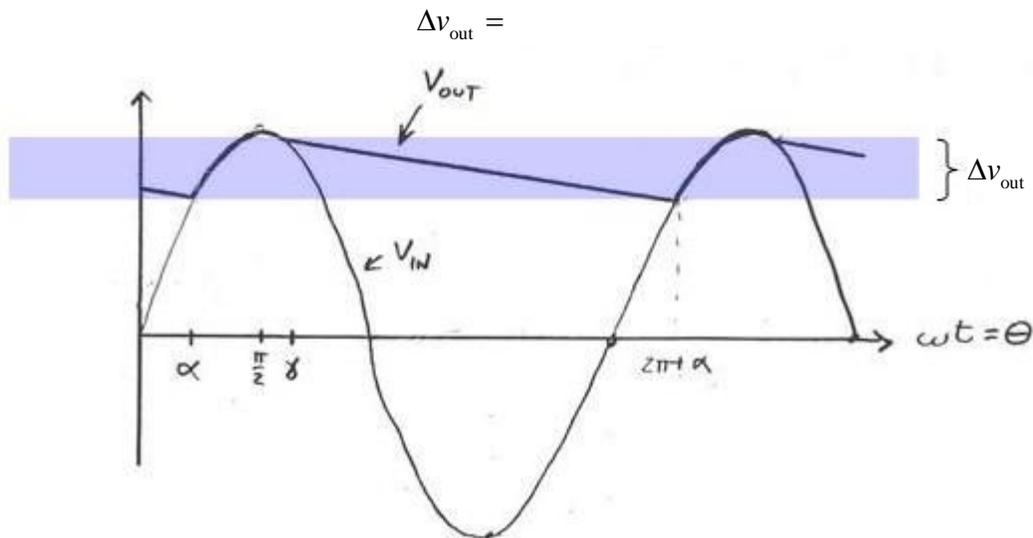Once γ and α are known, the magnitude of the capacitor voltage ripple can be determined




The average value is close to $\Delta v_{out,ave} = v_{pk} - \frac{v_{out}}{2}$

$$= \frac{1}{2} (v_{pk} + v_{pk} \sin \alpha)$$

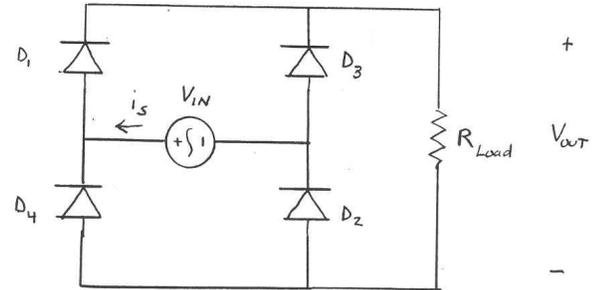Example Problem 1

We would like to deliver 2 W to a $20\text{-}\Omega$ load through a transformer with a $2\text{-}\Omega$ output resistance. Determine the no-load RMS value of the transformer secondary assuming a full-wave rectifier is used.



Example Problem 2

If $R_{load} = 500\ \Omega$, $C = 100\ \mu\text{F}$, $\omega = 377\ \text{rad/sec}$ and $v_{pk} = 15\ \text{V}$, determine the ripple and average voltage.