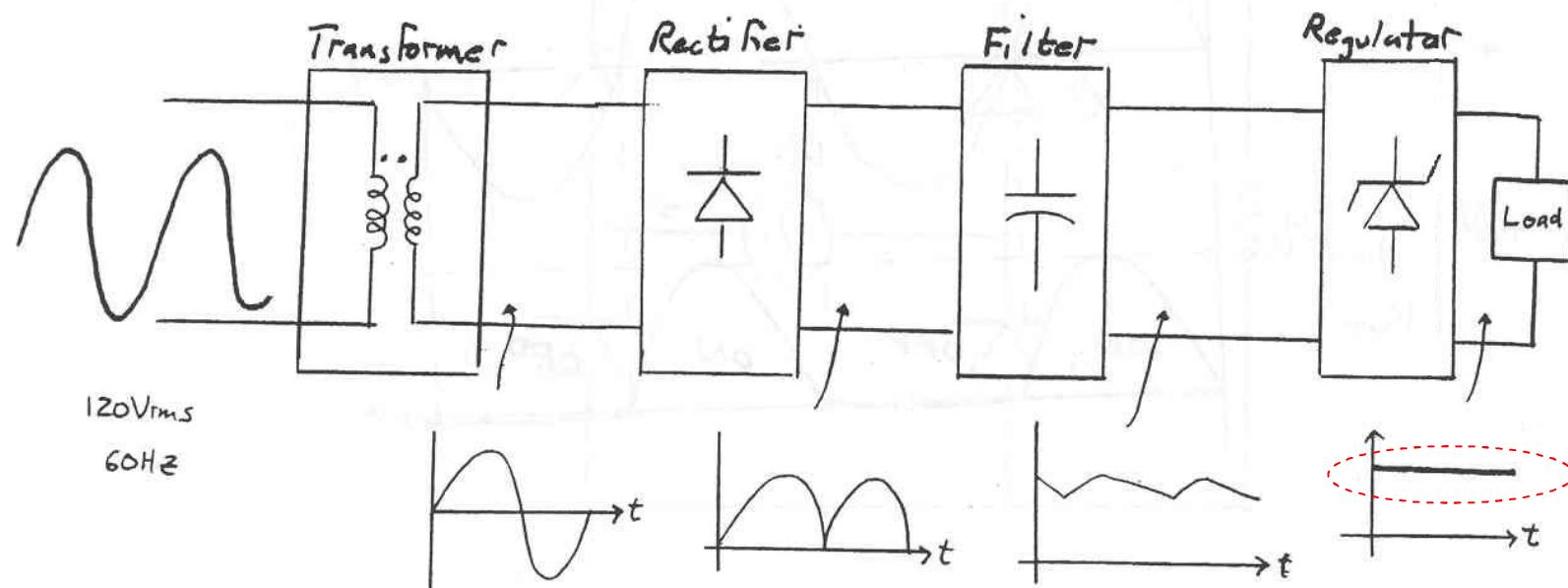


# Lesson 36: Power supply design

# Overview


- Now that we have analyzed all the elements, we are ready to design a simple power supply.



power supply block diagram
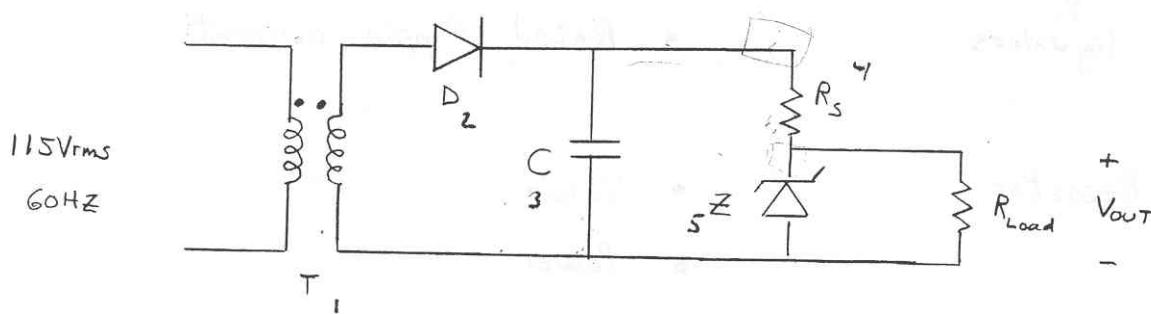
# Topology

- The power supply consists of 5 components.




power supply components

- Desired output

- $V_{out,min} < V_{out} < V_{out,max}$  for  $R_{load,min} < R_{load} < R_{load,max}$
- For our example, the goal is to create a 6.1 V reference voltage with a load in the range  $250 \Omega < R_{load} < \infty$
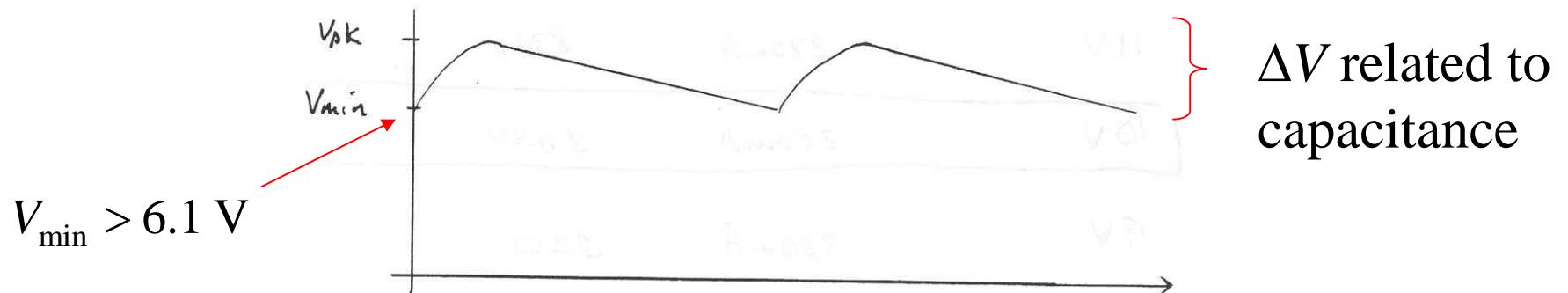
# Step 1: Choose a transformer

- Recall the output of a filtered half wave rectifier



$$V_{min} > 6.1 \text{ V}$$

where

$$v_{pk} \approx (v_{sec,pk,NL} - 0.7) \frac{R_{load}}{R_{load} + R_{tran}}$$

approximated as 0.96

transformer secondary voltages  
are specified in RMS

# Step 1: Choose a transformer


- Transformer choices from Digikey

Rated voltage (sec,rms)	Rated current (sec)	Cost	$V_{pk}$
12 V	250 mA	\$3.60	15.62
11 V	270 mA	\$3.60	14.26
10 V	250 mA	\$11.44	12.90
9 V	330 mA	\$3.60	11.55
8 V	300 mA	\$10.27	10.19
7 V	230 mA	2.98	8.83

$$v_{pk} = (\sqrt{2} \times v_{sec,rms} - 0.7)(0.96)$$

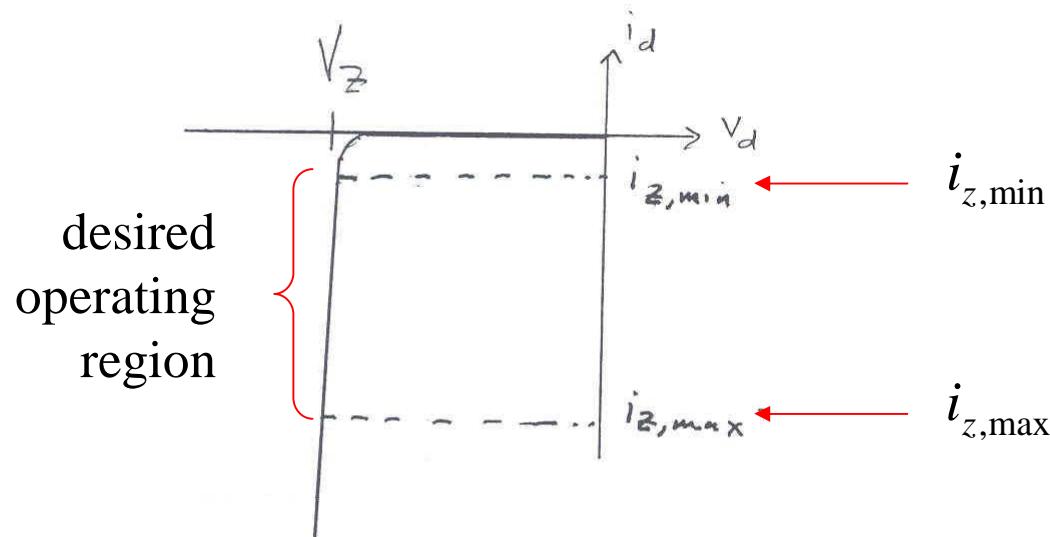
## Step 2: Specify the Zener diode

- We will use a 6.1 V zener diode rated for 0.5 W.
- How do we determine  $i_{z,\text{max}}$  and  $i_{z,\text{min}}$ ?


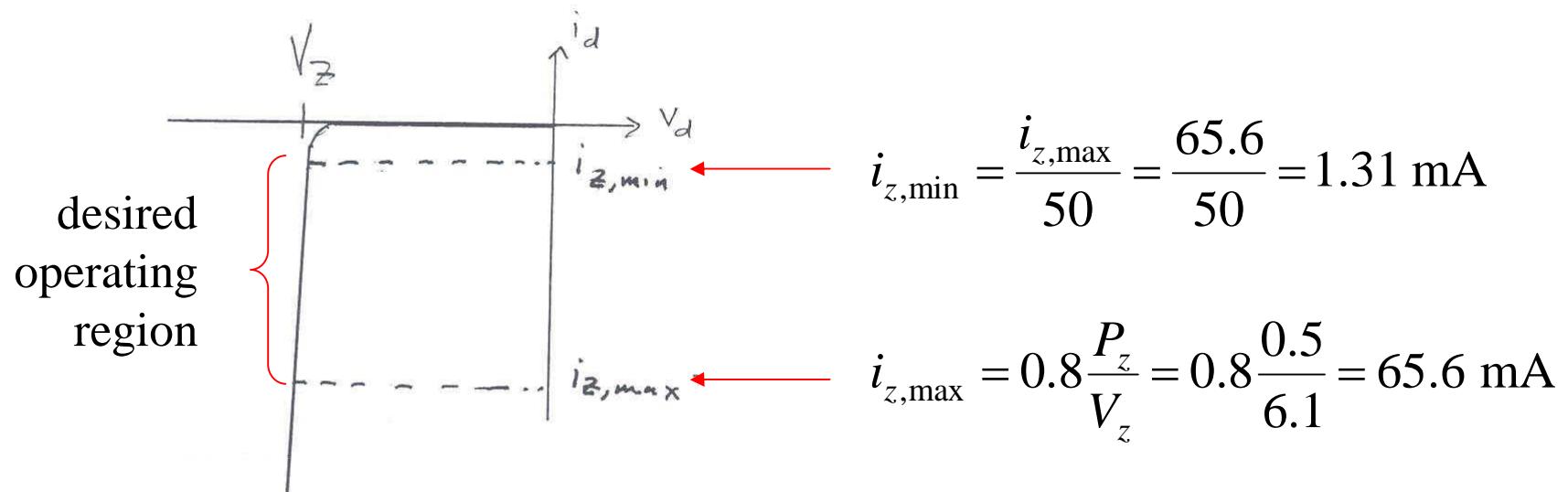
## Step 2: Specify the Zener diode


- We will use a 6.1 V zener diode rated for 0.5 W.
- How do we determine  $i_{z,\max}$  and  $i_{z,\min}$ ?


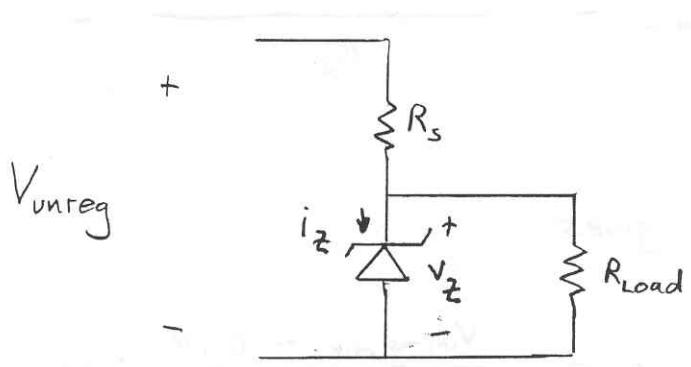
# Step 3: Specify $R_s$

- Recall that

$$i_{z,\max} = \frac{V_{\text{unreg,max}} - V_z}{R_s} - \frac{V_z}{R_{\text{load,max}}}$$



therefore  $i_{z,\max} = 65.6 = \frac{12.9 - 6.1}{R_s} - \frac{6.1}{\infty}$

solving for  $R_s = 103.9 \Omega$

- Because  $103.8 \Omega$  isn't a standard value, we choose  $R_s = 120 \Omega$ 
  - Why choose the next larger value?


## Step 3: Specify $R_s$

- We can now determine the minimum voltage to ensure the diode remains in breakdown.

$$i_{z,\min} = \frac{V_{\text{unreg,min}} - V_z}{R_s} - \frac{V_z}{R_{\text{load,min}}}$$

$$i_{z,\min} = 1.31 = \frac{V_{\text{unreg,min}} - 6.1}{120} - \frac{6.1}{250}$$

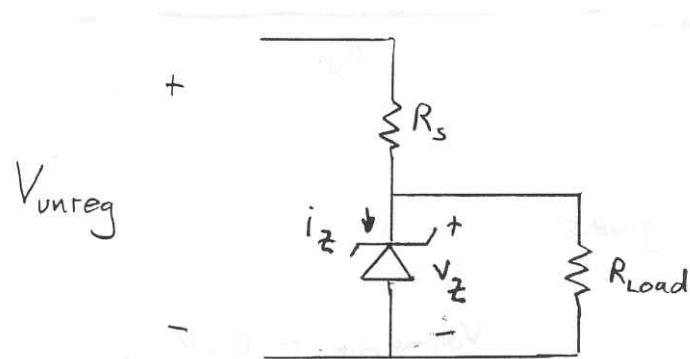
which yields  $V_{\text{unreg,min}} = 9.185 \text{ V}$




- Therefore,  $9.185 < V_{\text{unreg,min}} < 12.9 \text{ V}$   
so our capacitor voltage must achieve a peak-to-peak ripple of  $< 3.71 \text{ V}$ , so we'll choose  $\Delta V = 3 \text{ V}$
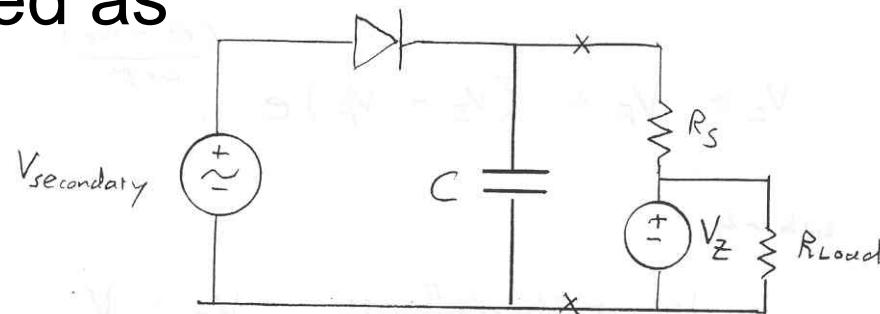
# Step 4: Establish the capacitance

- When the zener is in breakdown, the circuit can be modeled as





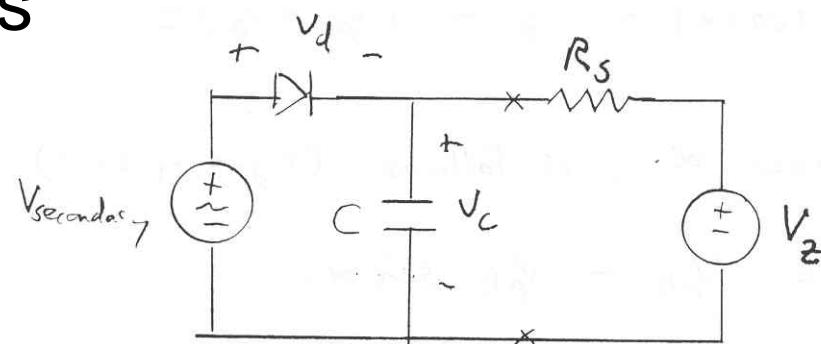- The Thévenin circuit seen to the right of the capacitor is



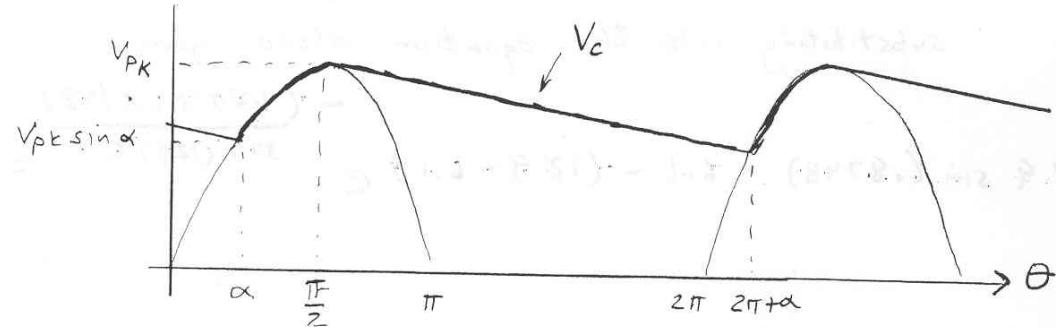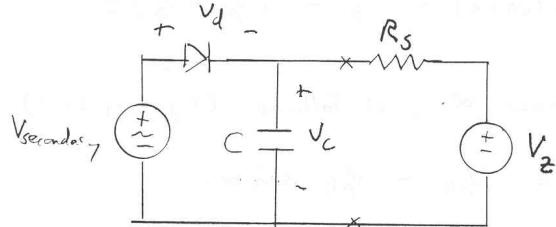
# Step 4: Establish the capacitance

- To simplify, consider we'll assume that the diode conducts until  $\theta = \pi/2$ .



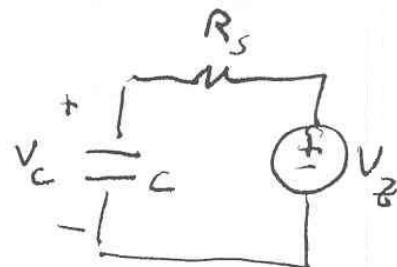- The diode remains off until  $v_d = v_{\text{secondary}} - v_c > 0$
- How do we express the capacitor voltage  $v_c$  ?





# Step 4: Establish the capacitance

- Recall for a capacitor, voltage is given

$$v_c = v_{\text{final}} - (v_{\text{initial}} - v_{\text{final}}) e^{\frac{-(\theta - \pi/2)}{\omega \tau}}$$
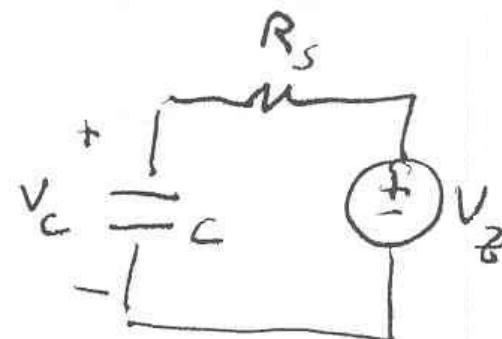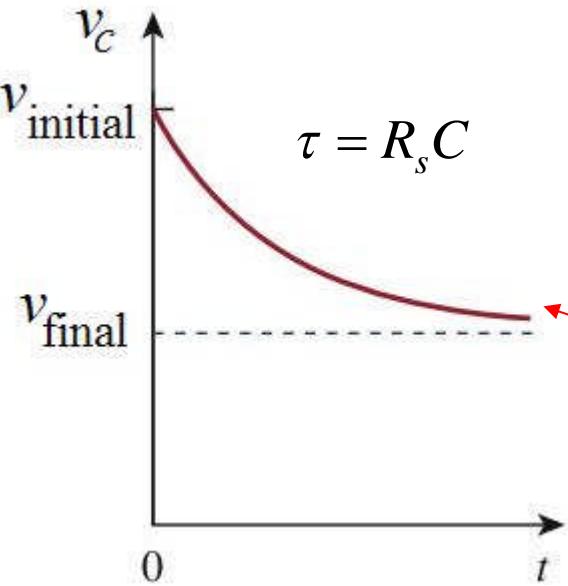
$$v_{\text{initial}} = v_{\text{pk}} \sin \frac{\pi}{2} = v_{\text{pk}}$$



$$v_{\text{final}} = v_z$$


# Step 4: Establish the capacitance

- With an expression for  $v_c$  we now have to solve

$$v_{\text{secondary}} - v_c = 0$$

$$v_{\text{pk}} \sin(2\pi + \alpha) - v_z - (v_{\text{pk}} - v_z) e^{-\left(\frac{2\pi + \alpha - \pi/2}{\omega R_s C}\right)} = 0$$

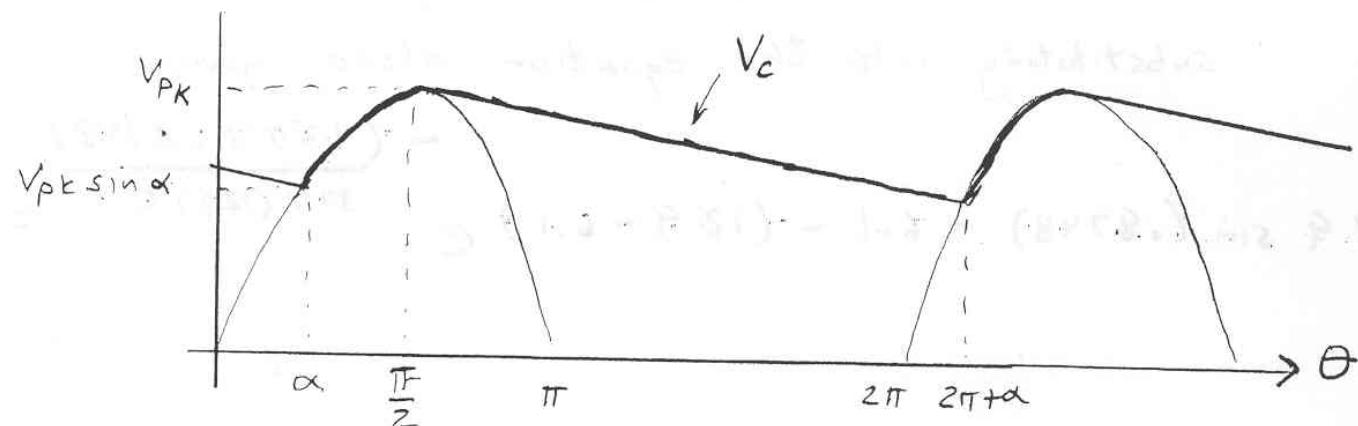
which is a function of  $\alpha$  and  $C$ .


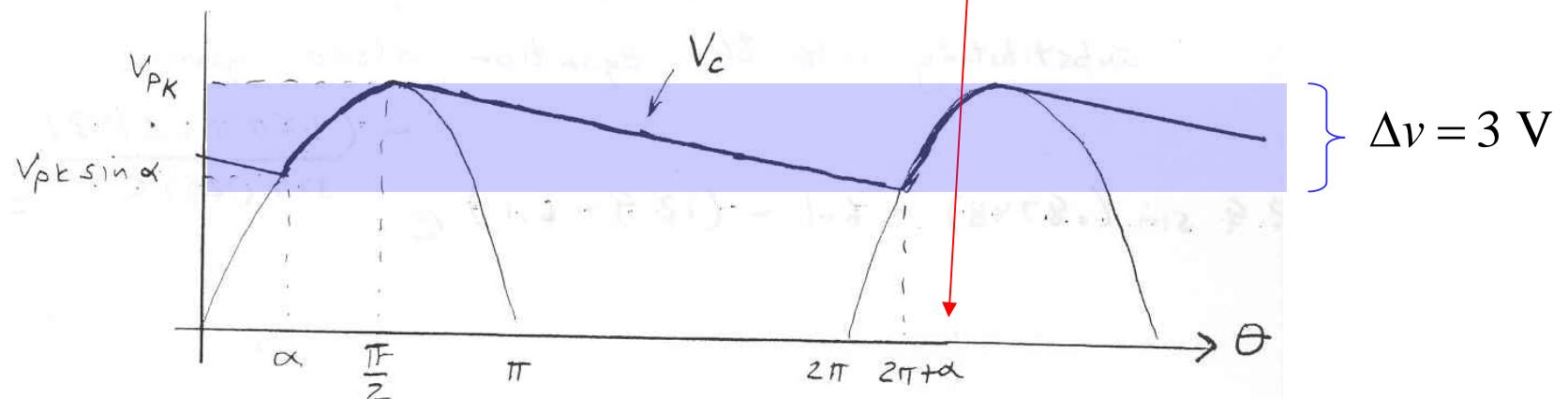
# Step 4: Establish the capacitance

- Recall that  $\Delta v_{\text{out}} = v_{\text{pk}} - v_{\text{pk}} \sin \alpha$  and we set  $\Delta v = 3 \text{ V}$

so we know that  $\sin \alpha = \frac{12.9 - 3}{12.9} \rightarrow \alpha = 0.8748 \text{ rad}$





# Step 4: Establish the capacitance

- Now we can solve

$$v_{pk} \sin(2\pi + \alpha) - v_z - (v_{pk} - v_z)e^{-\left(\frac{2\pi + \alpha - \pi/2}{\omega R_s C}\right)} = 0$$
$$12.9 \sin(0.8748) - 6.1 - (12.9 - 6.1)e^{-\frac{-(2\pi + 0.8748 - \pi/2)}{377(120)C}} = 0$$

- What is  $C$  ?

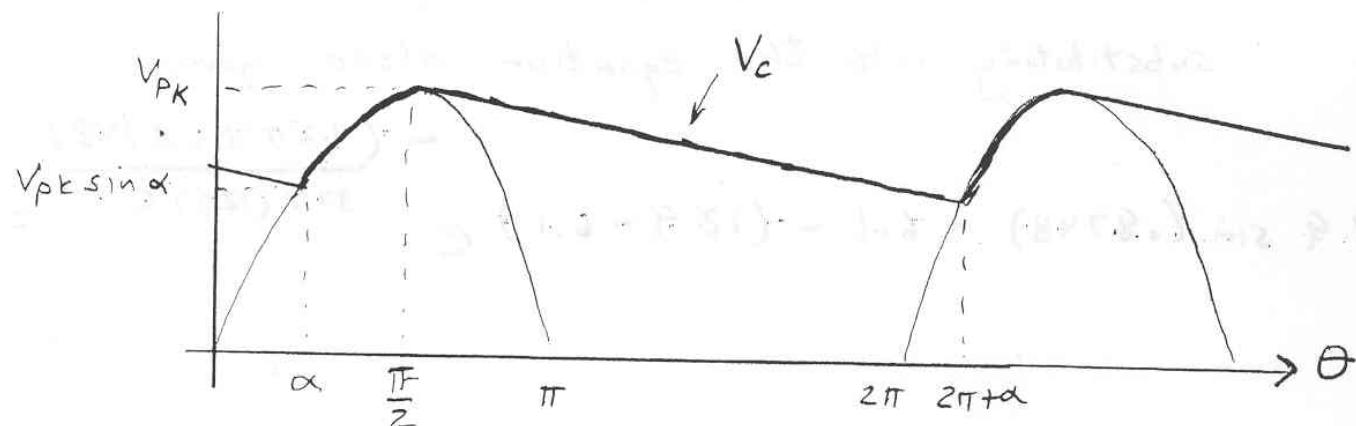

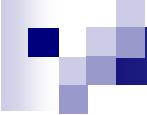

## Step 4: Establish the capacitance

- We find that  $C = 212 \mu\text{F}$  , so we choose the next larger standard value  $220 \mu\text{F}$ .

# Final circuit

- Thus, our  $6.1 \text{ V}_{\text{dc}}$  power supply handling  $250 \Omega < R_{\text{load}} < \infty$  is given

