

# Lesson 4: Voltage and current divider rules

# Circuit analysis toolbox



Ohm's law



Series  
resistance



KVL



Parallel  
resistance




KCL



Circuit analysis  
toolbox
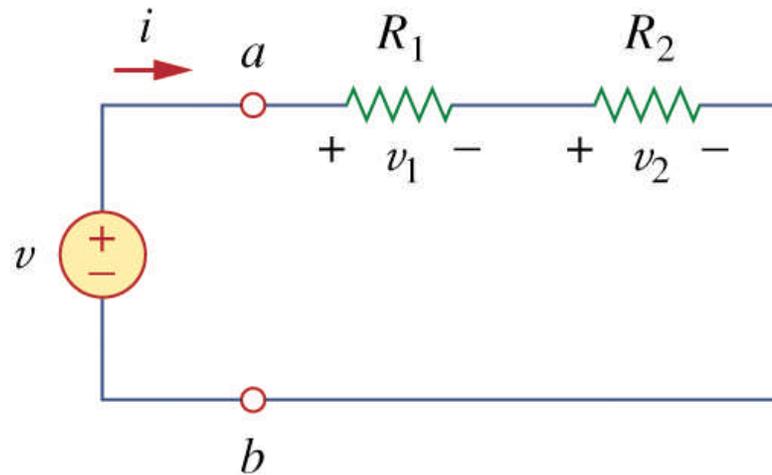
# Voltage across resistors in series


- Let us consider the voltages  $v_1$  and  $v_2$  across resistors in series.


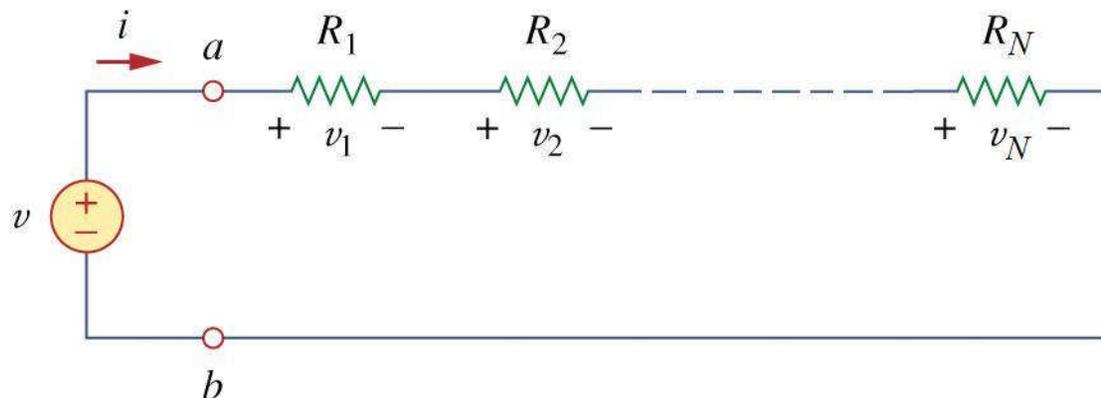
# Principle of voltage division


- The voltage drop across the  $n$ th resistor ( $R_n$ ) is equal to the ratio of  $R_n$  to the total equivalent resistance  $R_{eq}$  times the total voltage across all  $N$  series resistors.

$$v_n = \frac{R_n}{R_1 + R_2 + \dots + R_N} \cdot v = \frac{R_n}{R_{eq}} \cdot v$$



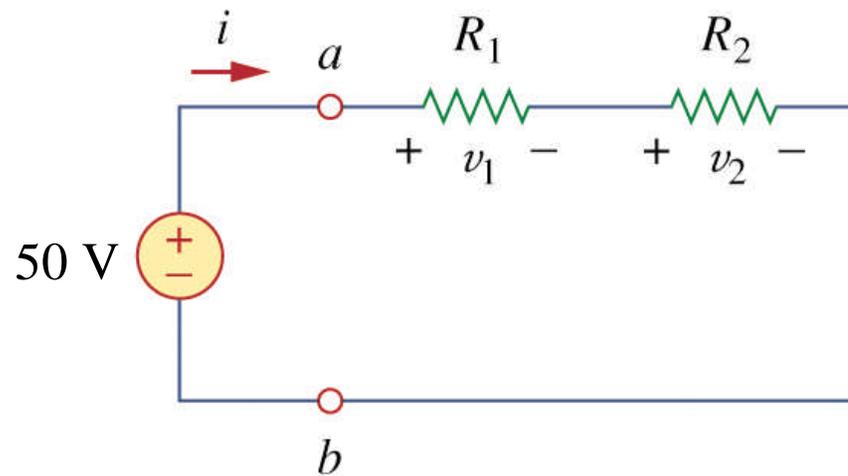
# Example Problem 1

A 50-V source and two resistors,  $R_1$  and  $R_2$  are connected in series. If  $R_2 = 3 R_1$ , find the voltages across the two resistors.


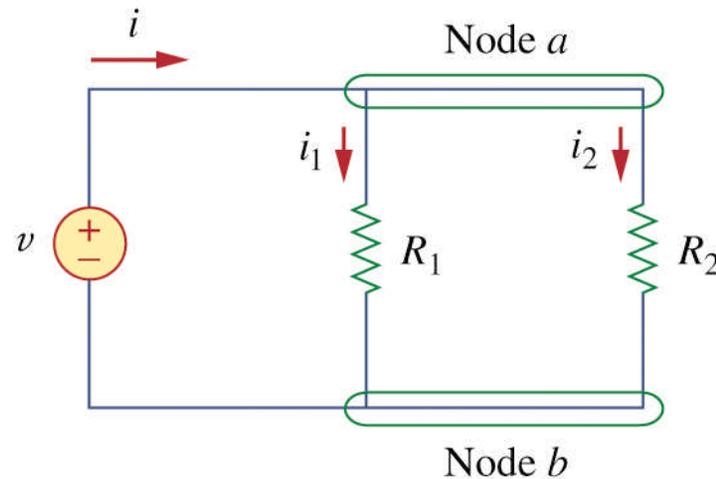
# Current through resistors in parallel


- Let us consider the current  $i_1$  and  $i_2$  through two resistors in parallel.




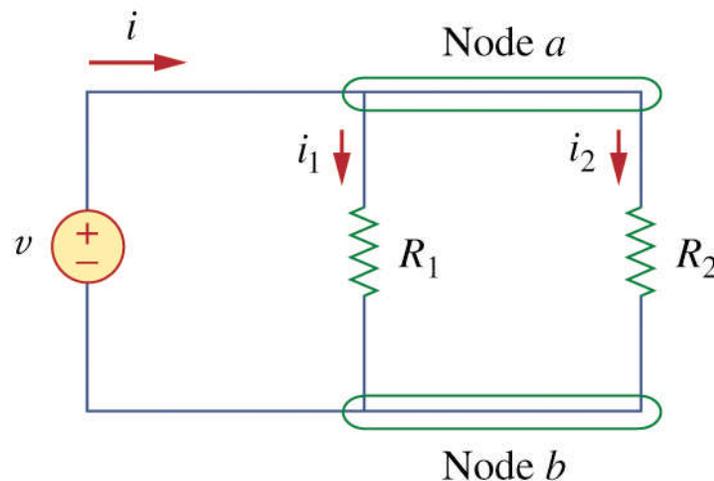
# Principle of current division

- The total current  $i$  is shared by the resistors in **inverse** proportion to their resistances.
- “Current follows the path of least resistance.”

$$i_1 = \frac{R_2 i}{R_1 + R_2} \quad i_2 = \frac{R_1 i}{R_1 + R_2}$$




# Extreme cases for current division

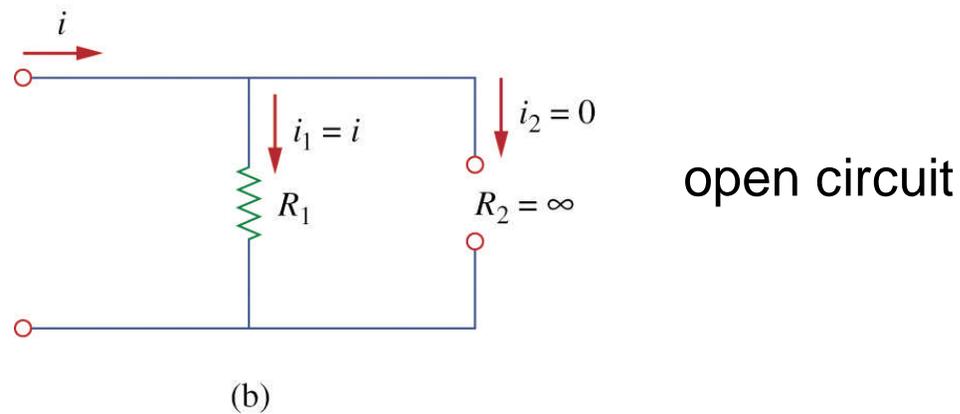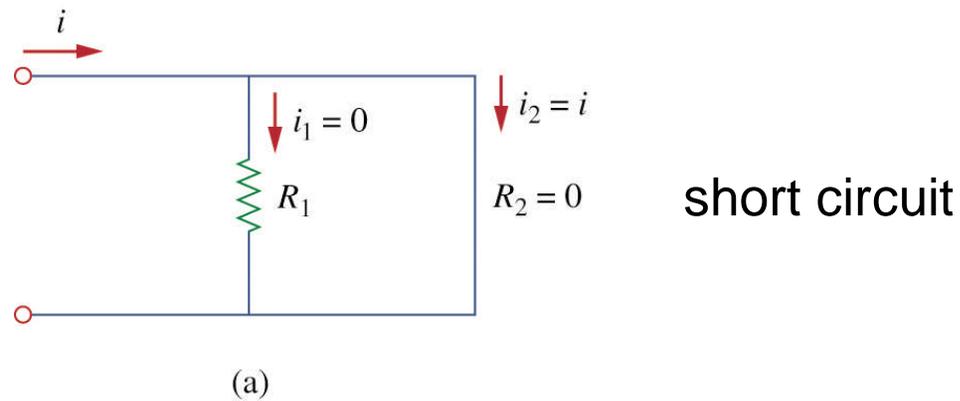
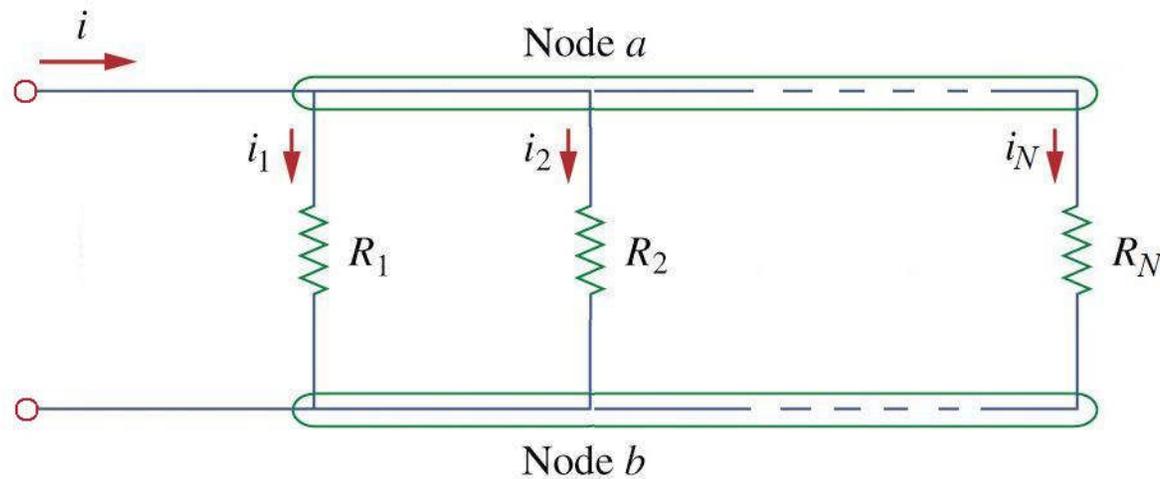
# $N$ resistors in parallel

- What is the current  $i_n$  for  $N$  resistors in parallel?



# Principle of current division

- The current through the  $n$ th resistor ( $R_n$ ) is equal to the **inverse** ratio of  $R_n$  to the total equivalent resistance  $R_{eq}$  times the total current through  $N$  parallel resistors.


$$i_n = \frac{\frac{1}{R_n}}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}} \cdot i = \frac{R_{eq}}{R_n} \cdot i$$

# Current division with conductances

- Using conductances ( $G$ ), the  $n$ th conductor will have current


$$i_n = \frac{G_n}{G_1 + G_2 + \dots + G_N} \cdot i$$

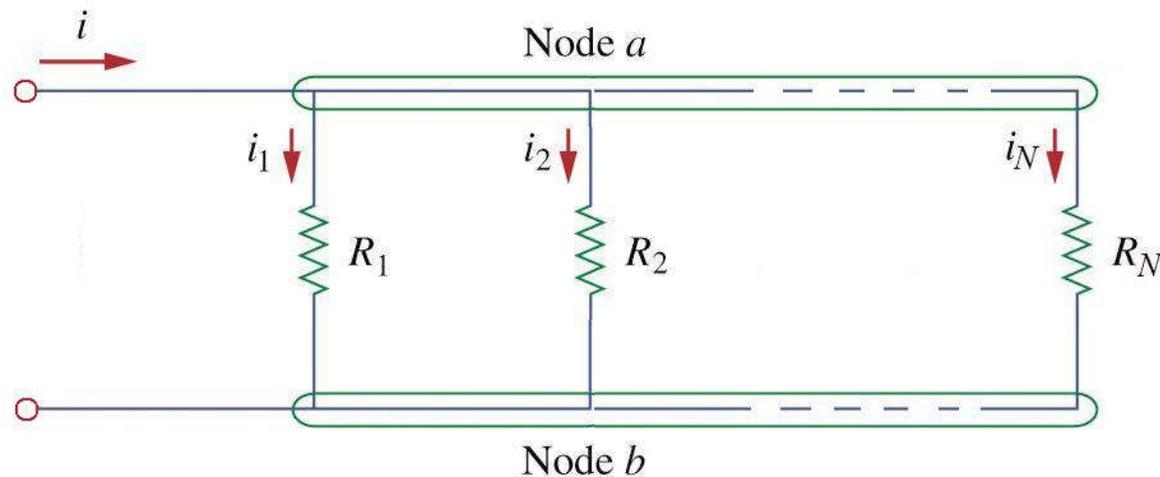where  $G_n = 1/R_n$  for  $n = 1, 2, \dots, N$



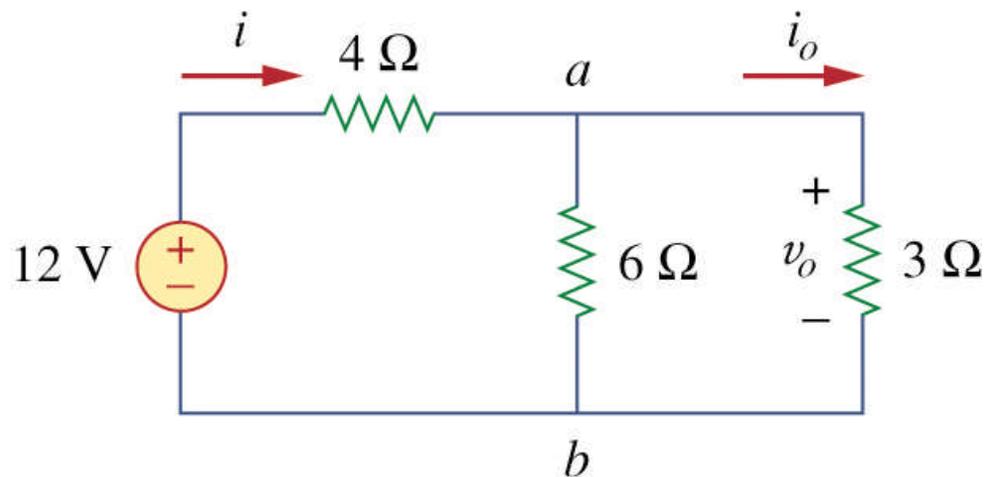
## Example Problem 2

Calculate  $i_o$  and  $v_o$  and find the power dissipated in the 3- $\Omega$  resistor.



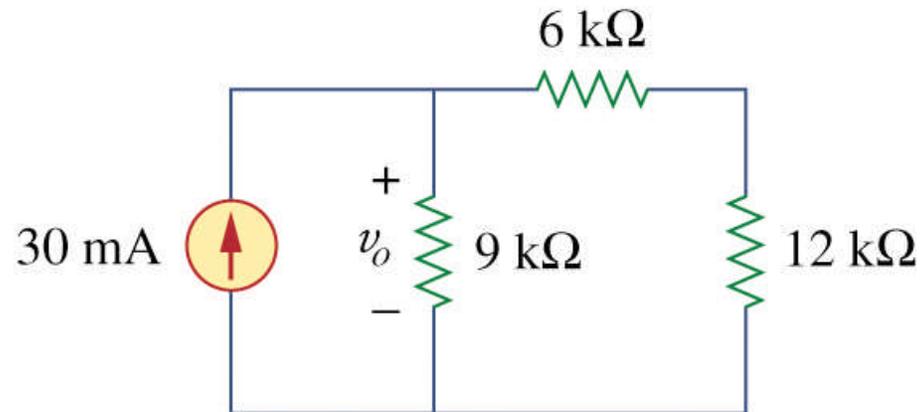
## Example Problem 3

Determine  $v_o$ , the power supplied by the current source, and the power absorbed by each resistor.




# Example Problem 4

Find  $i_1$  through  $i_4$ .

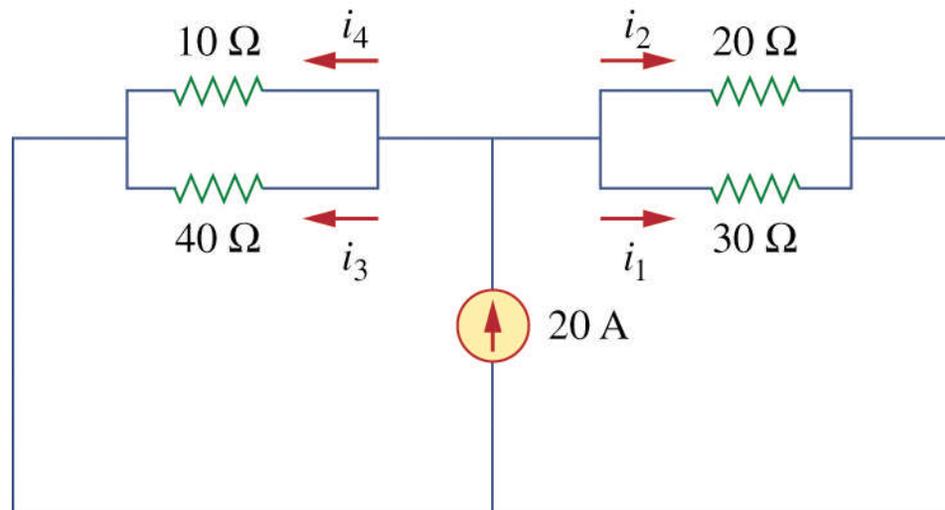

# Example Problem 5

Find  $V_o$  and  $I_o$ .

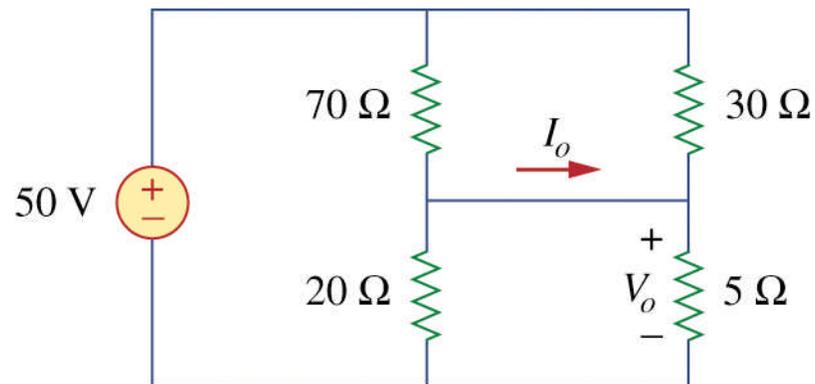

# Circuit analysis toolbox



Ohm's law



Series resistance



Voltage divider rule



KVL



Parallel resistance



Current divider



KCL



Circuit analysis toolbox