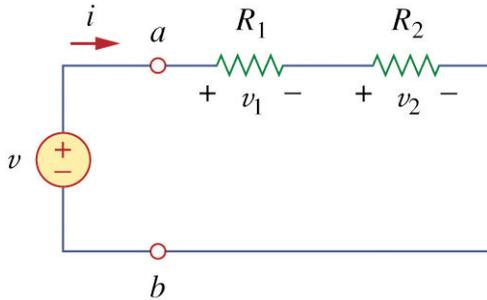


## Lesson 4: Voltage and current divider rules

### Voltage across resistors in series


Let us consider the voltages  $v_1$  and  $v_2$  across resistors in series.



### Principle of voltage division


The voltage drop across the  $n$ th resistor ( $R_n$ ) is equal to the ratio of  $R_n$  to the total equivalent resistance  $R_{eq}$  times the total voltage across all  $N$  series resistors.

$v_n =$

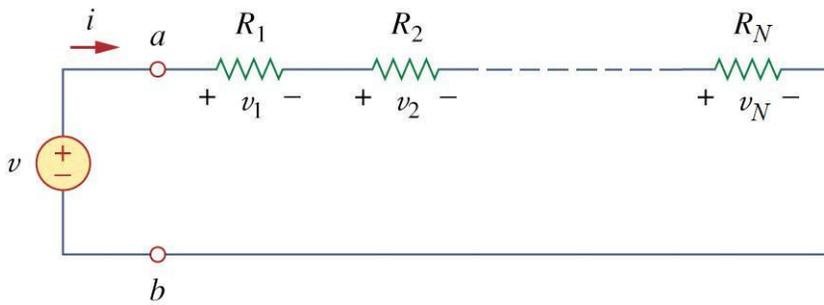
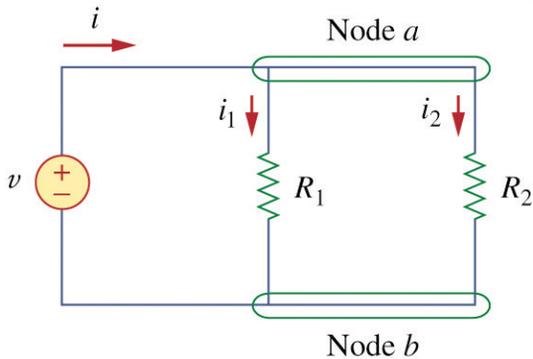
### Current through resistors in parallel

Let us consider the current  $i_1$  and  $i_2$  through two resistors in parallel.





### Principle of current division

The total current  $i$  is shared by the resistors in \_\_\_\_\_ proportion to their resistances.  
“Current follows \_\_\_\_\_.”

$i_1 =$


$i_2 =$

### Extreme cases for current division

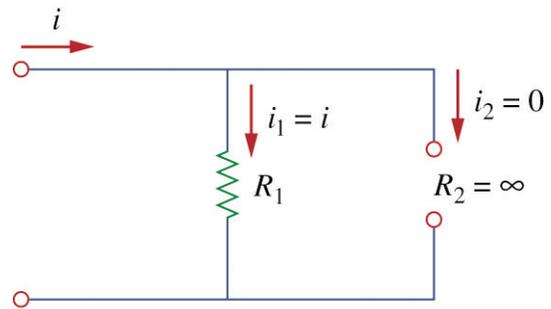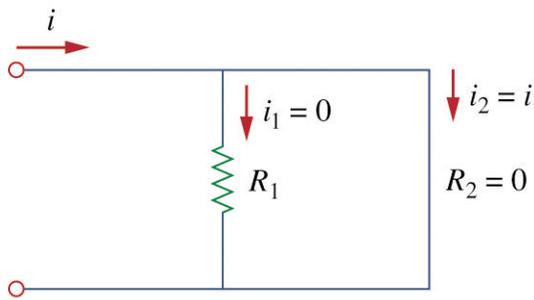
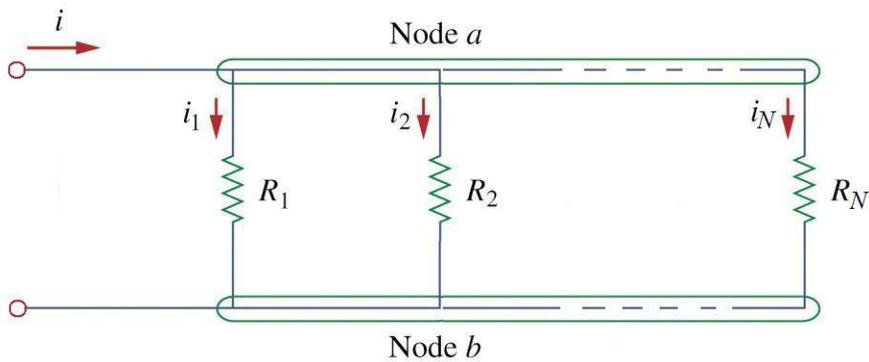
### $N$ resistors in parallel

What is the current  $i_n$  for  $N$  resistors in parallel?



### Principle of current division

The current through the  $n$ th resistor ( $R_n$ ) is equal to the **inverse** ratio of  $R_n$  to the total equivalent resistance  $R_{eq}$  times the total current through  $N$  parallel resistors.

$$i_n =$$


### Current division with conductances

Using conductances ( $G$ ), the  $n$ th conductor will have current

$$i_n =$$

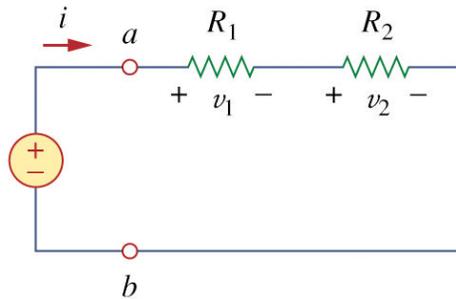
### Example Problem 1

A 50-V source and two resistors,  $R_1$  and  $R_2$  are connected in series. If  $R_2 = 3 R_1$ , find the voltages across the two resistors.



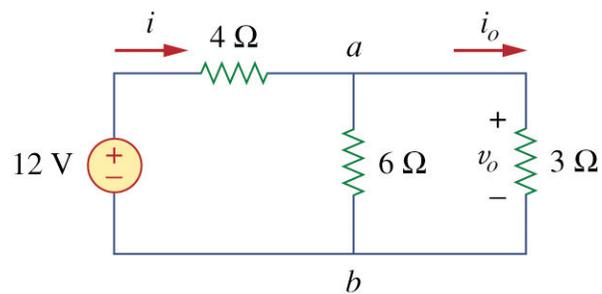
### Example Problem 2

Calculate  $i_o$  and  $v_o$  and find the power dissipated in the 3- $\Omega$  resistor.



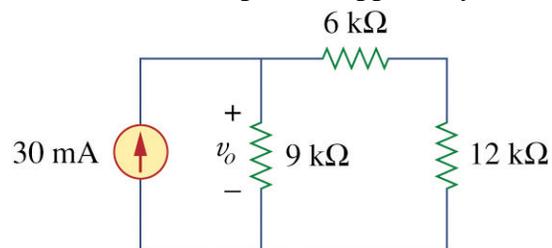
### Example Problem 3

Determine  $v_o$ , the power supplied by the current source, and the power absorbed by each resistor.



### Example Problem 4

Find  $i_1$  through  $i_4$ .

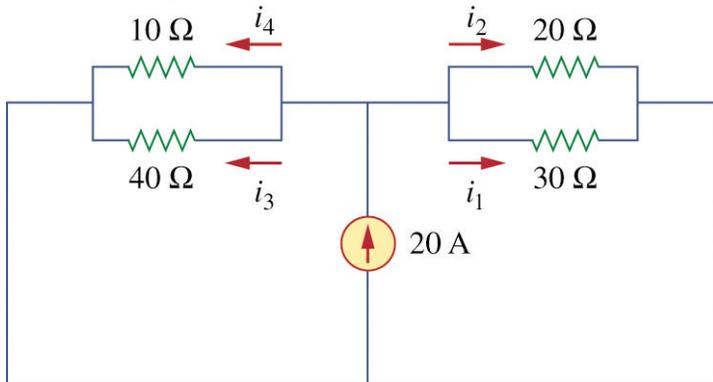

### Example Problem 5

Find  $V_o$  and  $I_o$ .

