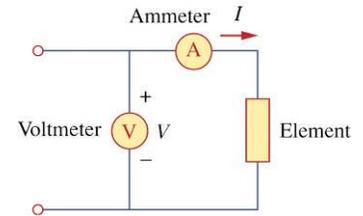


## Lesson 5: Practical sources and meters

### Ideal meters

For accurate measurement, our meters should not affect the parameters being measured.


- An ideal ammeter should have no voltage drop across it and hence \_\_\_\_\_ resistance.
- An ideal voltmeter should shunt no current through it and hence \_\_\_\_\_ resistance.


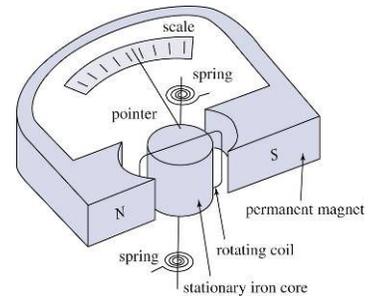
### The d'Arsonval meter

D'Arsonval meters are constructed by suspending an coil between the poles of a permanent magnet.

They are characterized by their \_\_\_\_\_ ( $I_{fs}$ ) which will cause the meter to fully deflect, typically 10- $\mu$ A to 10-mA. The rotating coil has a small resistance ( $R_m$ ).



### Ammeters

Large currents are handled by adding a \_\_\_\_\_ resistor ( $R_n$ ).

### Voltmeters


A d'Arsonval meter can also function as a voltmeter by combining it with a large series resistance ( $R_n$ ).

### Ohmmeters

To measure resistance, we need to know both voltage and current.

Ohmmeter consists of a d'Arsonval meter, a variable resistor ( $R$ ) and a \_\_\_\_\_ ( $E$ ).

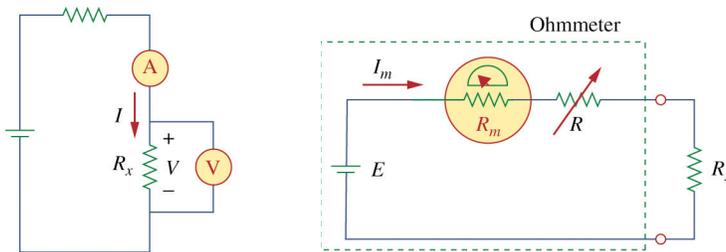- How do we choose  $R$  such that  $I_m = I_{fs}$  when  $R_x = 0 \Omega$  ?




### Ideal sources

An ideal source is an active element that provides a specified voltage or current that is completely independent of other circuit elements.

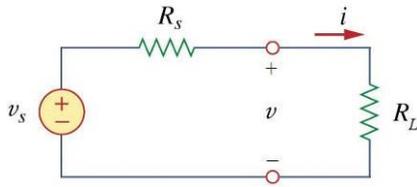
### Practical voltage sources

A real or \_\_\_\_\_ source supplies its rated voltage when its terminals are not connected to a load (\_\_\_\_\_) but its voltage drops off as the current it supplies increases.

We can model a practical source using an ideal source  $v_s$  in series with an \_\_\_\_\_ resistance  $R_s$ .



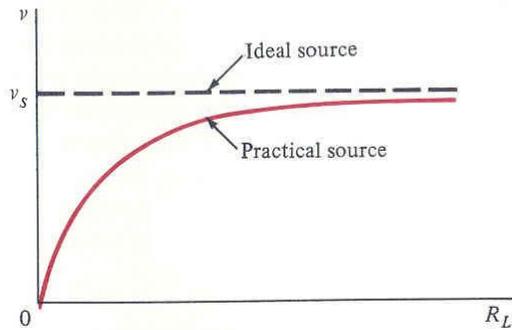
For a practical voltage source, both  $i$  and  $v$  vary with  $R_L$ .



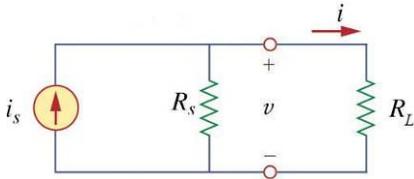
### Practical current source

A practical current source supplies its rated current when its terminals are \_\_\_\_\_ but its current drops off as the load increases.

We can model a practical current source using an ideal current source  $i_s$  in parallel with an internal resistance  $R_s$ .




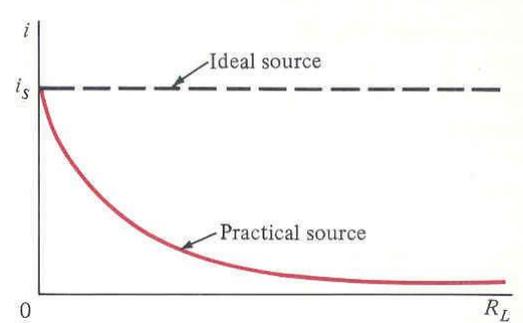For a practical current source, both  $i$  and  $v$  vary with  $R_L$ .


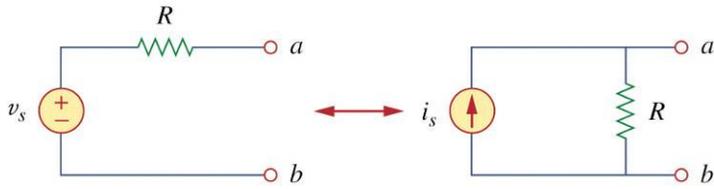
### Source transformation


The two circuits representing practical sources are actually \_\_\_\_\_ circuits.



Source transformation is the process of replacing a voltage source  $v_s$  in \_\_\_\_\_ with a resistor  $R$  by a current source  $i_s$  in \_\_\_\_\_ with a resistor  $R$ , or vice versa.

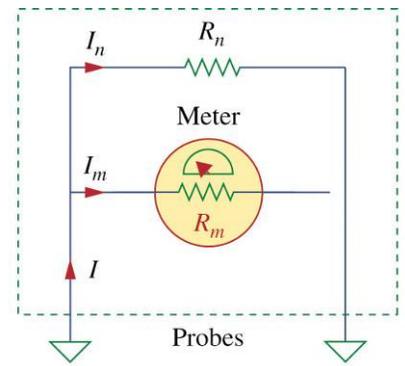
### Example Problem 1

If a d'Arsonval meter has an internal resistance  $R_m = 50 \Omega$  and a full-scale current  $I_{fs} = 1 \text{ mA}$ , determine  $R_n$  such that the meter will fully deflect when  $I = 1 \text{ A}$ .


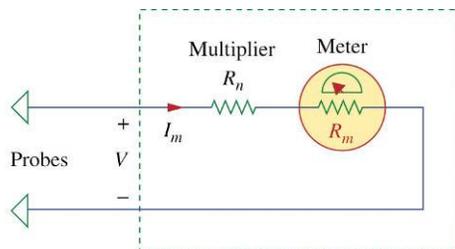
### Example Problem 2

Determine  $R_n$  for a voltmeter to have a full-scale voltage of  $100 \text{ V}$  using a d'Arsonval meter with  $R_m = 100 \Omega$  and a full-scale current  $I_{fs} = 50 \mu\text{A}$ .



### Example Problem 3

Use source transformation to determine  $v_o$ .

