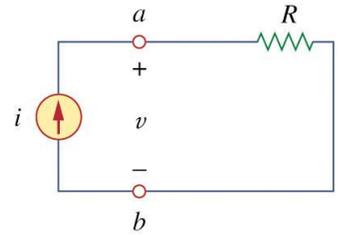


Lesson 7: Network Analysis 2: Thévenin's theorem

Linear circuits

Linear circuits are circuits composed of elements with a linear voltage-current (v - i) characteristic.

Resistors are an example of a linear element.



Requirements for linearity

Homogeneity (scaling) - Multiplying the excitation i by a constant k results in the response v also being scaled by k . if $v = iR$ then $kv =$

Additivity – the response to a sum of inputs is the sum of the responses to each input applied separately.

if $i = i_1 + i_2$ and $v_1 = i_1R$ and $v_2 = i_2R$, then

$$v = iR = (i_1 + i_2)R = i_1R + i_2R = v_1 + v_2$$

Superposition

A direct result of additivity is principle of superposition.

Superposition states that the voltage across (or current through) an element in a linear circuit is the _____ of the voltages across (or currents through) that element due to each independent source acting alone.



Applying superposition

1. _____ all but one _____ sources and determine the output (voltage or current) due to that source (leave dependent sources intact).
2. Repeat for each of the other independent sources.
3. _____ the individual contributions to determine the total response.

“Turning off” sources


“Turning off” a source means setting its value equal to _____.

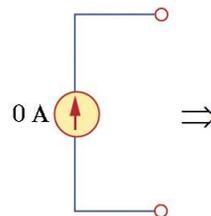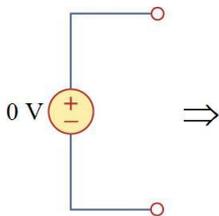- Voltage sources – 0 V is equivalent to a _____.
- Current sources – 0 A is equivalent to a _____.




Source transformation

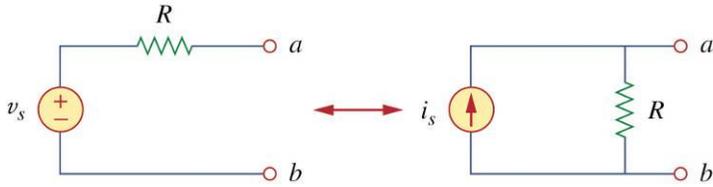Source transformation is another circuit analysis technique that allows us to replace a voltage source v_s in _____ with a resistor R by a current source i_s in _____ with a resistor R , or vice versa.




The two circuits are equivalent provided they have the same voltage-current characteristic at terminals a - b .

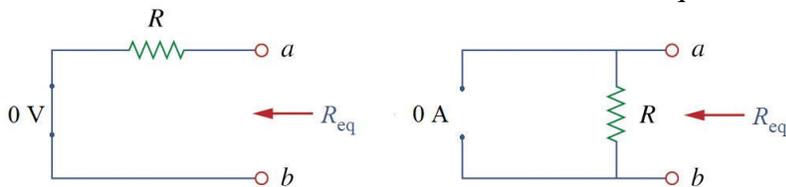If we turn off each source, note the both circuits an equivalent resistance R_{eq} .



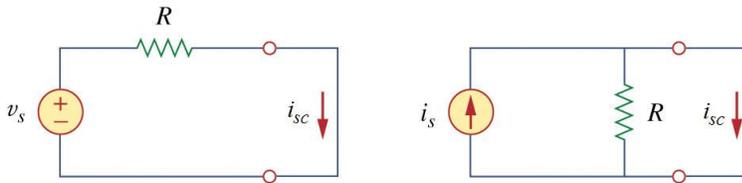If we short-circuit the terminals the short-circuit current $i_{sc} = v_s/R$.



Thus, if _____ the two circuits are equivalent.



Thévenin's theorem

Thévenin's theorem greatly simplifies analysis of complex linear circuits by allowing us to replace all of the elements with a combination of just one voltage source and one resistor.

Thévenin's theorem is another power tool.


Thévenin's theorem states that a linear two-terminal circuit can be replaced by an equivalent circuit consisting of a _____ V_{Th} in series with a _____ R_{Th} where

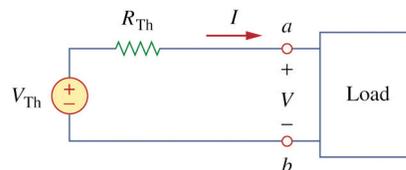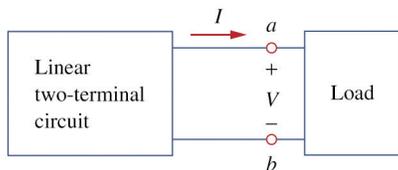- V_{Th} is the open circuit voltage at the terminals, and
- R_{Th} is the input or equivalent resistance at the terminals when the independent sources are turned off.




Equivalence

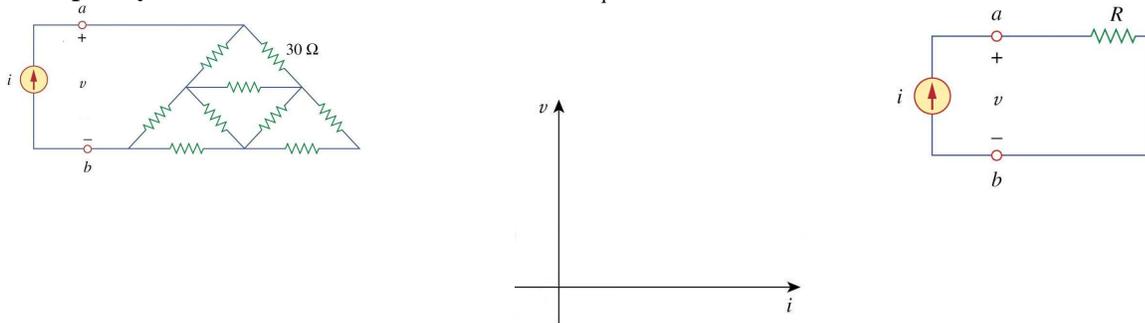Two circuits are said to be equivalent if they have the same voltage-current (v - i) relationship. For purely resistive networks we've found R_{eq} .



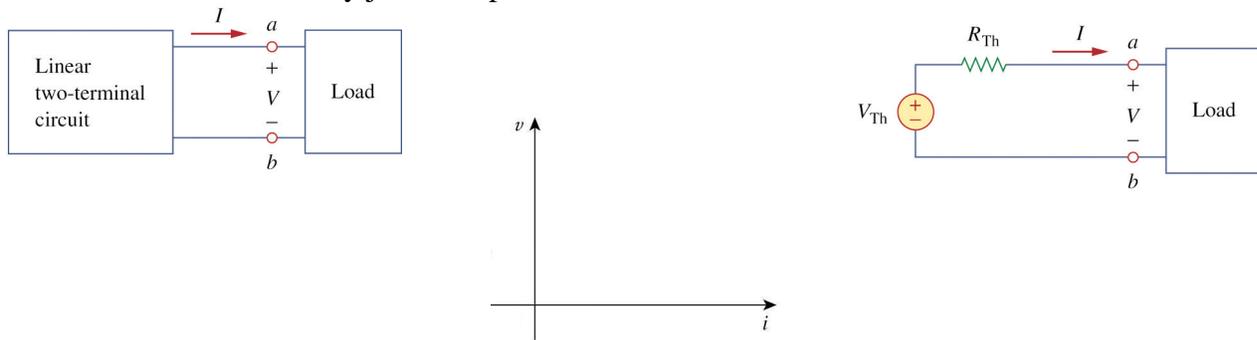Thévenin's theorem is really just an expansion to include networks with sources.



Determining V_{Th}

Referring to the plot, V_{Th} is voltage response when $i = 0$, therefore we just need to _____ (open-circuit) and measure the resulting voltage.



Determining R_{Th}



With the load disconnected, turn off all independent sources.

R_{Th} is equivalent resistance looking into the "dead" circuit through terminals a - b .




Case 1: If no _____ sources exist, find R_{Th} .

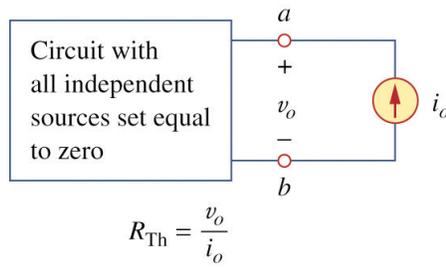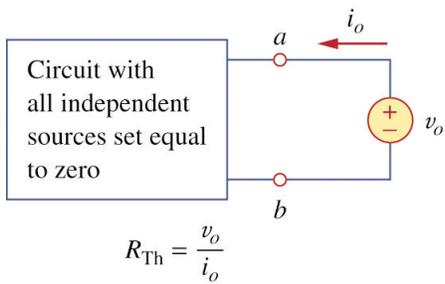Case 2: If the network contains dependent sources, apply any voltage at v_o and determine resulting i_o (or vice-versa). Thus, $R_{Th} = v_o / i_o$.



Negative R_{Th}

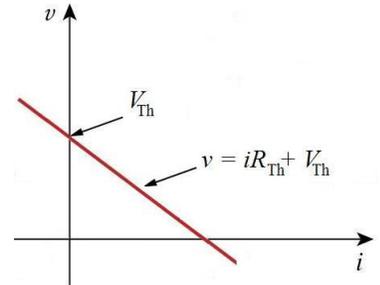With dependent sources present, it is possible that R_{Th} will be negative, implying that the circuit is providing power.





Applying Thévenin equivalent

Once V_{Th} and R_{Th} have been found, the original circuit is replaced by its equivalent and solving for I_L and V_L becomes trivial.


$I_L =$

$V_L =$

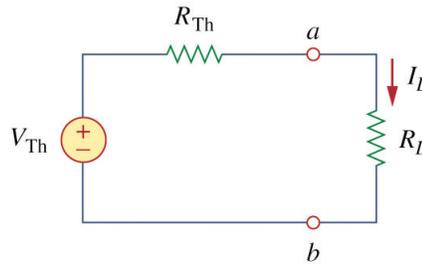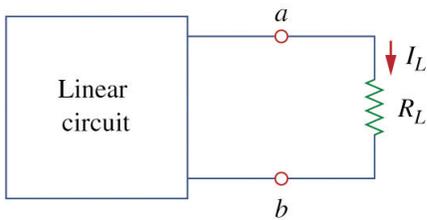

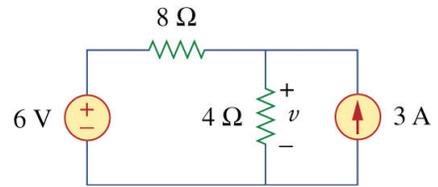
Example Problem 1

Use superposition to find v in the circuit.



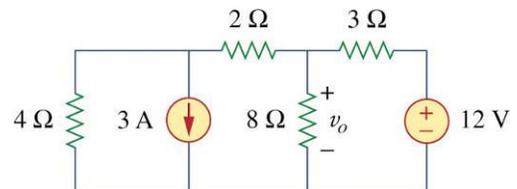Example Problem 2


Use source transformation to determine v_o .



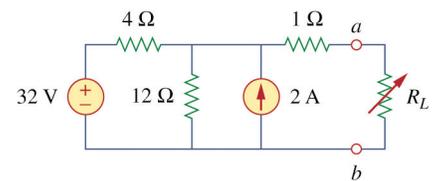Example Problem 3


Find the Thévenin equivalent circuit to the left of terminals a - b .

Then find the current through $R_L = 6, 16, \text{ and } 36\ \Omega$.



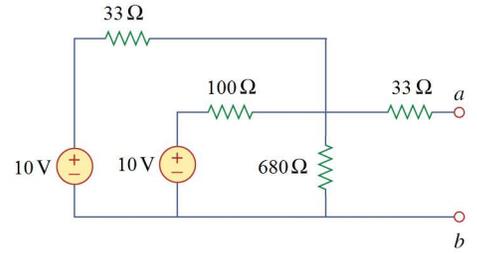Example Problem 4

Find the Thévenin equivalent of the circuit at terminals a - b .



Example Problem 5

Find the Thévenin equivalent of the circuit at terminals a - b .

