

**Lesson 8:
Network Analysis 3:
Maximum Power Transfer**

Circuit analysis toolbox



Ohm's law



Series resistance



Voltage divider rule



Nodal analysis



Thévenin's theorem



KVL



Meters



Circuit analysis toolbox



KCL



Parallel resistance



Current divider



Source transformation


Maximum power transfer

- In some applications, the purpose of a circuit is to provide maximum power to a load.
 - Stereo amplifiers
 - Radio transmitters
- While analysis of the amplifier circuit may be daunting, Thévenin's theorem provides a simple method to examine this problem.




NAD C372 Stereo Integrated Amplifier

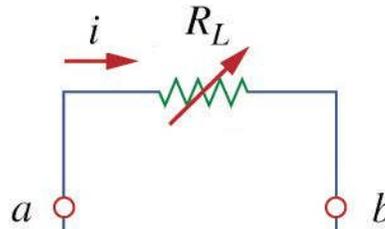- What load should be connected to maximize power transfer?



Power to the load

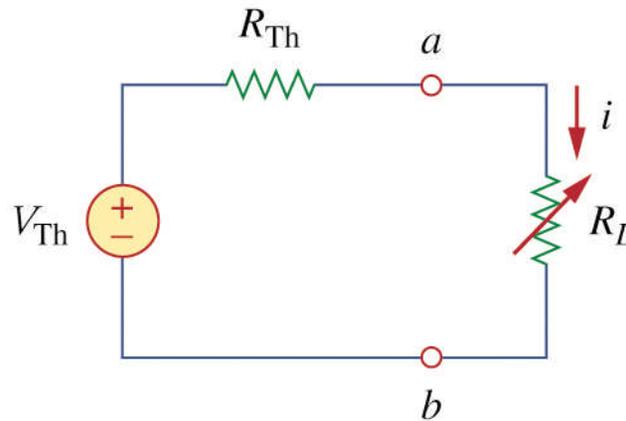
- We will replace the amplifier with a Thévenin equivalent.
- Consider the case that V_{Th} and R_{Th} are fixed and the load resistance R_L is variable.




- What is the power p_L delivered to the load?

Maximizing p_L

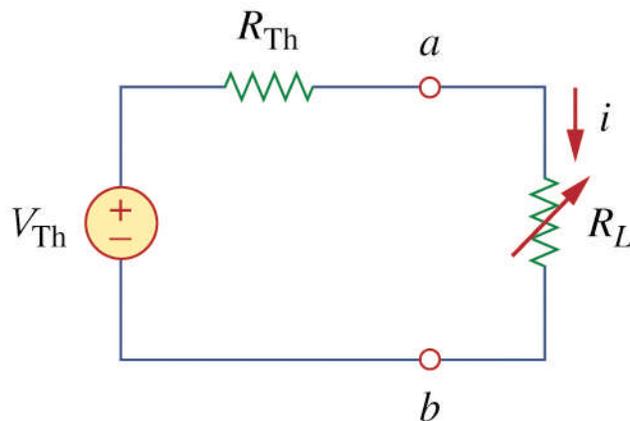- How might we determine R_L such that p_L is maximized?


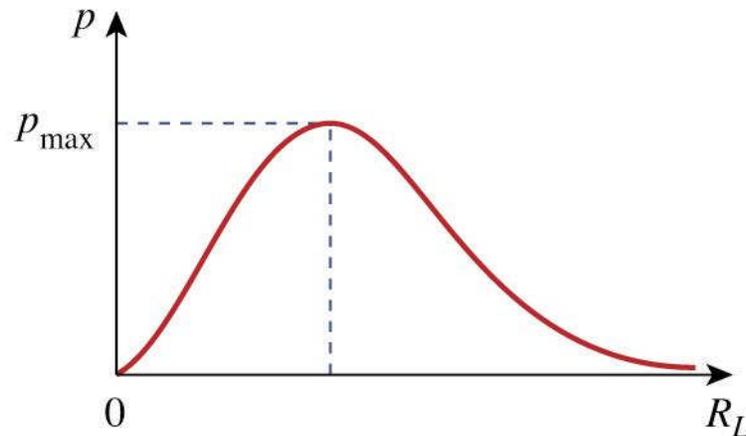
$$p_L = i^2 R_L = \left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$




Maximizing p_L

- Taking the derivative of p_L and setting it equal to zero, we find that

$$\frac{dp_L}{dR_L} = \frac{d}{dR_L} \left[\left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L \right] = V_{Th}^2 \left[\frac{R_{Th} - R_L}{(R_{Th} + R_L)^3} \right] = 0$$


This implies $R_{Th} - R_L = 0$

which yields $R_L = R_{Th}$

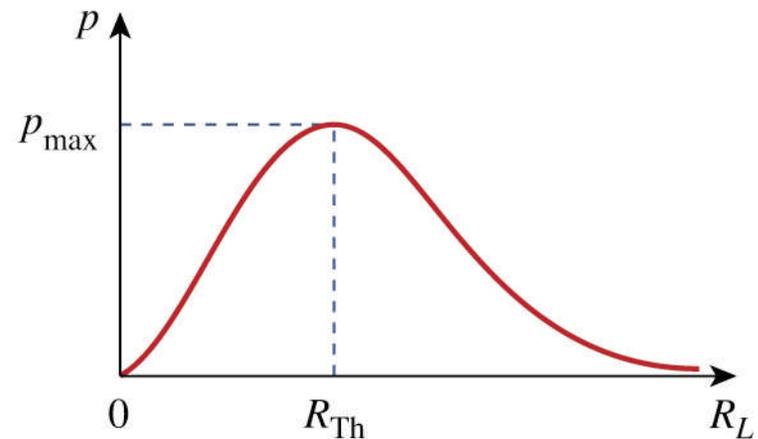

Maximum power transfer theorem

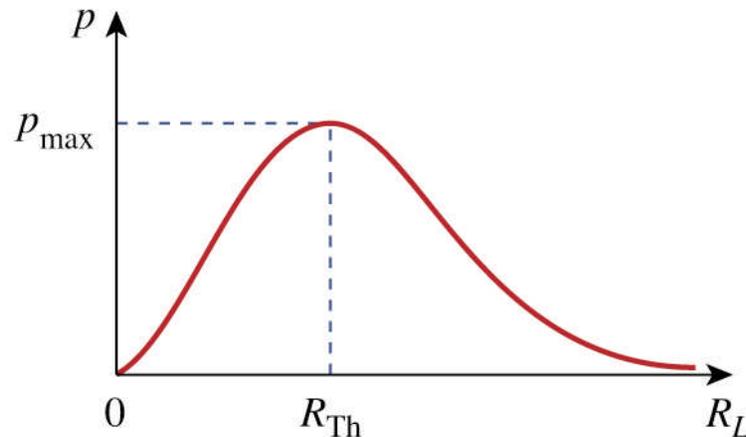- **Maximum power** is transferred to the load when the load resistance equals the Thévenin resistance as seen from the load ($R_L = R_{Th}$).
 - When $R_L = R_{Th}$, the source and load are said to be **matched**.



- Given $R_L = R_{Th}$, what is p_{max} ?



Maximum power

- The power delivered when $R_L = R_{Th}$ is

$$p_{\max} = \frac{V_{Th}^2}{4R_{Th}}$$

- Note that this is not true when $R_L \neq R_{Th}$.
- What does this say about efficiency (η)?

$$\eta = \frac{P_{\text{out}}}{P_{\text{in}}} \times 100\%$$

Efficiency


- When maximum power is delivered to R_L , the efficiency is a mere 50%.

$$\eta = \frac{p_{\text{out}}}{p_{\text{in}}} = \frac{i^2 R_L}{i^2 R_{\text{Th}} + i^2 R_L} \times 100\% = \frac{i^2 R_{\text{Th}}}{i^2 R_{\text{Th}} + i^2 R_{\text{Th}}} \times 100\% = 50\%$$

- Efficiency is maximized as $R_L \rightarrow \infty$.

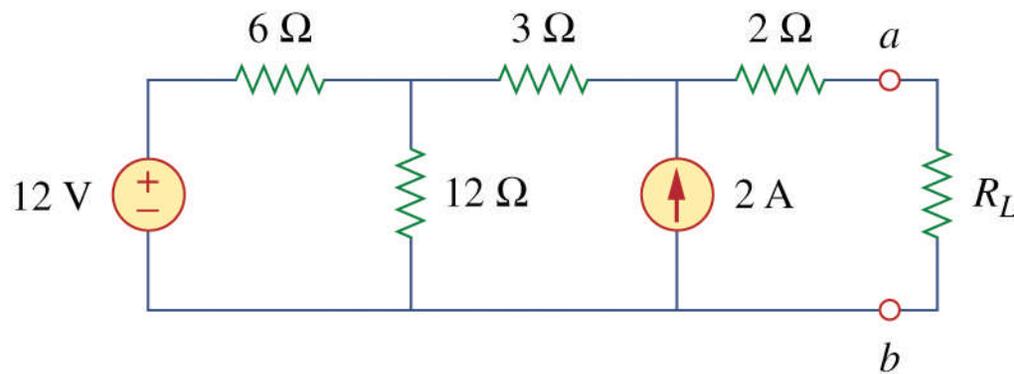Example Problem 1

Find the value of R_L for maximum power transfer in the circuit below. Find the maximum power.




Example Problem 2

According to the NAD C372 specs, maximum output power is 150 W per channel when $R_L = 8 \Omega$. What would the output power be if two 8Ω speakers were connected in parallel to one of the channels?



PSB Image T65

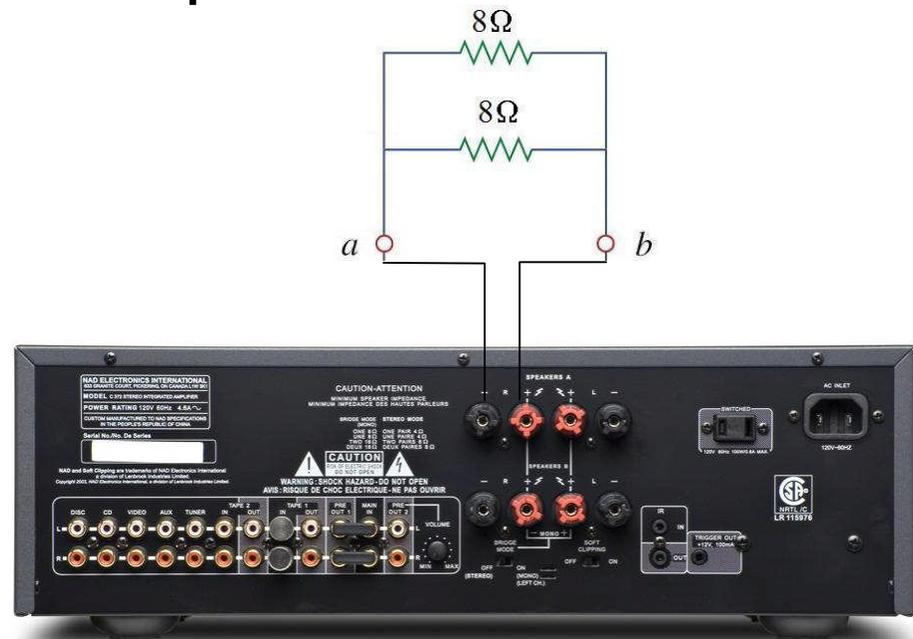

NAD C372 specifications

Minimum impedance warning

- Note the caution about “minimum speaker impedance.”
- In stereo mode, the minimum impedance for one pair is 4- Ω and for two pairs is 8- Ω .

