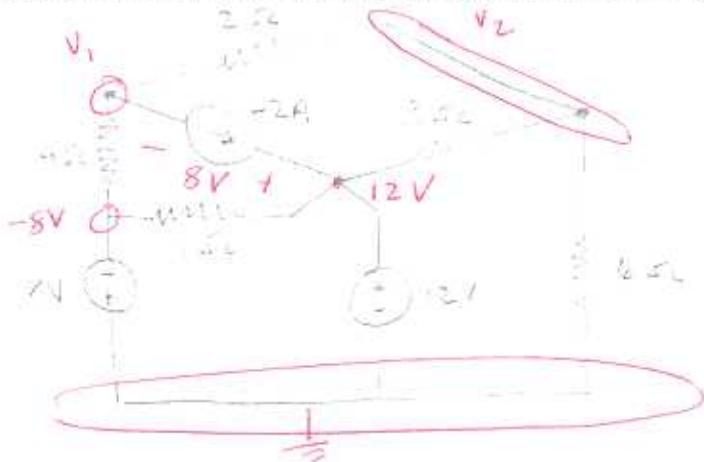


EE331 – Final Review

- I. Determine the power delivered by the current source in the circuit depicted below:




$$\frac{v_1 + 8}{4} + \frac{v_1 - v_2}{2} = 2 \Rightarrow v_1 + 8 + 2v_1 - 2v_2 = 8$$

$$3v_1 - 2v_2 = 0$$

$$\frac{v_2 - v_1}{2} + \frac{v_2 - 12}{3} + \frac{v_2}{6} = 0 \Rightarrow 3v_2 - 3v_1 + 2v_2 - 24 + v_2 = 0$$

$$-3v_1 + 6v_2 = 24$$

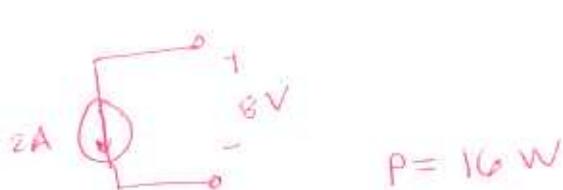


$$v_2 = 6$$

$$v_1 = 4$$

16W is being dissipated by the current source
-16W delivered.

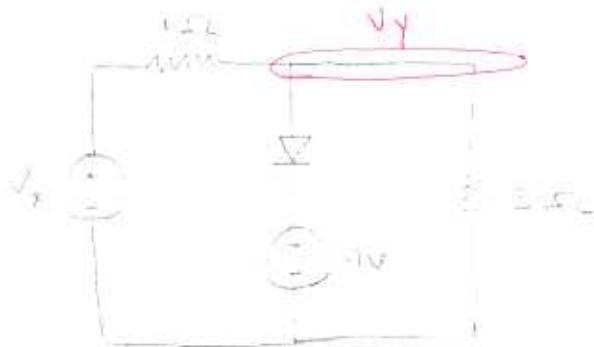2. Determine the range of V_x in the circuit below that will cause the ideal diode to be on (conducting).



in order for the diode to conduct $V_y - 9 > 0$
 $V_y > 9$

when is $V_y = 9 \text{ V}$?


If diode is off ($V_y \leq 9 \text{ V}$) then

$$V_y = \frac{3}{1+3} V_x$$


$$9 = \frac{3}{4} V_x \Rightarrow V_x = 12 \text{ V}$$

diode conducts when $V_x > 12 \text{ V}$

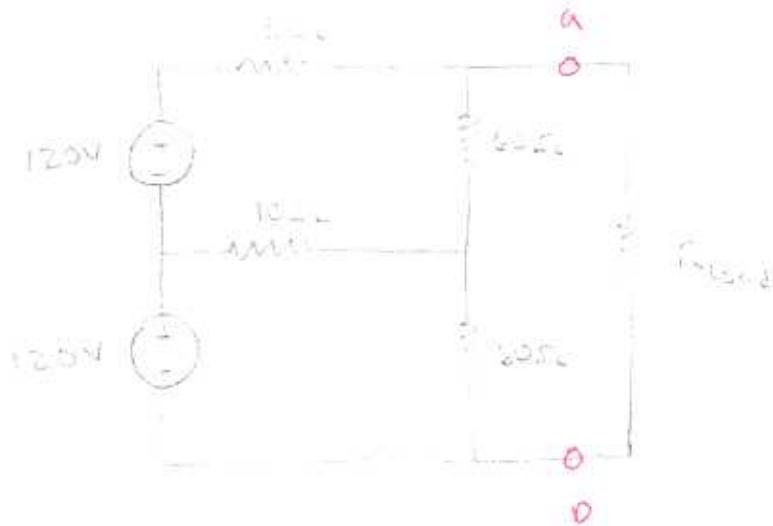
3. Calculate and draw the Thevenin equivalent circuit seen by R_{load} in the following circuit.



① calculate R_{th}

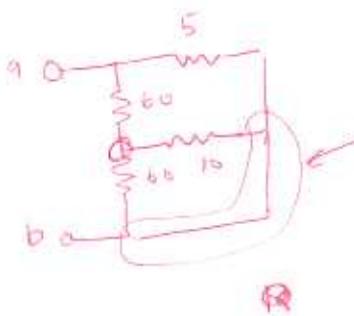

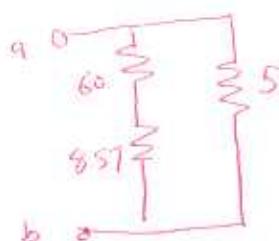
$$60 \parallel 10 = \frac{60 \cdot 10}{60 + 10} = 8.57 \Omega$$



$$R_{th} = 5 \parallel (60 + 8.57) \\ = 4.66 \Omega$$

② calculate V_{th}

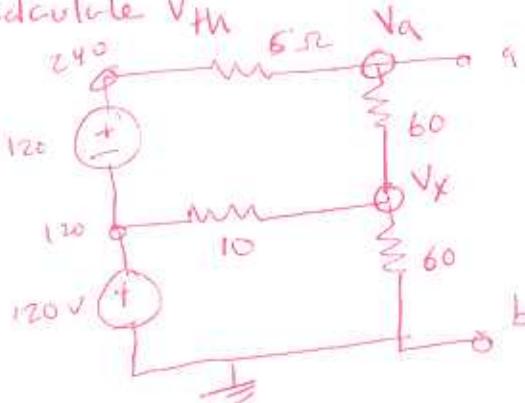

use nodal:

$$\textcircled{1} \quad \frac{V_a - 240}{5} + \frac{V_a - V_x}{60} = 0$$


$$\textcircled{2} \quad \frac{V_x - V_a}{60} + \frac{V_x - 120}{10} + \frac{V_x}{60} = 0$$

$$\textcircled{1} \quad 13V_a - V_x = 2880$$

$$\textcircled{2} \quad -V_a + 8V_x = 720$$

$$V_a = 230.7 \text{ V} \Rightarrow V_{ab} = 230.7 \text{ V}$$

$$V_x = 118.8 \text{ V}$$

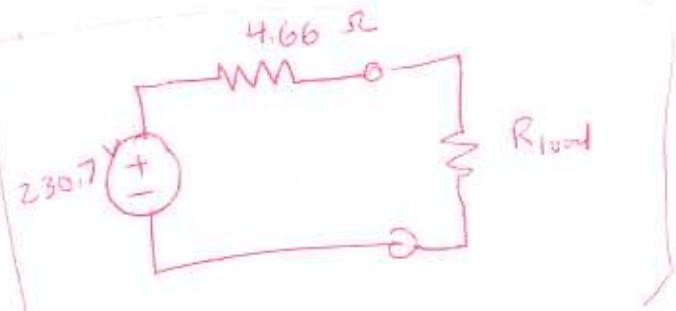


4. When an armature voltage of $24V_{DC}$ is applied to a loaded permanent magnet DC motor with $R_A = 0.8\Omega$ and $K_v = 0.1592V \cdot s$, it spins at 1200 rpm.

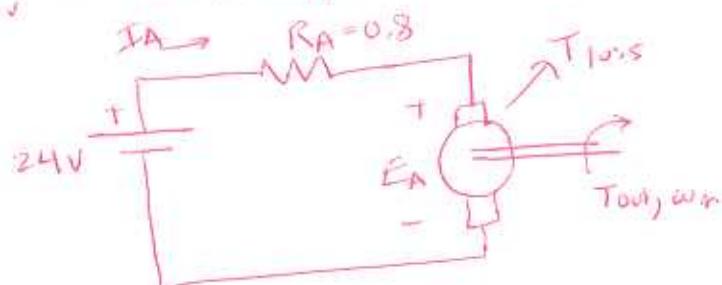- a. Determine the loss torque, T_{loss} , if this motor is 70% efficient at this speed.

$$\omega_m = \frac{1200 \text{ rpm}}{\text{min}} \cdot \frac{1 \text{ min}}{60 \text{ sec}} \cdot \frac{2\pi \text{ rad}}{1 \text{ rev}} = 125.7 \text{ rad/s}$$

$$E_A = K_v \omega_m \\ = (0.1592)(125.7) \\ = 20 \text{ V}$$



$$I_A = \frac{V_T - E_A}{R_A} = \frac{24 - 20}{0.8} = 5 \text{ A}$$

$$P_{in} = V_T I_A = (24 \times) 5 \text{ A} = 120 \text{ W}$$

$$P_{loss, total} = \underbrace{0.3 \cdot 120 \text{ W}}_{\uparrow(1-\eta)} = 36 \text{ W}$$

$$P_{RA} = I^2 R_A = 25^2 (0.8) = 20 \text{ W} \Rightarrow \text{power loss due to } T_{loss} \text{ is } 36 - 20 \text{ W} = 16 \text{ W}$$

$$P_{loss} = T_{loss} \cdot \omega_m$$

$$16 \text{ W} = \frac{T_{loss} \cdot 125.7}{\boxed{T_{loss} = 0.127 \text{ N} \cdot \text{m}}}$$

- b. If an external resistance of 0.8Ω were placed in series with the armature (R_a) with the same T_{load} and T_{loss} , what would be the new speed and efficiency?

$$\text{Ans} \quad T_{load} = \frac{0.7(120)}{\omega_M} = 0.668 \text{ N}\cdot\text{m}$$

$$T_{dev} = T_{load} + T_{loss} = 0.668 + 0.127 \\ = 0.796 \text{ N}\cdot\text{m}$$

$$T_{dev} = K_v I_A \Rightarrow I_A = \frac{T_{dev}}{K_v} = \frac{0.796}{0.1592} = 5 \text{ A (still)}$$

$$E_A = V_T - I_A (0.8 + 0.8) \\ = 24 - 5(1.6) \\ = 16 \text{ V}$$

$$\Rightarrow E_d < K_v \omega$$

$$\omega = \frac{E_d}{K_v} = \frac{16}{0.1592} = 100.5 \text{ rad/sec} \\ (\text{N} = 960 \text{ rpm})$$



$$P_{out} = T_{load} \omega \\ = (0.668)(100.5) = 67.2 \text{ W}$$

$$P_{in} = (24 \text{ V})(5) = 120 \text{ W}$$

$$\eta = \frac{P_{out}}{P_{in}} = \frac{67.2}{120} = 0.5598$$

$\boxed{56.0\%}$

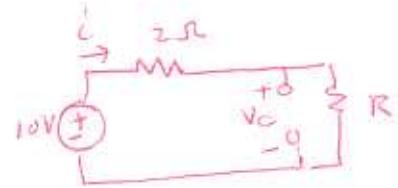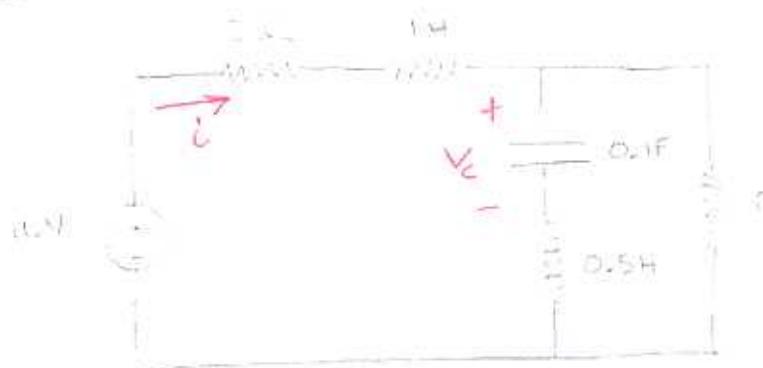5. Find the value of R that will result in a total steady-state stored energy of 10J in the following DC circuit.



- In steady-state, capacitor becomes open circuit, therefore the 0.5H inductor will store no energy.

- Total energy = $\frac{1}{2} L i^2 + \frac{1}{2} C V_c^2$

- note that in steady state, $V_c = iR$

thus $10 = \frac{1}{2} (1) i^2 + \frac{1}{2} C (iR)^2$

$$10 = \frac{i^2}{2} + \frac{i^2 R^2}{20}$$

$$200 = (10 + R^2) i^2$$


- also, from steady state $i = \frac{10}{(2+R)}$

- thus (2 eq, 2 unknown)

$$200 = (10 + R^2) \left(\frac{10}{2+R} \right)^2$$

$$\boxed{R = 0.243 \Omega}$$

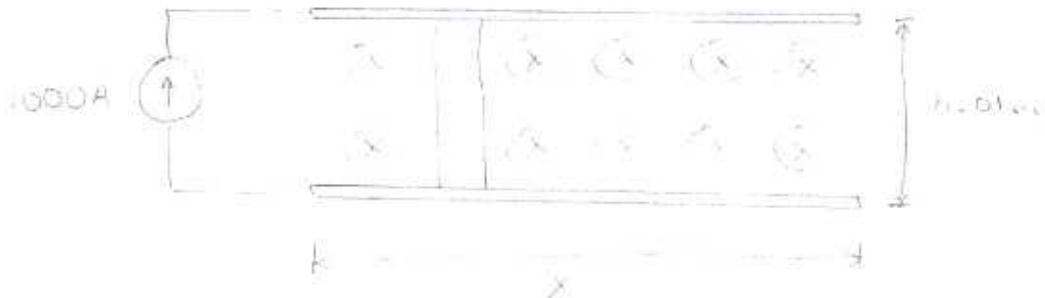6. Consider the following linear DC motor where $B = 1.5\text{T}$ and the mass of the projectile is 1kg.



- a. Determine the barrel length x necessary to result in a launch energy of 60J.

$$W = \frac{1}{2}mv^2 \quad \cancel{x}$$

$$60 = \frac{1}{2}(1)v^2 \Rightarrow v = \sqrt{120} = 10.95 \text{ m/s}$$

$$F = B \cdot l \cdot i = (1.5)(0.01)(1000) = 15 \text{ N}$$

$$a = \frac{F}{m} = \frac{15 \text{ N}}{1 \text{ kg}} = 15 \text{ m/s}^2$$

$$W = F \cdot x$$

$$60 = 15 \cdot x$$

$$\boxed{x = 4 \text{ m}}$$

- b. Find the time to launch:

$$\cancel{\bullet} \quad x = \frac{1}{2}at^2$$

$$4 = \frac{1}{2}(15)t^2$$

$$t = \sqrt{\frac{8}{15}} = \boxed{0.730 \text{ sec}}$$

$$v = at$$

$$10.95 = 15t$$

$$\boxed{t = 0.730}$$

- c. How much current would be required if you wished to shorten the launch time to 0.5s (keeping x the same).

If $x = 4 \text{ m}$ and $t = 1/2 \text{ sec}$


$$x = 1/2 a t^2$$

$$4 = 1/2 a (1/2)^2 \Rightarrow a = 32 \text{ m/s}^2$$

$$F = Bl i \quad F = ma$$

$$\Rightarrow i = \frac{F}{Bl} = \frac{ma}{Bl} = \frac{(1)(32)}{(1.5)(0.4)} = \boxed{2133 \text{ A}}$$

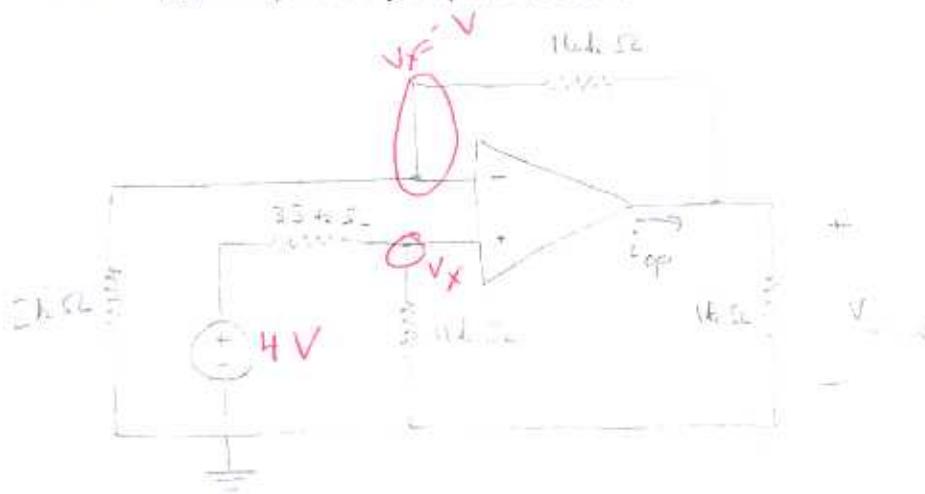7. Find V_{out} and i_{op} in the op-amp circuit below.



$$\textcircled{1} \quad V_x = \frac{11k}{11k+33k} \cdot 4 = 1V$$

\textcircled{2} KCL @ inverting input

$$\frac{1}{2k} + \frac{1 - V_{out}}{16k} = 0$$

$$8 + 1 - V_{out} = 0 \Rightarrow \boxed{V_{out} = 9V}$$


\textcircled{3} KCL @ V_{out}

$$\frac{V_{out} - 1}{16k} + \frac{V_{out}}{1k} = i_{op}$$

$$\frac{8}{16k} + \frac{9}{1k} = i_{op}$$

$$\boxed{i_{op} = 9.5 \text{ mA}}$$

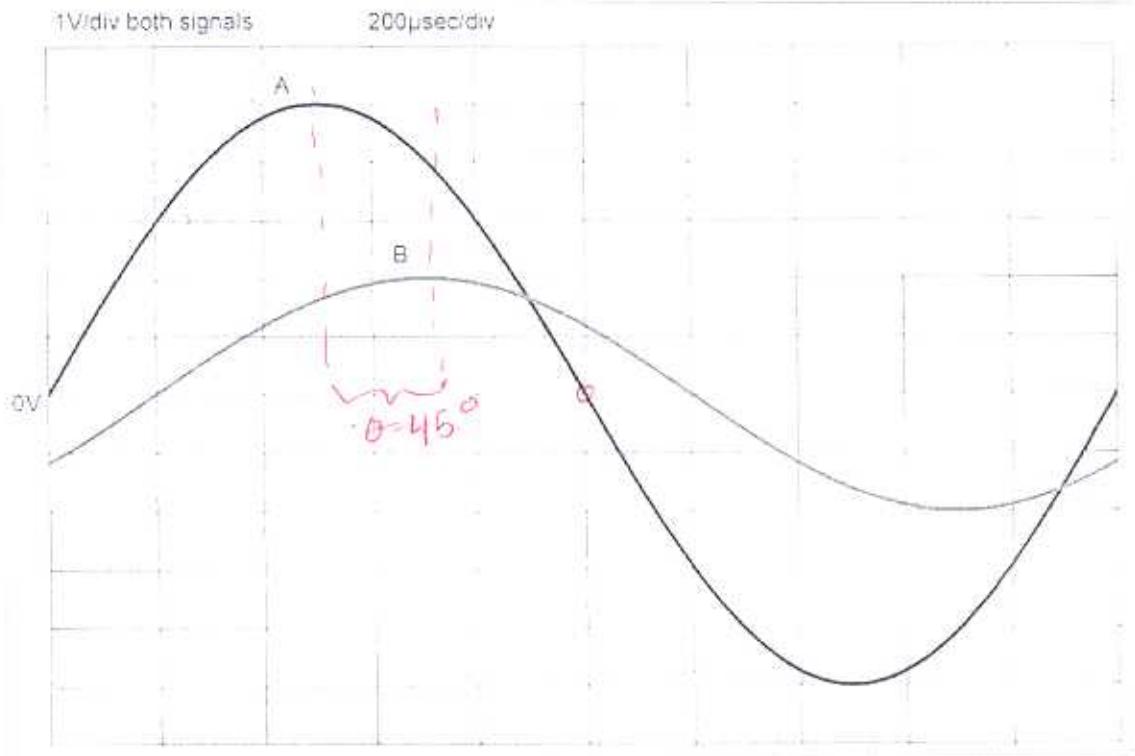8. Given the following sinusoidal waveforms:



a. Find the frequency of the two signals (Hz)

$$T = (10 \text{ div})(200 \mu\text{s}/\text{div}) = 0.002 \quad f = \frac{1}{T} = \boxed{500 \text{ Hz}}$$

b. What is the rms value of signal A?

$$V_m = (5 \text{ div})(1 \text{ V/div}) = 5 \text{ V} \quad V_{rms} = \frac{5}{\sqrt{2}} = \boxed{3.54 \text{ V}_{rms}}$$


c. What is the average value of signal B?

$$0 \text{ V}$$


d. Which signal leads and by how much?

$$\text{A leads by } 45^\circ$$

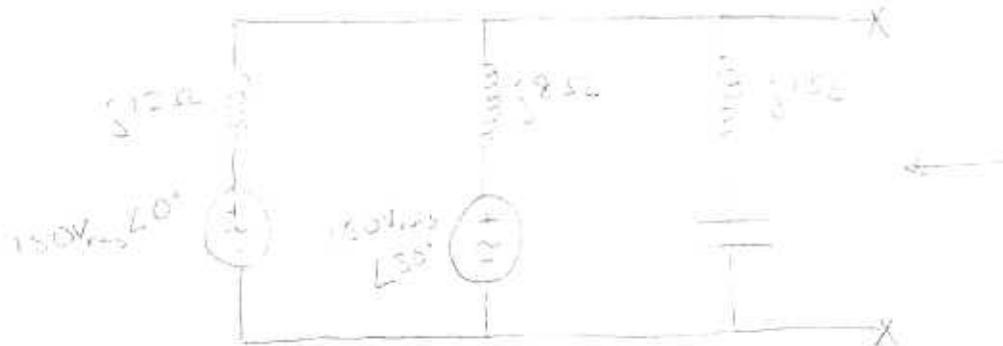9. Find the Thevenin equivalent of the following AC circuit from the terminals indicated:



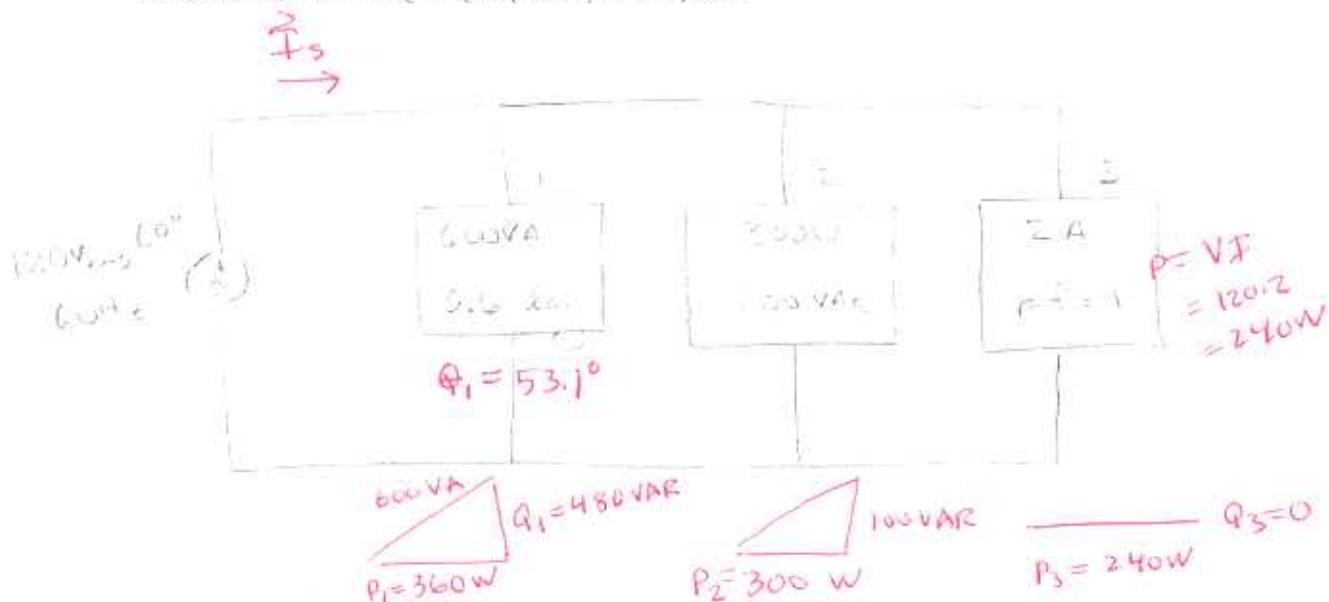10. Given the following single-phase power system



a. Determine the magnitude of the source current.

$$\text{Ansatz} \quad P_{\text{total}} = 360 + 300 + 240 = 900 \text{ W}$$

$$Q_{\text{total}} = 480 + 100 = 580 \text{ VAR}$$

$$S_{\text{total}} = \sqrt{900^2 + 580^2} = 1071 \text{ VA}$$

$$|I_s| = \frac{S_{\text{total}}}{V_s} = \boxed{8.92 \text{ Arms}}$$

- b. What capacitance in parallel with the loads is required to raise the power factor to 0.95 lagging?

$$\theta_2 = \cos^{-1}(0.95)$$


$$Q_1 = 580 \text{ VAR}$$

$$Q_2 = 900 \tan(18.2^\circ) = 295.8 \text{ VAR}$$

$$Q_c = Q_1 - Q_2 = -284.2 \text{ VAR}$$

$$C = \frac{Q_c}{\omega V^2} = \frac{284.2}{377 \cdot 120^2} = \boxed{52.3 \mu F}$$

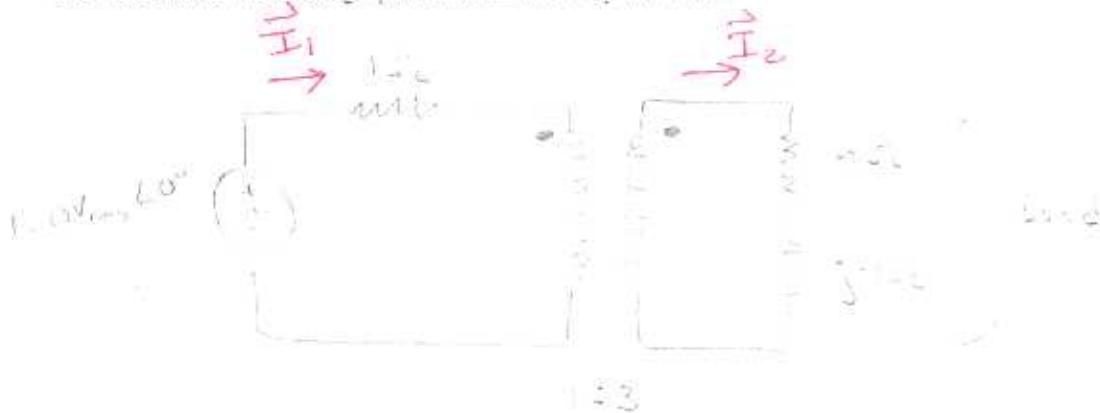11. Determine the average power consumed by the load:



$$Z_R = \frac{1}{3^2} (9 + j9) = 1 + j1$$


$$\vec{I}_1 = \frac{120\angle 0^\circ}{1 + 1 + j} = 53.67 \angle -26.6^\circ \text{ A}$$

$$\vec{I}_2 = \frac{1}{3} \cdot \vec{I}_1 = 17.89 \angle -26.6^\circ \text{ A}$$

in the load, \$9\Omega\$ is the only element to dissipate average power (P)

$$\begin{aligned} P_{\text{load}} &= |\vec{I}_2|^2 R \\ &= (17.89)^2 \cdot 9 = \boxed{2880 \text{ W}} \end{aligned}$$

12. Given the following 3-phase system

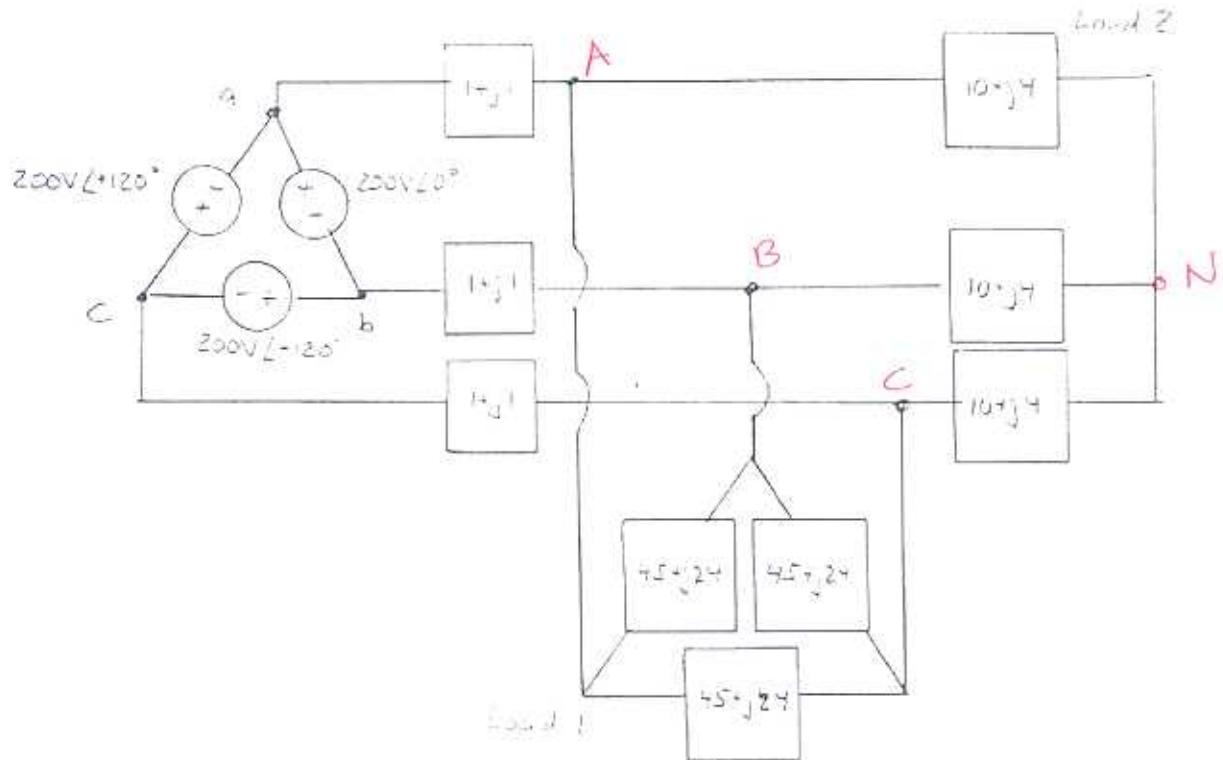

a. Find the total average and reactive power supplied to the 2 loads (combined).

Convert load 1 to Y-connection $Z_{\Delta 1} = 45 + j24 \rightarrow Z_Y = 15 + j8$

both loads 1 and 2 are Y-connected, combine them in parallel,


to create a combined load Z_Y

$$Z_Y = (15 + j8) \parallel (10 + j4) = 6.603 \angle 24.2^\circ \Omega$$

- convert source from $\Delta \rightarrow Y$

$$\vec{V}_{ab} = \sqrt{3} \vec{V}_{an} \angle 30^\circ \Rightarrow \vec{V}_{an} = \frac{200 \angle 0^\circ}{\sqrt{3} \angle 30^\circ} = 115.5 \angle -30^\circ$$

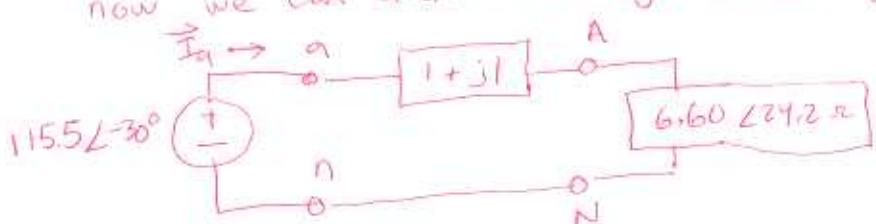now we can draw a single-phase equivalent, thus \vec{I}_a



$$\begin{aligned} \vec{I}_a &= \frac{115.5 \angle -30^\circ}{1+j1 + 6.603 \angle 24.2^\circ} \\ &= 14.54 \angle -57.9^\circ A \end{aligned}$$

$$\text{Thus } \vec{S}_{\text{Total}} = 3 \vec{V}_{an} \vec{I}_a^* = 3 |\vec{I}_a|^2 Z_{\text{load}}$$

$$= 3 |14.54|^2 \cdot 6.603 \angle 24.2^\circ = \boxed{3819 + 1719 \text{ VA}}$$

b. Find the line voltage at the loads.

$$\vec{V}_{AN} = \vec{I}_A \cdot (6.603 \angle 24.2^\circ) = 96.0 \angle -33.6^\circ$$

$$\vec{V}_{AB} = \sqrt{3} \vec{V}_{AN} \angle 30^\circ$$

$$\left. \begin{aligned} \vec{V}_{AB} &= 166.3 \angle -3.6^\circ \text{ V} \\ \vec{V}_{BC} &= 166.3 \angle -123.6^\circ \text{ V} \\ \vec{V}_{CA} &= 166.3 \angle 116.4^\circ \text{ V} \end{aligned} \right\}$$