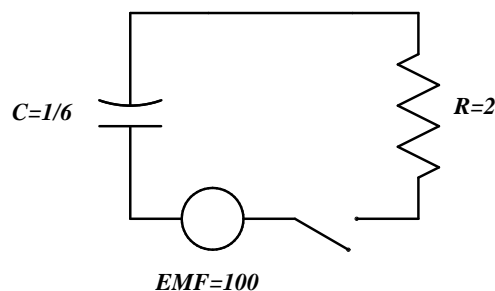


**III. Practice Problem 1: R-C DC Circuit**

**Task:** Work on solving for the charge for the given circuit; indicated links give (partial) solutions.



An R-C circuit consists of a 100 volt DC battery connected in series with a 2 ohm resistor and a 1/6 farad capacitor; there is no initial charge on the capacitor and no current flows until the switch is closed. The associated Initial Value Problem is

$$2Q'(t) + \frac{Q(t)}{1/6} = 100, \quad Q(0) = 0$$

**Method of Separation of Variables:**

- [a] Put the ODE in differential form.
- [b] Use algebra to separate variables.
- [c] Integrate both sides of the preceding equation to get a general solution to the ODE.
- [d] Use the initial condition to compute the value of the arbitrary constant and determine the implicit solution to the IVP.
- [e] Use the rules of logs and exponentials in order to solve the implicit solution to the ODE for the charge  $Q(t)$  for this circuit.
- [f] Rework the solution when the capacitor in this circuit is charged to 30 coulombs at the time when the switch is closed.

[a] Put the ODE in differential form.

The ODE

$$2Q'(t) + \frac{Q(t)}{1/6} = 100$$

becomes

$$Q'(t) + 3Q(t) = 50$$

or

$$\frac{dQ}{dt} = 50 - 3Q$$

which, after multiplying through by  $dt$ , becomes

$$dQ = (50 - 3Q) dt$$

[b] Use algebra to separate variables.

The differential form

$$dQ = (50 - 3Q) dt$$

can be written

$$\frac{dQ}{50 - 3Q} = dt$$

so that all terms involving  $Q$  are on one side of the equation and all terms involving  $t$  on the other side.

[c] Integrate both sides of the preceding equation to get a general solution to the ODE.

Integrating both sides of

$$\frac{dQ}{50 - 3Q} = dt$$

gives

$$\int \frac{dQ}{50 - 3Q} = \int dt$$

We use the substitution

$$x = 50 - 3Q$$

to get  $\frac{dx}{dQ} = -3$

or  $dQ = -\frac{1}{3}dx$

so that

$$\begin{aligned} \int \frac{1}{50 - 3Q} dQ &= \int \frac{1}{x} \left( -\frac{1}{3} dx \right) \\ &= -\frac{1}{3} \int \frac{1}{x} dx \\ &= -\frac{1}{3} \ln |x| + C \\ &= -\frac{1}{3} \ln |50 - 3Q| + C \end{aligned}$$

Hence the general solution to the ODE in implicit form is

$$-\frac{1}{3} \ln |50 - 3Q| = t + C$$

[d] Use the initial condition to compute the value of the arbitrary constant and determine the implicit solution to the IVP.

Since  $Q = 0$  when  $t = 0$ , we put  $t = 0$  into

$$-\frac{1}{3} \ln |50 - 3Q| = t + C$$

to get

$$-\frac{1}{3} \ln |50 - 0| = 0 + C \implies C = -\frac{1}{3} \ln 50$$

This leads us to the solution to the IVP in implicit form:

$$-\frac{1}{3} \ln |50 - 3Q| = t - \frac{1}{3} \ln 50$$

or, multiplying through by  $-3$ ,

$$\ln |50 - 3Q| = \ln 50 - 3t$$

[e] Use the rules of logs and exponentials in order to solve the implicit solution to the ODE for the charge  $Q(t)$  for this circuit.

Take the antilogarithm of both sides of the solution to the IVP

$$\ln |50 - 3Q| = \ln 50 - 3t$$

to get

$$e^{\ln|50-3Q|} = e^{\ln 50 - 3t}$$

which, when simplified, yields

$$|50 - 3Q| = 50 e^{-3t}$$

or

$$50 - 3Q = \pm 50 e^{-3t}$$


Since  $Q = 0$  when  $t = 0$ , the sign must be  $+$ , allowing us to solve for  $Q$ :

$$50 - 3Q = +50 e^{-3t}$$

or

$$Q(t) = \frac{50}{3} (1 - e^{-3t})$$

whose graph is plotted below.

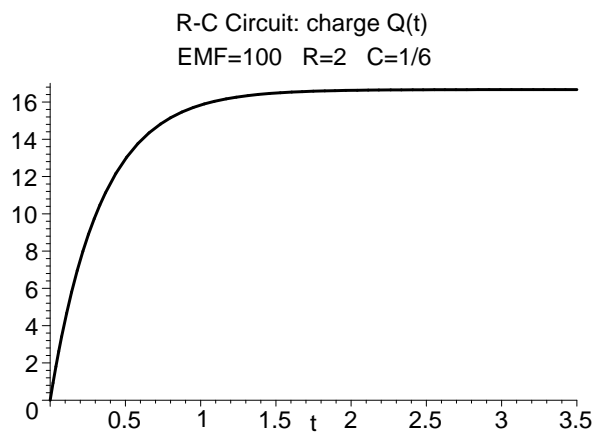

[f] Rework the solution when the capacitor in this circuit is charged to 30 coulombs at the time when the switch is closed.

Start with the general solution

$$-\frac{1}{3} \ln |50 - 3Q| = t + C$$

from part [c] and substitute  $Q = 30$  and  $t = 0$ :

$$-\frac{1}{3} \ln |50 - 3(30)| = 0 + C$$

which yields

$$C = -\frac{1}{3} \ln(40)$$

Hence

$$-\frac{1}{3} \ln |50 - 3Q| = t - \frac{1}{3} \ln(40)$$

which we can solve as before.

Multiply by  $-3$ :

$$\ln |50 - 3Q| = -3t + \ln(40)$$

Take antilogs:

$$|50 - 3Q| = e^{-3t + \ln(40)}$$

Simplify exponentials:

$$e^{-3t + \ln(40)} = e^{-3t} \times e^{\ln(40)} = e^{-3t} \times 40$$

to arrive at:

$$|50 - 3Q| = 40 e^{-3t}$$

or

$$50 - 3Q = \pm 40 e^{-3t}$$

Now  $Q = 30$  when  $t = 0$  means

$$50 - 3(30) = \pm 40 e^0$$

or

$$-40 = \pm 40$$

So the sign must be  $-$  and the solution to the IVP is

$$50 - 3Q = -40 e^{-3t}$$

or

$$Q(t) = \frac{10}{3} (5 + 4e^{-3t})$$

Charge (below left) and current (below right) are plotted for  $Q(0) = 0$  (thinner curve) and  $Q(0) = 30$  (thicker curve).

