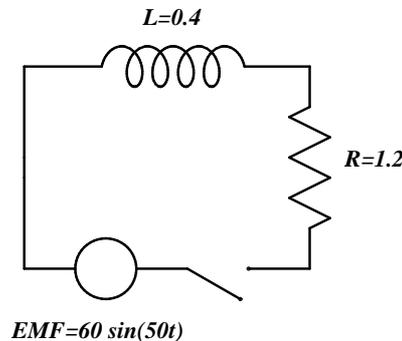


III. Practice Problem 2: R-L AC Circuit

Task: Work on solving for the current for the given circuit; indicated links give (partial) solutions.



An R-L circuit consists of a $60 \sin(50t)$ volt AC generator connected in series with a 0.4 henry inductor and a 1.2 ohm resistor; no current flows until the switch is closed. The associated Initial Value Problem is

$$0.4 I'(t) + 1.2 I(t) = 60 \sin(50t), \quad I(0) = 0$$

Method of Integrating Factor:

- [a] Put the ODE in standard form.
- [b] Determine the integrating factor μ .
- [c] Multiply the standard form ODE by the integrating factor.
- [d] Use the product rule for derivatives to simplify the preceding equation so that $[\mu I]'$ is on one side of it.
- [e] Integrate both sides of the preceding equation with respect to t .
- [f] Solve the preceding equation for the general solution I .
- [g] Use the initial condition to determine the current $I(t)$ for this circuit and graph $I(t)$.
- [h] Determine the steady-state current and the transient current for this circuit and graph both.

[a] Put the ODE in standard form.

After dividing through by the coefficient of $I'(t)$

$$0.4 I'(t) + 1.2 I(t) = 60 \sin(50t)$$

becomes

$$I'(t) + 3 I(t) = 150 \sin(50t)$$

[b] Determine the integrating factor μ .

From the general standard form ODE $y' + p(x)y = q(x)$ we recognize that

$$I'(t) + 3I(t) = 150 \sin(50t)$$

has $p(t) = 3$ and so

$$\mu = e^{\int p(t) dt} = e^{\int 3 dt} = e^{3t}$$

[c] Multiply the standard form ODE by the integrating factor.

Standard form:

$$I'(t) + 3I(t) = 150 \sin(50t)$$

Integrating factor:

$$\mu = e^{3t}$$

Product:

$$e^{3t}I' + 3e^{3t}I = 150e^{3t} \sin(50t)$$

[d] Use the product rule for derivatives to simplify the preceding equation so that $[\mu I]'$ is on one side of it.

By the product rule

$$e^{3t} I' + 3 e^{3t} I = [e^{3t} I]'$$

So the preceding ODE

$$e^{3t} I' + 3 e^{3t} I = 150 e^{3t} \sin(50t)$$

is equivalent to

$$[e^{3t} I]' = 150 e^{3t} \sin(50t)$$

[e] Integrate both sides of the preceding equation with respect to t .

Integrating both sides of

$$[e^{3t} I]' = 150 e^{3t} \sin(50t)$$

yields

$$e^{3t} I = \int 150 e^{3t} \sin(50t) dt$$

[f] Solve the preceding equation for the general solution I .

Using integration by parts on the right hand side of

$$e^{3t}I = \int 150 e^{3t} \sin(50t) dt$$

we get (after rounding numbers to 3 decimal digits)

$$e^{3t}I = e^{3t} [-2.989 \cos(50t) + 0.179 \sin(50t)] + C$$

which, after dividing both sides by e^{3t} , becomes

$$I(t) = -2.989 \cos(50t) + 0.179 \sin(50t) + C e^{-3t}$$

[g] Use the initial condition to determine the current $I(t)$ for this circuit and graph $I(t)$.

From the general solution

$$I(t) = -2.989 \cos(50t) + 0.179 \sin(50t) + C e^{-3t}$$

in the preceding part we have at $t = 0$

$$I(0) = -2.989 \cos(0) + 0.179 \sin(0) + C e^0 = -2.989 + 0 + C = -2.989 + C$$

whereas by the initial condition from the IVP we have

$$I(0) = 0$$


So these two equations together imply that

$$-2.989 + C = 0 \quad \text{or} \quad C = 2.989$$

Putting this C into the general solution yields the circuit current

$$I(t) = -2.989 \cos(50t) + 0.179 \sin(50t) + 2.989 e^{-3t}$$

graphed below.

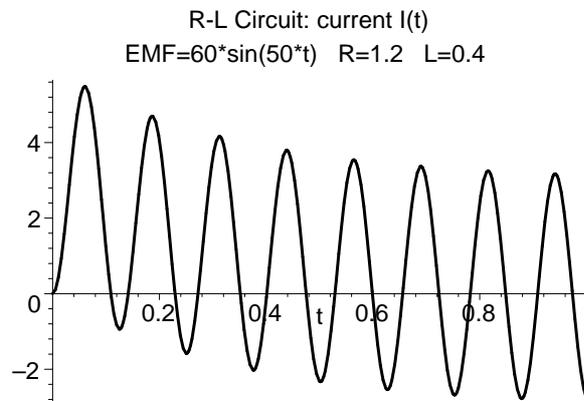

[h] Determine the steady-state current and the transient current for this circuit and graph both.

The current

$$I(t) = -2.989 \cos(50t) + 0.179 \sin(50t) + 2.989 e^{-3t}$$

has a steady-state part $-2.989 \cos(50t) + 0.179 \sin(50t)$ (graphed below left) and a transient part $2.989 e^{-3t}$ (graphed below right).

