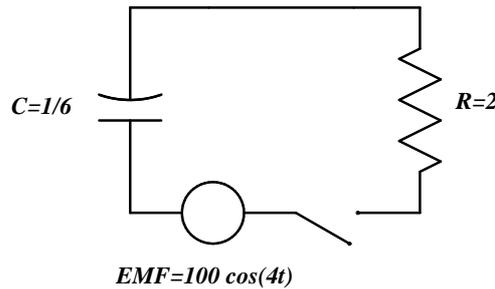


I. Example 1: R-C AC Circuit

Note: a circuit with oscillating or periodic EMF is called an *alternating current circuit* or *AC circuit*.

Questions:

[a] Use Kirchoff's law to write the Initial Value Problem — ODE and initial condition(s) — for the simple circuit consisting of a $100 \cos(4t)$ volt AC generator connected in series with a 2 ohm resistor and a $\frac{1}{6}$ farad capacitor. There is no charge on the capacitor is 0 when the open switch is closed.



- [b] Verify that $Q(t) = 6 \cos(4t) + 8 \sin(4t) - 6e^{-3t}$ is the solution to this IVP.
 [c] Find $I(t)$, the current at time t , then graph both charge $Q(t)$ and current $I(t)$.

Answers:

[a] By Kirchoff's law we have that $E_R + E_C = E$ which, with $E_R = R \cdot Q'(t)$ and $E_C = Q(t)/C$, translates into the Initial Value Problem (for $t \geq 0$)

$$2Q'(t) + \frac{1}{1/6}Q(t) = 100 \cos(4t), \quad Q(t) = 0 \quad \text{at} \quad t = 0$$

or

$$Q'(t) + 3Q(t) = 50 \cos(4t), \quad Q(t) = 0 \quad \text{at} \quad t = 0 \quad (*)$$

[b] If $Q(t) = 6 \cos(4t) + 8 \sin(4t) - 6e^{-3t}$ then its derivative

$$\begin{aligned} Q'(t) &= 6(-4 \sin(4t)) + 8(4 \cos(4t)) - 6(-3e^{-3t}) \\ &= -24 \sin(4t) + 32 \cos(4t) + 18e^{-3t} \end{aligned}$$

and so the left hand side of the ODE in (*) above becomes


$$\begin{aligned} Q'(t) + 3Q(t) &= -24 \sin(4t) + 32 \cos(4t) + 18e^{-3t} + 3(6 \cos(4t) + 8 \sin(4t) - 6e^{-3t}) \\ &= -24 \sin(4t) + 32 \cos(4t) + 18e^{-3t} + 18 \cos(4t) + 24 \sin(4t) - 18e^{-3t} \\ &= 50 \cos(4t) \end{aligned}$$

Hence $Q(t)$ satisfies the ODE in (*). Also, $Q(0) = 6 \cos(0) + 8 \sin(0) - 6e^0 = 6 + 0 - 6 = 0$ and $Q(t)$ also satisfies the IC in (*).

[c] Current is the time derivative of charge:

$$I(t) = Q'(t) = -24 \sin(4t) + 32 \cos(4t) + 18e^{-3t}, \quad t > 0$$

Graphs of $Q(t)$ and $I(t)$ are below.

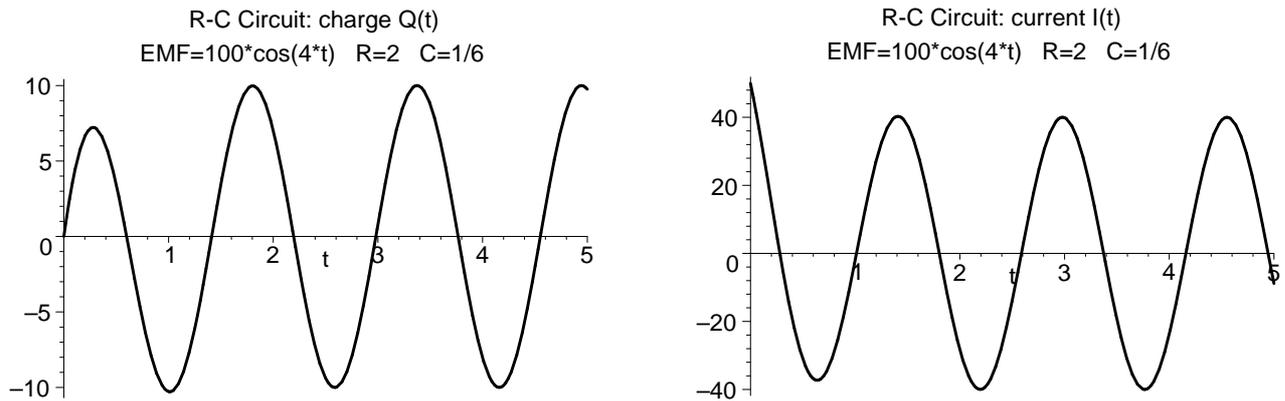

Notice that $Q(t)$ settles into a *steady-state* $6 \cos(4t) + 8 \sin(4t)$ after the *transient term* $6e^{-3t}$ “dies off” (converges to 0). Can you identify the *steady-state term* and the *transient term* for $I(t)$?