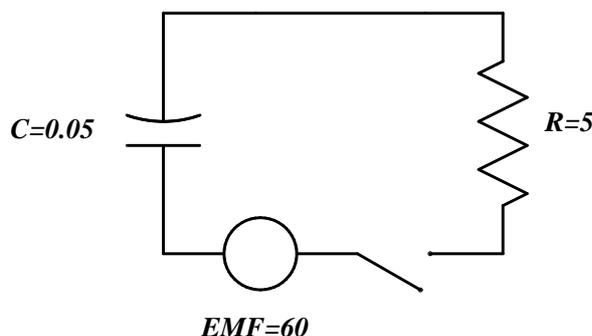


I. Example 2: R-C DC Circuit**Questions:**

[a] Use Kirchhoff's law to write the Initial Value Problem — ODE and initial condition(s) — for the simple circuit consisting of a 60 volt DC battery connected in series with a 0.05 farad capacitor and a 5 ohm resistor. There is no charge on the capacitor and current flows when the open switch is closed. (Note: This is Exercise #27 on p. 521 and p. 528 of Stewart: **Calculus—Concepts and Contexts**, 2nd ed.)



- [b] Verify that $Q(t) = 3(1 - e^{-4t})$, $t \geq 0$ is the solution to the IVP in part [a].
- [c] Find $I(t)$, the current at time t , then graph both charge $Q(t)$ and current $I(t)$.
- [d] What is the asymptotic limit of $Q(t)$ as $t \rightarrow \infty$? This is called the *steady-state* charge and we will label it Q_∞ .
- [e] At what time t does the charge $Q(t)$ reach 50% of its steady state value?

Answers:

[a] By Kirchhoff's law we have that $E_R + E_C = E$ which, with $E_R = R \cdot Q'(t)$ and $E_C = Q/C$, translates into the Initial Value Problem (for $t \geq 0$)

$$5Q'(t) + \frac{Q(t)}{0.05} = 60, \quad Q(t) = 0 \quad \text{at} \quad t = 0$$

or, after simplifying,

$$Q'(t) + 4Q(t) = 12, \quad Q(t) = 0 \quad \text{at} \quad t = 0 \quad (*)$$

[b] If $Q(t) = 3(1 - e^{-4t})$ then its derivative

$$Q'(t) = 3(0 - (-4)e^{-4t}) = 3(4e^{-4t}) = 12e^{-4t}$$

and so the left hand side of the ODE in (*) above becomes


$$\begin{aligned} Q'(t) + 4Q(t) &= (12e^{-4t}) + 4(3(1 - e^{-4t})) \\ &= 12e^{-4t} + 12 - 12e^{-4t} \\ &= 12 \end{aligned}$$

Hence $Q(t)$ satisfies the ODE of (*). Also, $Q(0) = 3(1 - e^0) = 3(1 - 1) = 0$ and $Q(t)$ also satisfies the IC of (*).

[c] Current is the time derivative of charge:

$$I(t) = Q'(t) = 12e^{-4t} \quad \text{for } t > 0$$

Graphs of $Q(t)$ and $I(t)$ are below.

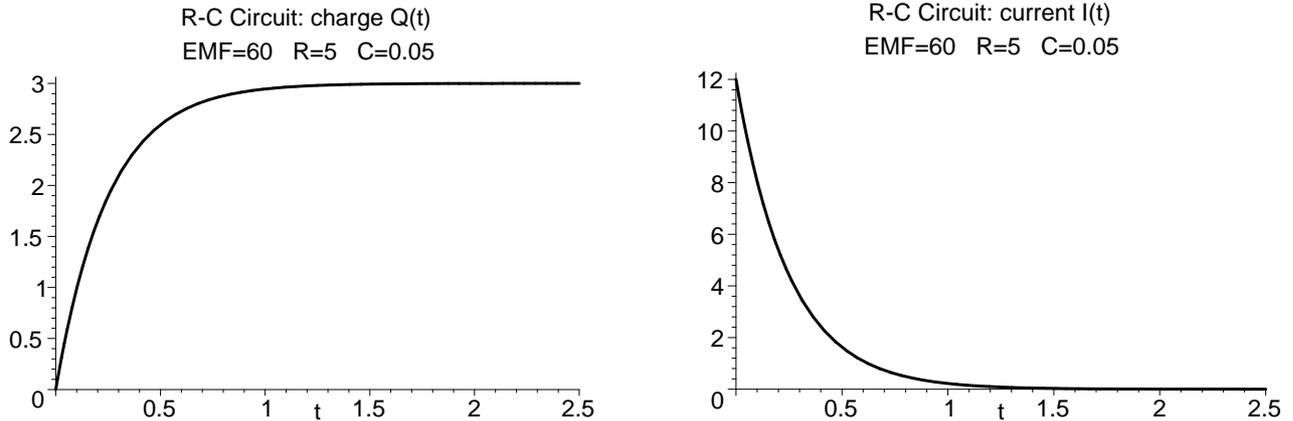

[d] As $t \rightarrow \infty$ we have $Q(t) = 3(1 - e^{-4t}) \rightarrow 3(1 - 0) = 3$ as indicated in the preceding graph of $Q(t)$. The steady-state charge $Q_\infty = 3$ coulombs.

We can see that as $t \rightarrow \infty$ and the graph of $Q(t)$ levels off toward the steady-state value Q_∞ , then the slope of the graph $Q'(t) \rightarrow 0$. If we take the limit $\lim_{t \rightarrow \infty}$ of both sides of the ODE in (*) we get

$$\lim_{t \rightarrow \infty} (Q'(t) + 4Q(t)) = \lim_{t \rightarrow \infty} (12)$$

which yields $0 + 4Q_\infty = 12$ or $Q_\infty = 12/4 = 3$.

Remark. An R-C circuit with constant DC voltage E has steady-state charge $Q_\infty = E \cdot C$.

[d] We need to solve $Q(t) = 0.50I_\infty$. In this circuit, this is the same as $3(1 - e^{-4t}) = 0.5(3)$ which, after canceling the threes, leads to

$$1 - e^{-4t} = 0.5$$

$$\implies e^{-4t} = 0.5$$

$$\implies -4t = \ln(0.5)$$

$$\implies t = -\frac{\ln(0.5)}{4} \approx 0.173$$

This answer could also have been approximated by plotting $Q(t)$ on a graphing calculator and tracing or zooming in on the curve to see where $Q(t)$ achieves the value 1.5 coulombs.

Remark. In R-C DC circuits, a *time unit* τ is defined by $\tau = C \cdot R$. After 5 time units, the charge will be at a little more than 99% of its steady-state: $Q(5\tau) \approx 0.9933 Q_\infty$.

In this example, $\tau = C \cdot R = 0.05 \cdot 5 = 0.25$ and $5\tau = 1.25$ seconds. We see in the preceding graph of $Q(t) = 3(1 - e^{-4t})$ that the charge is indeed very near Q_∞ when t is past 1.25 seconds. Algebraically,

$$Q(1.25) = 3 \left(1 - e^{-4(1.25)} \right) = 3 \left(1 - e^{-5} \right) \approx 3(0.99326) \approx 2.980$$