

**I. Practice Problem 1: R-C AC Circuit**


Work on the questions for the given circuit; indicated links give (partial) solutions.

An R-C circuit consists of a  $60 \cos(4t)$  volt AC generator connected in series with a 5 ohm resistor and a 0.05 farad capacitor.

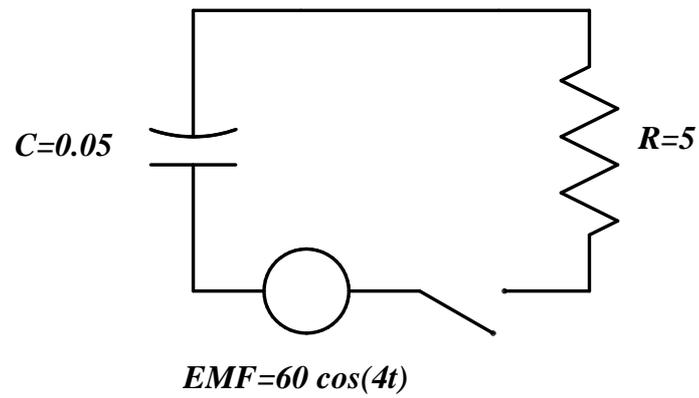**Questions:**

- [a] Sketch the circuit diagram.
- [b] Use Kirchhoff's law to write the Initial Value Problem; assume current starts to flow and that there is no charge on the capacitor when the open switch is closed.
- [c] Verify that  $Q(t) = 1.5 (\cos(4t) + \sin(4t) - e^{-4t})$  is the charge on the capacitor in this circuit for  $t \geq 0$ .
- [d] Find the current  $I(t)$  for the circuit.
- [e] Graph  $Q(t)$  and  $I(t)$ .

[a] Sketch the circuit diagram for the circuit with  $R = 5 \Omega$ ,  $C = 0.05 \text{ F}$ , and  $E(t) = 60 \cos(4t) \text{ V}$ .



[b] Use Kirchhoff's law to write the Initial Value Problem; assume current starts to flow and that there is no charge on the capacitor when the open switch is closed.

$E_R + E_C = E$ , with  $E_R = R \cdot Q'(t)$  and  $E_C = Q(t)/C$ , translates into

$$5Q'(t) + \frac{Q(t)}{0.05} = 60 \cos(4t)$$

which simplifies to

$$Q'(t) + 4Q(t) = 12 \cos(4t), \quad Q(t) = 0 \quad \text{at} \quad t = 0$$

[c] Verify that  $Q(t) = 1.5 (\cos(4t) + \sin(4t) - e^{-4t})$  is the charge on the capacitor in this circuit for  $t \geq 0$ .

If  $Q(t) = 1.5 (\cos(4t) + \sin(4t) - e^{-4t})$  then

$$\begin{aligned} Q'(t) &= 1.5 (-4 \sin(4t) + 4 \cos(4t) + 4e^{-4t}) \\ &= -6 \sin(4t) + 6 \cos(4t) + 6e^{-4t} \end{aligned}$$

and so

$$\begin{aligned} Q'(t) + 4Q(t) &= -6 \sin(4t) + 6 \cos(4t) + 6e^{-4t} + 4 (1.5 (\cos(4t) + \sin(4t) - e^{-4t})) \\ &= -6 \sin(4t) + 6 \cos(4t) + 6e^{-4t} + 6 \cos(4t) + 6 \sin(4t) - 6e^{-4t} \\ &= 12 \cos(4t) \end{aligned}$$

and therefore  $Q(t)$  does satisfy the ODE. Also,  $Q(0) = 1.5 (\cos(0) + \sin(0) - e^0) = 1.5(1 + 0 - 1) = 0$  and  $Q(t)$  thus satisfies the IC.

[d] Find the current  $I(t)$  for the circuit.

Current is the time derivative of charge, or

$$I(t) = Q'(t) = 1.5 (\cos(4t) + \sin(4t) - e^{-4t})' = -6 \sin(4t) + 6 \cos(t) + 6e^{-4t}$$

[e] Graph  $Q(t)$  and  $I(t)$ .

