

I. Practice Problem 2: R-C DC Circuit


Work on the questions for the given circuit; indicated links give (partial) solutions.

An R-C circuit consists of a 2 V DC battery connected in series with a $1 \mu\text{F}$ capacitor and a $5 \text{ k}\Omega$ resistor. (This problem is related to the example on p. 175 of Hambley: **Electrical Engineering—Principles & Applications**, 1997. The symbol k stands for “kilo”, so $5 \text{ k}\Omega$ is 5000 ohms. The symbol μ stands for “micro”, so $1 \mu\text{F}$ stands for 1×10^{-6} farads.)

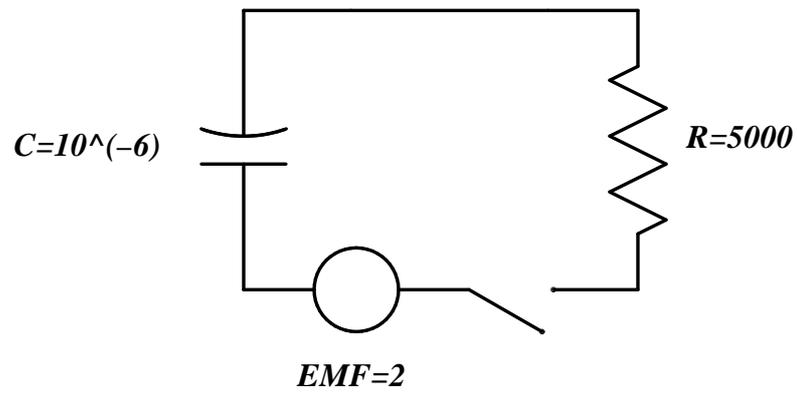Questions:

- [a] Sketch the circuit diagram.
- [b] Use Kirchhoff’s law to write the Initial Value Problem; assume current starts to flow and that there is a charge of $1 \mu\text{C}$ (or micro coulombs) on the capacitor when the open switch is closed.
- [c] Verify that $Q(t) = 2 - e^{-200t} \mu\text{C}$ is the charge on the capacitor in this circuit for $t \geq 0$.
- [d] Find the current $I(t)$ for the circuit.
- [e] Graph $Q(t)$ and $I(t)$.
- [f] What is the steady-state charge Q_∞ for this circuit by formula? Does your answer agree with the pictures in part [e]?
- [g] What is the time constant τ for this circuit? Do the pictures in part [e] suggest that $Q(5\tau) \approx Q_\infty$?

[a] Sketch the circuit diagram for the circuit with $R = 5 \text{ k}\Omega = 5000 \Omega$, $C = 1 \mu\text{F} = 1 \times 10^{-6} \text{ F}$, and $E(t) = 2 \text{ V}$.



[b] Use Kirchhoff's law to write the Initial Value Problem; assume current starts to flow and that there is no charge on the capacitor when the open switch is closed.

$E_R + E_C = E$, with $E_R = R \cdot Q'(t)$ and $E_C = Q(t)/C$, translates into

$$5000 Q'(t) + \frac{Q(t)}{10^{-6}} = 2$$

which simplifies to

$$Q'(t) + 200 Q(t) = 4 \times 10^{-4}, \quad Q(t) = 10^{-6} \quad \text{at} \quad t = 0$$

[c] Verify that $Q(t) = 2 - e^{-200t} \mu\text{C}$ is the charge on the capacitor in this circuit for $t \geq 0$.

If $Q(t) = 2 - e^{-200t} \mu\text{C}$ then

$$\begin{aligned} Q'(t) + 200 Q(t) &= (2 - e^{-200t})' + 200(2 - e^{-200t}) \\ &= (0 + 200e^{-200t}) + 400 - 200e^{-200t} \\ &= 200e^{-200t} + 400 - 200e^{-200t} \\ &= 400 \end{aligned}$$



and therefore $Q(t) = (2 - e^{-200t}) \times 10^{-6}$ does satisfy the ODE. Also, $Q(0) = 2 - e^0 = 2 - 1 = 1 \mu\text{C}$ and $Q(t)$ thus satisfies the IC.

[d] Find the current $I(t)$ for the circuit.

Current is the time derivative of charge; for $t > 0$:


$$I(t) = Q'(t) = (2 - e^{-200t})' \times 10^{-6} = 200 e^{-200t} \text{ micro amps}$$

[e] Graph $Q(t)$ and $I(t)$.

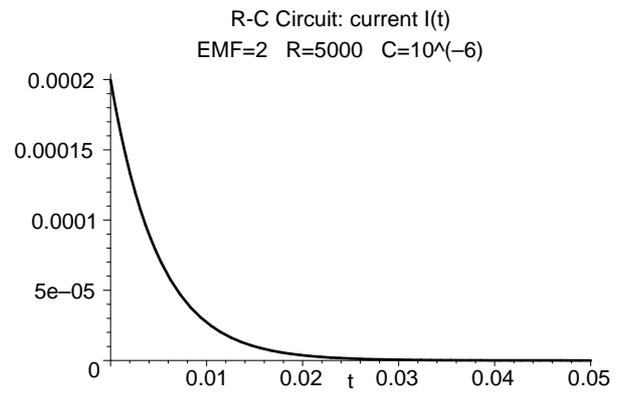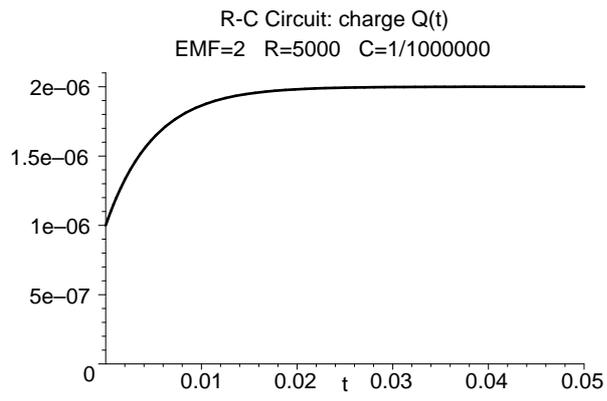

[f] What is the steady-state charge Q_∞ for this circuit by formula? Does your answer agree with the pictures in part [e]?

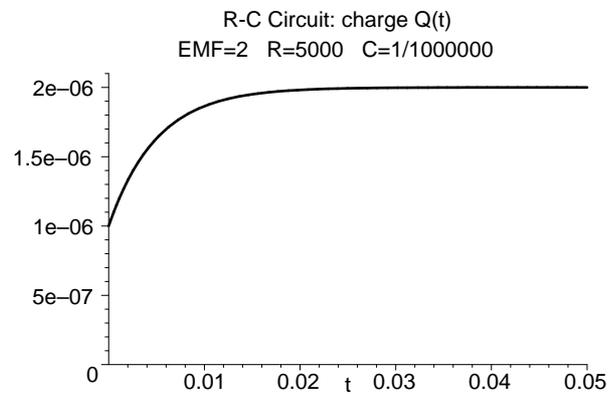$Q_\infty = E \cdot C = 2 \cdot 10^{-6}$ which does indeed look like the horizontal asymptote for the graph of $Q(t)$.



[g] What is the time constant τ for this circuit? Do the pictures in part [e] suggest that $Q(5\tau) \approx Q_\infty$.

For an R-C DC circuit

$$\tau = C \cdot R = 10^{-6} (5 \times 10^3) = 5 \times 10^{-3}$$

Hence $5\tau = 25 \times 10^{-3} = 0.025$ and from the solution given in part [c]:

$$Q(5\tau) = \left(2 - e^{-200 \cdot (0.025)}\right) \times 10^{-6} = (2 - e^{-5}) \times 10^{-6} \approx 1.993 \times 10^{-6}$$

which is very near $Q_\infty = 2 \times 10^{-6}$ as shown in the following graph.

