

### Setting Up Electric Circuit ODE and Verifying Solution

In each of the following problems you are to: [a] use Kirchhoff's law to write down the Initial Value Problem — ODE and initial condition(s) — for the given circuit ; [b] show that the given function is the solution to the IVP . (The quantities  $R$ ,  $L$ ,  $C$ , and  $E$  below do not necessarily represent realistic physical electric circuits.)

- [a]  $L = 25$  henries,  $R = 50$  ohms, no capacitor, constant EMF  $E(t) = 100$  volts, initial current is 0 amps when the switch is closed; [b]  $I(t) = 2 - 2e^{-2t}$
- [a] No inductor,  $R = 30$  ohms,  $C = 0.01$  farads, constant EMF  $E(t) = 50$  volts, initial charge is 0 coulombs when the switch is closed; [b]  $Q(t) = \frac{1}{2} - \frac{1}{2}e^{-10t/3}$
- [a]  $L = 25$  henries,  $R = 25$  ohms, no capacitor, decaying EMF  $E(t) = 50e^{-2t}$  volts, initial current is 0 amps when the switch is closed; [b]  $I(t) = 2e^{-t} - 2e^{-2t}$
- [a] No inductor,  $R = 25$  ohms,  $C = 0.01$  farads, decaying EMF  $E(t) = 50e^{-2t}$  volts, initial charge is 0 coulombs when the switch is closed; [b]  $Q(t) = e^{-2t} - e^{-4t}$
- [a]  $L = 15$  henries,  $R = 40$  ohms, no capacitor, oscillatory EMF  $E(t) = 50 \cos(6t)$  volts, initial current is 0 amps; [b]  $I(t) = \frac{1}{97} (20 \cos(6t) + 45 \sin(6t) - 20e^{-8t/3})$
- [a] No inductor,  $R = 25$  ohms,  $C = 0.005$  farads, oscillatory EMF  $E(t) = 50 \cos(6t)$  volts, initial charge is 0 coulombs; [b]  $Q(t) = \frac{1}{25} (4 \cos(6t) + 3 \sin(6t) - 4e^{-8t})$
- [a] A simple series circuit consists of 25 ohm resistor, a 25 henry inductor, and an EMF  $E(t) = 20e^{-3t} + 10e^{-6t}$  volts; the initial current is 0 amps when the switch is closed; [b]  $I(t) = \frac{1}{25} (12e^{-t} - 10e^{-3t} - 2e^{-6t})$
- [a] A simple series circuit consists of a 20 ohm resistor, a 0.01 farad capacitor, and an EMF  $E(t) = 20e^{-3t} + 10e^{-6t}$  volts; the initial charge on the capacitor is 0 coulombs when the switch is closed; [b]  $Q(t) = \frac{1}{2} (e^{-3t} - e^{-6t})$
- [a] A simple series circuit consists of 25 ohm resistor, a 25 henry inductor, and a decaying oscillatory EMF  $E(t) = 50e^{-3t} \cos(4t)$  volts; the initial current is 0 amps when the switch is closed; [b]  $I(t) = \frac{1}{5} (e^{-t} - e^{-3t} \cos(4t) + 2e^{-3t} \sin(4t))$
- [a] A simple series circuit consists of a 25 ohm resistor, a 0.01 farad capacitor, and a decaying oscillatory EMF  $E(t) = 50e^{-2t} \cos(6t)$  volts; the initial charge on the capacitor is 0 coulombs when the switch is closed; [b]  $Q(t) = \frac{1}{10} e^{-2t} (\cos(6t) + 3 \sin(6t) - e^{-2t})$
- [a] A simple series circuit consists of a 1 henry inductor, 12 ohm resistor, a 0.01 farad capacitor, and a constant EMF  $E(t) = 100$  volts; the initial charge on the capacitor is 0 coulombs and the current is 0 amps when the switch is closed; [b]  $Q(t) = 1 - e^{-6t} (\cos(8t) + (3/4) \sin(8t))$

- 12.** [a] A simple series circuit consists of a 2 henry inductor, 60 ohm resistor, a 0.004 farad capacitor, and a constant EMF  $E(t) = 50$  volts; the initial charge on the capacitor is 0 coulombs and the current is 0 amps when the switch is closed; [b]  $Q(t) = \frac{1}{5} - \frac{1}{4}e^{-5t} + \frac{1}{20}e^{-25t}$