

LC Circuits


SP212 - General Physics II




UNITED STATES
NAVAL ACADEMY

ANNAPOLIS

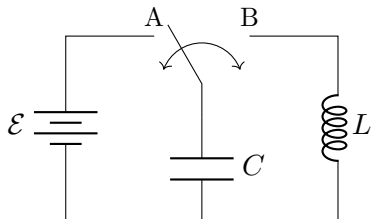Imagine the circuit shown below. The switch is moved left (to position A). The battery quickly charges the capacitor to $Q_{\text{peak}} = C\mathcal{E}$. Then, at time $t = 0$, the switch is flipped right (to position B). What happens?



- ➊ With the battery removed, the capacitor will discharge. Current will flow clockwise.
- ➋ Eventually, the capacitor is uncharged. But at this point the current is large and the inductor causes the current to keep going. This causes the capacitor to recharge *with the opposite polarity*.
- ➌ Eventually the current falls to zero. At this point the capacitor is fully charged, but with opposite polarity from how it started.
- ➍ Current flows counter-clockwise to discharge the capacitor.
- ➎ When the capacitor is uncharged, the current is large and the inductor keeps the current going.
- ➏ Eventually the current falls to zero when the capacitor is back to where it started. The process repeats.

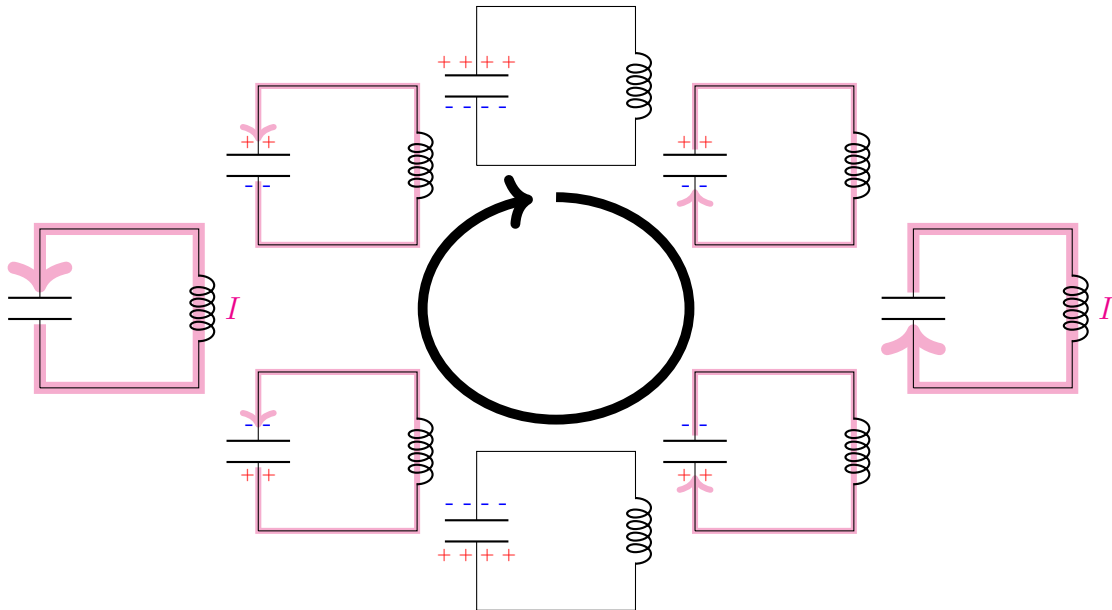

LC circuits

Do a clockwise loop rule. Define Q as positive when the top plate is positive. Define a clockwise current as positive.

$$+\frac{Q}{C} - L\frac{dI}{dt} = 0$$


$$I = -\frac{dQ}{dt} \text{ (positive current leads away from the positive plate).}$$

$$+\frac{Q}{C} + L\frac{d^2Q}{dt^2} = 0 \text{ or } \frac{d^2Q}{dt^2} = -\frac{Q}{LC} = -\omega^2Q \text{ where } \omega = \frac{1}{\sqrt{LC}}$$

Solve this differential equation with initial conditions

$$Q(t=0) = Q_{\text{peak}} \text{ and } I(t=0) = 0:$$
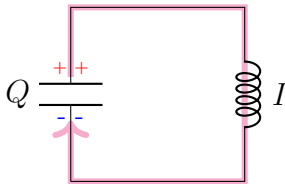
$$Q(t) = Q_{\text{peak}} \cos \omega t \text{ and } I(t) = -\omega Q_{\text{peak}} \sin \omega t$$



$$\omega = \frac{1}{\sqrt{LC}} = 2\pi f = \frac{2\pi}{T}$$

Angular frequency of the oscillation



$$Q(t) = Q_{\text{peak}} \cos \omega t$$

Charge on the capacitor as a function of time

$$I(t) = -\omega Q_{\text{peak}} \sin \omega t$$

Current through the inductor as a function of time

- C is the capacitance in this circuit [units are farads, F]
- L is the inductance in this circuit [units are henries, H]
- ω is the angular frequency of the oscillations [units are radians per second, rad/s]
 - ▶ Note: units are rad/s. Your calculator must be set for radians.
 - ▶ f is the frequency [units are hertz, Hz]; T is the period [units are seconds, s]
- Q_{peak} is the maximum (peak) charge on the capacitor. It is assumed that we define $t = 0$ as a moment when this is the charge on the capacitor.

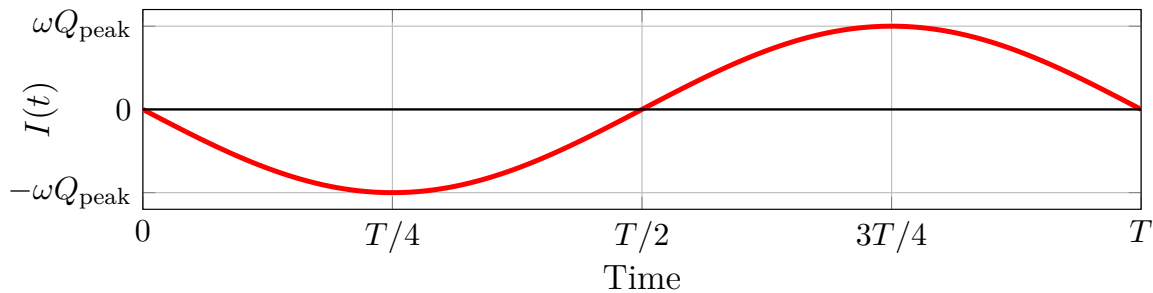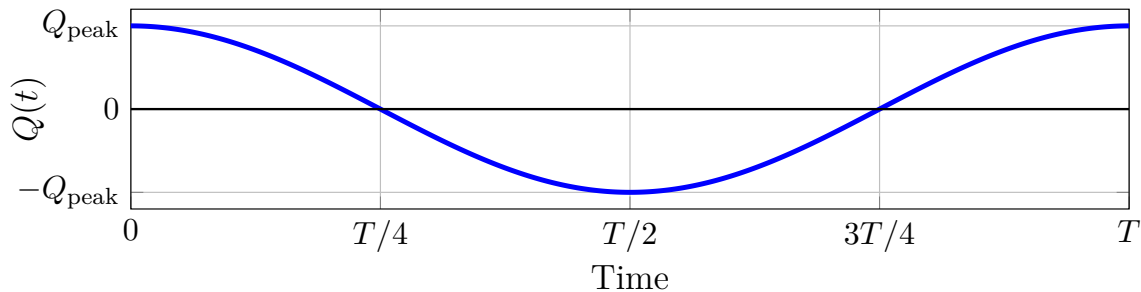

Energy in an LC Circuit

Energy stored in the capacitor: $U_e = \frac{Q^2}{2C} = \frac{[Q_{\text{peak}} \cos \omega t]^2}{2C} = \frac{Q_{\text{peak}}^2}{2C} \cos^2 \omega t$

Energy in an LC Circuit

Energy stored in the capacitor: $U_e = \frac{Q^2}{2C} = \frac{[Q_{\text{peak}} \cos \omega t]^2}{2C} = \frac{Q_{\text{peak}}^2}{2C} \cos^2 \omega t$

Energy stored in the inductor: $U_m = \frac{1}{2}LI^2 = \frac{1}{2}L[-\omega Q_{\text{peak}} \sin \omega t]^2 = \frac{L\omega^2 Q_{\text{peak}}^2}{2} \sin^2 \omega t$

Remember, $\omega = \frac{1}{\sqrt{LC}}$ which means $\frac{\omega^2 L}{2} = \frac{1}{2C}$

This gives $U_m = \frac{Q_{\text{peak}}^2}{2C} \sin^2 \omega t$

Energy in an LC Circuit

Energy stored in the capacitor: $U_e = \frac{Q^2}{2C} = \frac{[Q_{\text{peak}} \cos \omega t]^2}{2C} = \frac{Q_{\text{peak}}^2}{2C} \cos^2 \omega t$


Energy stored in the inductor: $U_m = \frac{1}{2}LI^2 = \frac{1}{2}L[-\omega Q_{\text{peak}} \sin \omega t]^2 = \frac{L\omega^2 Q_{\text{peak}}^2}{2} \sin^2 \omega t$

Remember, $\omega = \frac{1}{\sqrt{LC}}$ which means $\frac{\omega^2 L}{2} = \frac{1}{2C}$

This gives $U_m = \frac{Q_{\text{peak}}^2}{2C} \sin^2 \omega t$

Total energy stored: $U = U_e + U_m = \frac{Q_{\text{peak}}^2}{2C} [\cos^2 \omega t + \sin^2 \omega t] = \frac{Q_{\text{peak}}^2}{2C}$

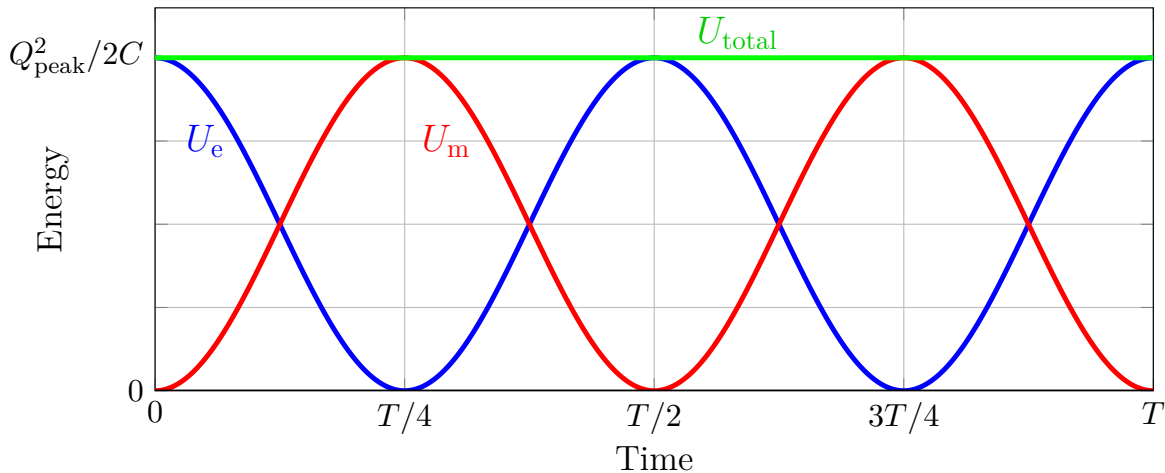This is constant in time! This circuit had no resistor to dissipate heat.



Interesting to note: the energies will cycle twice each period. After half of a period the capacitor is charged with opposite polarity, but $U_e \propto Q^2$ so the minus sign doesn't matter.