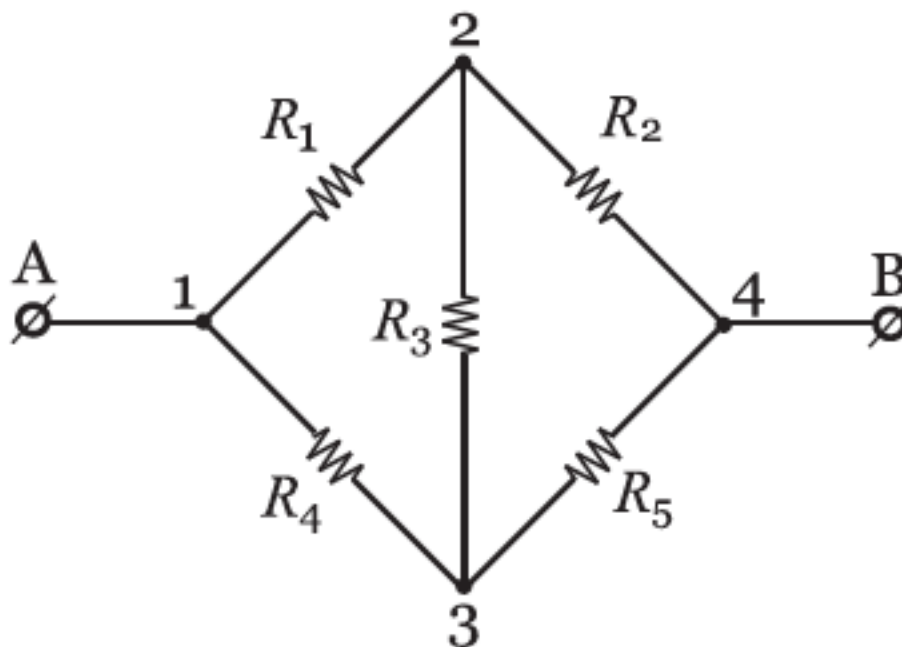


Equivalent Resistance of a Wheatstone Bridge—C.E. Mungan, Fall 2014

ref: AJP 83, 53 (2015)

Find the equivalent resistance of the Wheatstone bridge sketched below.



The method of nodal potentials is simpler than the Kirchhoff method of branch circuits. We assume that point A is connected to the positive terminal of a battery of potential ε , and point B to the negative terminal of zero potential. Let node 2 have potential V_2 and node 3 have potential V_3 . Then the junction rule implies that the sum of the currents into node 2 is zero,

$$\frac{\varepsilon - V_2}{R_1} + \frac{V_3 - V_2}{R_3} + \frac{0 - V_2}{R_2} = 0 \quad (1)$$

and likewise for node 3,

$$\frac{\varepsilon - V_3}{R_4} + \frac{V_2 - V_3}{R_3} + \frac{0 - V_3}{R_5} = 0. \quad (2)$$

Conductance σ is the reciprocal of resistance R . Defining $\sigma_{123} \equiv \sigma_1 + \sigma_2 + \sigma_3$ and likewise for σ_{345} , and $v_2 \equiv V_2 / \varepsilon$ and likewise for v_3 , Eqs. (1) and (2) can be rewritten as

$$\sigma_{123}v_2 - \sigma_3v_3 = \sigma_1 \quad (3)$$

and

$$-\sigma_3v_2 + \sigma_{345}v_3 = \sigma_4. \quad (4)$$

The equivalent conductance of the circuit is the current flowing from the positive to the negative terminal of the battery—equal to the sum of the currents across resistors 2 and 5—divided by the battery voltage,

$$\sigma_{\text{eq}} = \frac{(V_2 - 0)/R_2 + (V_3 - 0)/R_5}{\mathcal{E}} \quad (5)$$

which simplifies to

$$R_{\text{eq}} = (\sigma_2 v_2 + \sigma_5 v_3)^{-1}. \quad (6)$$

Linear equations (3) and (4) are to be solved simultaneously for v_2 and v_3 , and substituted into this expression to get the final solution.